

# Radio **Electronics**

DECEMBER 1992

Combined with

# Electronics NOW

## Build our MODEM/FAX PROTECTOR

and prevent damage from  
surges and transients

## Add an INRUSH-CURRENT LIMITER

to your sensitive  
electronic equipment

## Now you can TALK ON A LIGHT BEAM


with our experimental  
light-beam communicator

## How to put the 555 TIMER IC to work in practical circuits

## How improvements in COMPUTER MONITOR TECHNOLOGY

have made PC's better  
than ever!

## BUILD THIS GLITTER GLOBE

 

Brighten the holidays with this  
fascinating electronic sculpture!



\$3.50 U.S.  
\$3.95 CAN

**GERNSBACK**  
PUBLICATIONS

\*\*\*\*\* CAR-RT SORT \*\* CR03  
750456HRR5165M093 12 P81

NOV 93

RE

53151-8142

# The Fluke 79: More Of A Good Thing

More high-performance features. More advanced measurement capabilities. More of the vital information you need to troubleshoot even the toughest problems — with both analog and digital displays.

Meet the latest, greatest member of our best selling 70 Series II family — the new Fluke 79 digital multimeter.

It picks up where the original family left off. In fact, it's a quantum leap forward — in performance, value and affordability.

It's got the features you'd expect from Fluke. Including high resolution. Fast autoranging. Patented, automatic Touch Hold<sup>®</sup>. A quick continuity beeper. Diode test. Automatic self-test. Battery-conserving sleep mode. And it's just as rugged and reliable as the rest of the 70 Series II family. Easy to operate, too — with one hand.

And thanks to the Fluke 79's proprietary new integrated circuit technology, that's only the beginning. When it comes to zeroing in on tough electrical problems, the Fluke 79 leaves the competition behind:

## Hz

**Frequency:** The Fluke 79's built-in frequency counter lets you measure from below 1 Hz to over 20 kHz. And while you view frequency on the digital display, the analog bar graph shows you AC voltage. So you can see if potentially hazardous voltage is present.



**Fast 63-segment analog bar graph:** The Fluke 79's bargraph moves as fast as the eye can see, updating at a rate of 40 times per second to simulate the functionality of an analog needle. You get the high speed and high resolution you need to detect peaking, nulling and trending.



**Capacitance:** No need to carry a separate dedicated capacitance tester; the Fluke 79 measures capacitance from 10 pF to 9999  $\mu$ F.



Actual Size

## 40 $\Omega$

**Lo-Ohms range:** Our proprietary Lo-Ohms function lets you measure resistance as low as 0.01 ohms. High noise rejection and a test lead Zero Calibration function make the Fluke 79 ideal for detecting small resistance changes.

## SMOOTHING

**Smoothing<sup>™</sup>:** Our exclusive new Smoothing mode gives you a stable digital readout for unstable signals — by displaying the running average of eight readings. No more jitter or "digit rattle" due to noisy signals.

**Get a good thing going:** To put more meter to work for you — at a price that works for you, too — head for your nearest Fluke distributor. For the name of your nearest distributor, or for more product information, call 1-800-87-FLUKE.

The Fluke 79 comes with a yellow holster and patented Flex-Stand<sup>™</sup> — easy to hang from a door or pipe, clip onto a belt or tool kit, or stand at virtually any viewing angle. There's even storage space for test leads.



### Fluke 79 Series II

\$185*
4000 Count Digital Display (9999 in Hz, capacitance, and Lo-Ohms)
63-segment Analog Bar Graph
0.3% Basic DC Voltage Accuracy
Automatic Touch Hold
Diode Test, Audible Continuity Beeper
Autoranging, Manual Ranging
Holster with Flex-Stand
Frequency Counter to over 20 kHz
Capacitance, 10 pF to 9999 $\mu$ F
Lo-Ohms Range with Zero Calibration
Smoothing
700 Hours Battery Life (alkaline)
3-Year Warranty
* Suggested U.S. list price

FLUKE AND PHILIPS  
THE T & M ALLIANCE

John Fluke Mfg. Co., Inc. P.O. Box 9090, M/S 250E Everett, WA 98206. © Copyright 1991. Prices and specifications subject to change without notice. Ad no. 00172.

**FLUKE** <sup>®</sup>

### ON THE COVER



Once again, the holidays are just around the corner, and it's time to start thinking about gift giving and tree trimming. If you agree with us that hand-made items make the nicest gifts and add special sparkle to the holiday decor, be sure to check out the Glitter Globe. Not an ordinary ornament, this sophisticated piece

of "electronic sculpture" is made entirely of electronic components and small circuit boards. The two LED's on each PC board "chase" each other, creating the illusion that the Glitter Globe is spinning. Hanging on the tree, or in a window, it's a sure attention-grabber! Turn to page 35 for all the details.



PAGE 51



PAGE 69



PAGE 43

As a service to readers, ELECTRONICS NOW publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, ELECTRONICS NOW disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry described in ELECTRONICS NOW may relate to or be covered by U.S. patents, ELECTRONICS NOW disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

ELECTRONICS NOW, (ISSN 0033-7862) November 1992. Published monthly by Gernsback Publications, Inc., 500-B Bi-County Boulevard, Farmingdale, NY 11735. Second-Class Postage paid at Farmingdale, NY and additional mailing offices. Second-Class mail registration No. R125166280, authorized at Toronto, Canada. One-year subscription rate U.S.A. and possessions \$19.97, Canada \$27.79 (includes G.S.T. Canadian Goods and Services Tax Registration No. R125166280), all other countries \$28.97. All subscription orders payable in U.S.A. funds only, via international postal money order or check drawn on a U.S.A. bank. Single copies \$3.50. © 1992 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

POSTMASTER: Please send address changes to ELECTRONICS NOW, Subscription Dept., Box 55115, Boulder, CO 80321-5115.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

PLEASE TURN PAGE FOR COMPLETE CONTENTS

## BUILD THIS

- 35 BUILD THE GLITTER GLOBE**  
Add some sparkle to the holidays with this electronic ornament.  
**Ron Holzwarth**
- 43 FAX/MODEM PROTECTOR**  
A low-cost project that safeguards your telephone-based gear.  
**Tom Petruzzellis**
- 47 INRUSH CURRENT LIMITER**  
Protect sensitive electronics with this device.  
**Douglas Wirth**
- 51 LIGHT BEAM COMMUNICATOR**  
The inexpensive "Air Hop" communicates with light!  
**Rodney A. Kreuter**

## COMPUTERS

- 69 MONITOR TECHNOLOGY**  
A look at today's computer monitors.  
**Stan Warner**

## TECHNOLOGY

- 62 THE VERSATILE 555**  
More circuits than you ever thought possible!  
**Ray M. Marston**

## DEPARTMENTS

- |  |   |
|--|---|
| <b>8 VIDEO NEWS</b><br>What's new in this fast-changing field.<br><b>David Lachenbruch</b> | <b>88 DRAWING BOARD</b><br>A SSAVI descrambler.<br><b>Robert Grossblatt</b>                   |
| <b>16 EQUIPMENT REPORT</b><br>Beckman Industrial HD-160 DMM                                | <b>94 AUDIO UPDATE</b><br>Hear today, gone tomorrow.<br><b>Larry Klein</b>                    |
| <b>77 HARDWARE HACKER</b><br>Conventional currents, and more.<br><b>Don Lancaster</b>      | <b>97 COMPUTER CONNECTIONS</b><br>Computers and consumer electronics.<br><b>Jeff Holtzman</b> |

## AND MORE

- |  |                        |
|--|------------------------|
| <b>108 Advertising and Sales Offices</b> | <b>14 Letters</b>      |
| <b>108 Advertising Index</b>             | <b>32 New Lit</b>      |
| <b>91 Buyer's Market</b>                 | <b>22 New Products</b> |
| <b>4 Editorial</b>                       | <b>12 Q&amp;A</b>      |
|  | <b>6 What's News</b>   |

# Electronics NOW<sup>®</sup>

Hugo Gernsback (1884-1967) founder

**Larry Steckler, EHF, CET,**  
editor-in-chief and publisher

### EDITORIAL DEPARTMENT

**Brian C. Fenton,** editor  
**Marc Spiwak,** associate editor  
**Neil Sclater,** associate editor  
**Teri Scaduto,** assistant editor  
**Jeffrey K. Holtzman**  
computer editor  
**Robert Grossblatt,** circuits editor  
**Larry Klein,** audio editor  
**David Lachenbruch**  
contributing editor  
**Don Lancaster**  
contributing editor  
**Kathy Terenzi,** editorial assistant

### ART DEPARTMENT

**Andre Duzant,** art director  
**Injae Lee,** illustrator  
**Russell C. Truelson,** illustrator

### PRODUCTION DEPARTMENT

**Ruby M. Yee,** production director  
**Karen S. Brown**  
advertising production  
**Marcella Amoroso**  
production assistant  
**Lisa Rachowitz**  
editorial production

### CIRCULATION DEPARTMENT

**Jacqueline P. Cheseboro**  
circulation director  
**Wendy Alanko**  
circulation analyst  
**Theresa Lombardo**  
circulation assistant  
**Michele Torriello**  
reprint bookstore

Typography by Mates Graphics  
Cover inset photo by Diversified Photo Services. Background by David P. Dill, Unicorn Stock Photos

Electronics Now is indexed in *Applied Science & Technology Index*, *and Readers Guide to Periodical Literature*, *Academic Abstracts*, and *Magazine Article Summaries*. Microfilm & microfiche editions are available. Contact circulation department for details.

### Advertising Sales Offices listed on page 102.

Electronics Now Executive and Administrative Offices  
**1-516-293-3000.**

Subscriber Customer Service:  
**1-800-288-0652.**

Order Entry for New Subscribers:  
**1-800-999-7139.**



Audit Bureau  
of Circulations  
Member



# DC-2000 MHz AMPLIFIERS

In plastic and ceramic packages, for low-cost solutions to dozens of application requirements, select Mini-Circuits' flatpack or surface-mount wideband monolithic amplifiers. For example, cascade three MAR-2 monolithic amplifiers and end up with a 25dB gain, 0.3 to 2000MHz amplifier for less than \$4.50. Design values and circuit board layout available on request.

It's just as easy to create an amplifier that meets other specific needs, whether it be low noise, high gain, or medium power. Select from Mini-Circuits' wide assortment of models (see Chart), sketch a simple interconnect layout, and the design is done. Each model is characterized with S parameter data included in our 740-page RF/IF Designers' Handbook.

All Mini-Circuits' amplifiers feature tight unit-to-unit repeatability, high reliability, a one-year guarantee, tape and reel packaging, off-the-shelf availability, with prices starting at 99 cents.

Mini-Circuits' monolithic amplifiers...for innovative do-it-yourself problem solvers.



Models above shown actual size

from **99¢**

Unit price \$ (1-25 qty)  
for plastic surface-mount add suffix SM (example MAR-1SM)

PLASTIC SURFACE-MOUNT	MAR-1	MAR-2	++VAM-3 1.45	MAR-3	MAR-4	+VAM-6 1.29	++VAM-7 1.75	MAR-8	MAV-11 2.15
	1.04	1.40	1.50	1.60	1.34	1.80	1.75		
	MAV-1 1.15	+MAV-2 1.45	+MAV-3 1.55	MAV-4 1.65					
CERAMIC SURFACE-MOUNT	RAM-1	RAM-2	RAM-3	RAM-4	RAM-6	RAM-7	RAM-8		
	4.95	4.95	4.95	4.95	4.95	4.95	4.95		
PLASTIC FLAT-PACK	MAV-1	+MAV-2	+MAV-3	MAV-4				MAV-11	
	1.10	1.40	1.50	1.60				2.10	
	MAR-1 0.99	MAR-2 1.35	MAR-3 1.45	MAR-4 1.55	MAR-6 1.29	MAR-7 1.75	MAR-8 1.70		
Freq. MHz, DC to	1000	2000	2000	1000	2000	2000	1000	1000	
Gain, dB at 100MHz	18.5	12.5	12.5	8.3	20	13.5	32.5	12.7	
Output Pwr. +dBm	1.5	4.5	10.0	12.5	2.0	5.5	12.5	17.5	
NF, dB	5.5	6.5	6.0	6.5	3.0	5.0	3.3	3.6	

Notes: + Frequency range DC-1500MHz ++ Gain 1/2 dB less than shown

designer's kit, KH-1 available only \$59.95 includes:

40 AMPLIFIERS\* 10 MAR-1, 10 MAR-3, 10 MAR-4, 10 MAR-8


150 CAPACITORS\* 50 100 pf, 50 1,000 pf, 50 10,000 pf

740 page RF/IF DESIGNER'S HANDBOOK

\* MIXERS • POWER SPLITTER/COMBINERS • AMPLIFIERS • ELECTRONIC ATTENUATORS  
• I/Q/QPSK MODULATORS • ATTENUATORS/TERMINATIONS • DIRECTIONAL COUPLERS  
• RF TRANSFORMERS • DIGITAL ATTENUATORS • PHASE DETECTORS • SWITCHES/DRIVERS  
• FILTERS • LIMITERS • FREQUENCY DOUBLERS

\*values or models may be substituted without notice, depending on supplies

Typical Circuit Arrangement

 

finding new ways ...  
setting higher standards

## Mini-Circuits™

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

Distribution Centers NORTH AMERICA 800-654-7949 • 417-335-5935 Fax 417-335-5945 EUROPE 44-252-835094 Fax 44-252-837010

CIRCLE 186 ON FREE INFORMATION CARD

# EDITORIAL

## IT'S NOW OR NEVER

Now. This moment, this instant—it lives but a microsecond. Then it moves on and changes and becomes something new and different and better.

That's exactly what our magazine—our magazine, yours and mine—is doing. I grew up on *Radio-Craft* and *Radio-Electronics*. You've probably grown up on *Radio-Electronics*. The next generation of electronics professionals may not even remember *Radio-Electronics*, but they will know **Electronics Now**. For this new, yet old, publication will be their introduction to electronics. It will be their primer, their teacher, their guide, their companion. It will travel with them through their career just as *Radio-Electronics* has through yours. As long as there are electronics professionals, as long as there are people who follow the wonderful ever-changing world of electronics, **Electronics Now** will be there.

**Electronics Now** is not a new magazine, it is simply a refinement of what has always been. It's an evolution to something better, something wiser, something stronger. A magazine more closely matched to electronics today. Carefully designed, tailored and directed by selected experts who can point you, our reader, through our pages, toward tomorrow.

**Electronics Now** is *your* magazine. It is the culmination of almost 100 years of progress from the *Electrical Experimenter* to *Radio-Electronics* and finally **Electronics Now**.


If our founder, Hugo Gernsback, were here today, he'd probably note that we should have acted sooner. Perhaps he would have been right. But no matter what, we know we are correct in taking you and us on this new adventure. Join us as we go. Revel in the excitement of today and the adventure of tomorrow. Tell us what you like, what you hate, what we should do, and what we shouldn't.

Write our editors, contact our bulletin board, send me your ideas, comments, and criticisms. Help us make **Electronics Now** exactly the kind of magazine you know it should be. And never forget we may now bear the name **Electronics Now**, but at heart we are *Radio-Electronics*, *Radio Craft*, *Shortwave Craft*, *Television*, and the *Electrical Experimenter*.



Larry Steckler, EHF/CET  
Editor-in-Chief and Publisher

# The DMM our customers designed.

 

Before we built the new generation Beckman Industrial Series 2000 DMMs, we asked people like you what you *really* want.

You want more. More test and measurement capabilities. More troubleshooting features. All in an affordable hand-held DMM. The Series 2000 features the widest range Frequency Counter in any professional DMM, a full-range Capacitance Meter, True RMS measurements, Intermittent Detection, 50ns Pulse Detection, and Peak Measurement capabilities. Plus, the Series 2000 is the only meter to offer autoranging Min/Max recording and relative modes.

You want a DMM that's easier to use. The Series 2000's display is 25% larger, with bigger digits and backlighting for easier reading, even in the worst light. Plus the fast 4 digit display provides the high resolution needed for adjusting power supplies and generators down to 1mV. And only the Series 2000 features a menuing system for fast, simple feature access.



Made in the USA

The Beckman Industrial Series 2000, priced from \$209 to \$279 offers you the best performance for your dollar. Look again at these features:

- 4 Digit, 10,000 Count Resolution
- Basic Accuracy to 0.1%
- True RMS, AC or AC on DC
- 0.01 $\Omega$  Resolution
- Automatic Reading Hold
- 1ms Peak Hold
- Fully Autoranging Relative and Min Max Modes
- Intermittent Detector
- UL1244, IEC1010 Design
- Three Year Warranty

The Series 2000 offers the most solutions for your everyday test and measurement needs. The only DMMs designed by the people who use them. You.

For more information on these new DMMs call (outside CA) 1-800-854-2708 or (inside CA) 1-800-227-9781. Beckman Industrial Corporation, 3883 Ruffin Rd., San Diego, CA 92123-1898.

**BI**<sup>™</sup>

**Beckman Industrial<sup>™</sup>**

An Affiliate of Emerson Electric Co.

Specifications subject to change without notice.  
© 1992 Beckman Industrial Corp.

CIRCLE 98 ON FREE INFORMATION CARD

# WHAT'S NEWS

*A review of the latest happenings in electronics.*

## **Fluke and Philips restructuring**

John Fluke Mfg. Co., Inc. (Everett, WA) and Philips Electronics N.V. (Eindhoven, The Netherlands) on August 26 announced their intention to restructure their five-year-old alliance in the test and measurement business. Under the plan, which is expected to take several months to finalize, Fluke would acquire most of Philips' test and measurement operations for cash and stock. Once the contingency factors have been met (approval by Fluke shareholders and the Philips Board of Management, and review by the appropriate social and regulatory organizations), Fluke would acquire essentially all existing Philips' test and measurement businesses, with the exception of professional TV test equipment and power supplies. Fluke would then assume direct responsibility for worldwide marketing, development, manufacturing, sales, and support of most of the combined companies' present product lines. That includes the acquisition of sales and service operations in Europe. About 900 Philips employees would transfer to Fluke.

The management of both companies see the move as a logical progression in their alliance. According to Bill Parzybok, Fluke Chairman and CEO, "All along, we have been evolving the alliance to optimize our performance and improve our position in a changing marketplace. It has become apparent to both companies that a unified management structure, aligned under a single mission, would accelerate our growth and success." That mission, he said, is to position Fluke as the leader in compact, professional electronic test tools. The single focus is expected make the combined company more effective in product definition, design, and marketing, leading to streamlined production and better time-to-market

for new products. In addition, Fluke hopes its European presence will allow the company to take advantage of EC'92.

The transaction is expected to add about \$125 million to Fluke's revenues, and to favorably impact Fluke's earnings per share beginning in the first year of operations. Fluke expected to issue its proxy statement to shareholders in early November.

## **See-through magnetic material**

Scientists at Xerox Corporation's Webster Research Center (Webster, NY) have produced a transparent magnetic material with potential applications in color imaging, computer information storage, magnetic fluids, and even magnetic refrigeration. (When a magnetic material is moved into a magnetic field it heats up; when moved out, it cools down. That so-called magnetocaloric effect can theoretically be used to build refrigerators. Although magnetic refrigerators have been built, none have worked at anything near room temperature.) The crystalline material is chemically identical to the gamma ferric oxide that has been used for decades to coat audio and video recording tape. But the crystals that make up the physical form of the new material are far smaller than those of conventional magnetic material. The  $Fe_2O_3$  crystals comprising the magnetic material range in size from two to ten nanometers. With such small crystals, the material loses its usual ferromagnetic property and becomes superparamagnetic—a state in which the crystals will stick to a magnet but not to each other.

The transparency is an added bonus that is not generally found in magnetic materials at room temperature. The scientists have not yet determined why the nanocrystals are more transparent than the larger

crystals of conventional  $Fe_2O_3$ . Although some transparent magnetic materials already exist, their magnetic properties are either too weak to be useful, or they function only at temperatures near absolute zero.

## **World's most powerful laser-light beam**

A breakthrough in the international race to create the world's most powerful laser-light beam has been achieved by scientists at The University of Michigan (Ann Arbor, MI) and the French National Atomic Energy Commission. The 55-terawatt beam of laser light—one terawatt is equivalent to one trillion watts—was produced in April 1992 at the Centre d'Etudes de Limeil-Valenton (Limeil, France). The previous record, set last year in Japan, was 30 terawatts. The beam was produced by the Center's P-102 laser with a laser amplification technique and a second preamplifying laser developed by Gerard A. Mourou, professor of electrical engineering and computer science at Michigan, and his co-researchers.

During the brief laser burst, researchers produced the 55-terawatt of power—the equivalent of 100 times the total electrical power generated in the United States. According to Mourou, "The laser beam can be focused over a spot smaller than the diameter of a human hair to produce extremely high power densities." The researchers say that the most immediate application of the new technology will be to determine what happens when extremely intense laser beams interact with matter.

Preliminary experiments showed that when high-powered laser pulses are shot through plasma, shock waves are created that are capable of accelerating electrons close to the speed of light in very small distances. That could lead to

*Continued on page 74*



# Pulse. Function. And Wave.

(Good-bye to imported instruments)

## Ultravariabile Pulse Generator

- 0.5 to 5MHz
- Run, Triggered, Gate, Single-Shot
- Independent width and space controls
- Variable 50Ω output

Model 4001

\$199.95

## Audio/Sweep Generator

- Sine/Square/Triangle
- 1Hz to 100kHz
- Variable DC offset
- Sweepable 100:1

Model 2001

\$178.50

## 2MHz Sweep Function Generator

- 0.2Hz to 2MHz
- Duty-cycle, symmetry controls
- 50Ω output
- VCO input

Model 2002

\$219.95

## Digitally Synthesized Generator

- DC to 1.6MHz
- Trigger, Sweep, Burst, Hop and Gate modes
- Internal/External Sweep
- Sine, Square, Triangle, Ramps
- Optional RS-485 communications port
- 16 programmable memories

Model 2003

\$499.95



Compare the specifications and the prices of these four instruments with the competition. Then compare the labels. Global's say "Proudly Made in U.S.A.". Designed and manufactured in our Connecticut factory with the value and quality that Global is known for. The competitors, they look alike because they are. Different names on the front. The same label on the back. "Made in Taiwan".

With Global you'll get a Good Buy, and can say Good-bye to imports.



**Can't Wait? Call... 1-800-572-1028**

**GLOBAL SPECIALTIES**  
70 Fulton Terrace  
New Haven, CT 06512  
FAX 468-0060

© 1992 Interplex Electronics  
Specifications subject to change without notice.

an Interplex  
Industries  
company

A004

# VIDEO NEWS

What's new in the fast-changing video industry.

DAVID LACHENBRUCH

● **Nintendo goes 32-bit.** Taking its competitors by surprise, Nintendo announced that, unlike other video-game manufacturers, it will skip the current generation of 16-bit games and go directly to a 32-bit processor when it introduces its CD-ROM accessory next year. The company announced that it had developed a proprietary "Super FX" chip that will make possible 16-bit cartridge games with "true 3D effects." Because its next-generation cartridge games will be 16-bit, the company decided that it would need an enhanced CD-ROM to offer customers a "truly superior game experience."

The new CD-ROM drive will function within the CD-ROM/XA environment, Nintendo said, which theoretically would make it compatible with Philips' CD-I.

● **VIS vs. CD-I.** Tandy's Video Interactive System, or VIS, designed to play CD-ROM's through consumer TV sets (**Electronics Now**, November 1992), formally carries a suggested list price of \$699, which includes Compton's *Multimedia Encyclopedia*. Philip's incompatible CD-I system also lists at \$699, after recent price reductions, and dealers have been selling it at \$599. Consumers who bought players at higher prices are being mailed coupons good for \$100 worth of free software. In addition, purchasers returning warranty cards are sent coupons that are good for transfer of their photos to a Photo CD. The CD-I format is compatible with Kodak's Photo CD system (but VIS currently isn't).

● **TV's are growing.** Larger picture sizes continue to grow as a share of the television-receiver market. In the first half of 1992, sales of direct-view sets with tubes 30 inches and larger (diagonally) were up 64% from the same period of 1991. Projection TV sales were up

14%, but the larger sized projectors (50 inches and larger) rose by more than 21%.

● **Who's number one?** Number one in TV set sales, that is. That position is still held by RCA as the leading brand in the United States, with just over 16% of the market. Zenith continues as number two, with a little more than 10%, followed by Magnavox with 9%. Sony is fourth with 7%, and Sharp is fifth with 5½%. The rankings are by *Television Digest*, which has been surveying TV market shares for 26 years. In the first brand rankings for projection TV, Mitsubishi was the clear winner with 22.6% of the market, followed by Magnavox with 4% and RCA with 13%.

● **Digital HDTV works.** The first report on digital high-definition TV by the Advanced Television Test Center (ATTC), which is testing proposed systems for the FCC, offered great encouragement for the future of digital TV transmission. Reporting on the first digital system it tested—General Instrument's DigiCipher—the ATTC's results indicated generally good picture quality with low levels of interference. Contrary to doubts expressed in Europe and Japan, where analog systems are espoused, the tests showed that DigiCipher produces less interference with other broadcasts than the analog NTSC system used in the United States. The tests also appeared to show that the DigiCipher system can provide the same coverage distance from the transmitter as the NTSC system, but at 13-dB lower power. However, digital HDTV does appear to be more sensitive to phase noise, which can probably be overcome by the development of improved filters in TV sets.

● **Priming HDTV's pump.** The fact that HDTV is technically possi-

ble doesn't necessarily mean that it will proceed rapidly once a system is chosen. As a matter of fact, it's difficult to determine how the first HDTV pictures will be delivered—by terrestrial broadcast stations, direct satellite, cable, or even possibly by prerecorded media such as videotape or laserdisc. Although the FCC-sponsored tests are designed to determine the best system for terrestrial HDTV broadcasting, it's entirely possible that broadcasters will take a wait-and-see attitude toward HDTV before going to the tremendous expense of adding new studio and transmission equipment—and quite likely new antenna towers to disseminate two separate types of broadcasts during the interim period of HDTV's introduction while NTSC signals are still being broadcast.

When color TV was introduced, TV station owners were extremely reluctant to add color origination equipment because the lack of audience meant that they couldn't charge advertisers a premium for color broadcasts. And it wasn't until 10 years after the introduction of color TV that consumers bought a million sets in any year. (The figure is now well over 20 million a year.) Broadcasters say they can't be certain that there is any market for HDTV—but they do see a lucrative by-product of the current HDTV tests. All digital HDTV systems rely on data compression to squeeze four times the current information into a single 6-MHz channel. So broadcasters are asking whether it might be more lucrative for them to use compression technology to cram two or more standard-definition broadcasts onto a single channel, and thus help on-air broadcasters attain the multi-channel capacity that will let them compete with cable.

Cable itself is in a better position than broadcasters to provide early

*Continued on page 74*



# Plug a Friend into **Electronics NOW**<sup>®</sup> and Save \$17.43!

*This Christmas give an electrifying gift ... plug a friend into Electronics Now and brighten the whole new year! Whether electronics is your friend's livelihood or hobby, your gift will illuminate the whole spectrum of electronics throughout the coming year and provide a monthly reminder of your friendship.*

Electronics Now will keep your friend informed and up-to-date with new ideas and innovations in all areas of electronics technology ... computers, video, radio, stereo, solid state devices, satellite TV, industrial and medical electronics, communications, robotics, and much, much more.

We'll provide great plans and printed circuit patterns for great electronic projects. In just the last year, Electronics Now has presented amateur TV equipment, computer peripherals, stereo transmitters, test equipment, speakerphones, robots, audio amplifiers, power inverters, and much more.

In coming issues, Electronics Now will present practical, educational, and money-saving projects like: an electronic drum, an audio effects generator, communications equipment, a light-beam communicator, a remote car starter, an uninterruptible power supply, and many others!

PLUS ... equipment troubleshooting techniques ... circuit design ... reports on new technology and new products ... equipment test reports ... in-depth coverage on computers, video, audio, shortwave radio ... and lots more exciting features and articles.

SAVE \$17.43\* ... OR EVEN \$35.83\* ... For each gift of Electronics Now you give this Christmas, you save a full \$17.43\* off the newsstand price. And as a gift donor, you're entitled to start or extend your own subscription at the same Special Holiday Gift Rate — you save an additional \$17.43\*!

No need to send money ... if you prefer, we'll hold the bill till January, 1993. But you must rush the attached Gift Certificate to us to allow time to process your order and send a handsome gift announcement card, signed with your name, in time for Christmas.

So do it now ... take just a moment to fill in the names of a friend or two and mail the Gift Certificate to us in its attached, postage-paid reply envelope. That's all it takes to plug your friends into a whole year of exciting projects and new ideas in Electronics Now!

See page 100A  
for envelope.

\*Basic sub rate — 1 yr/\$19.97 2 yrs/\$38.97



Write to Q & A, Electronics Now, 500-B Bi-County Blvd., Farmingdale, NY 11735

#### 50-OHM TERMINATION

I recently bought a card for my PC that lets me control things like motors and relays. My problem is that the instructions tell me that each line to the relay or motor must be terminated with at least 50 ohms. I'm not exactly sure what that means, and I was hoping you could explain it to me.—G. Cherben, Nighten, IN

I'm not exactly sure what kind of hardware you bought for your PC, but no matter what it is, yours is the kind of question I like—nice and easy.

All the instructions are telling you is that each of the card's outputs want to see a load of 50 ohms. That kind of termination is standard for computer networks and other things. If you're having a hard time understanding why it's needed, think for a minute of the power-amplifier outputs on a stereo. It's never a good idea to leave them unconnected to anything because an infinite load like that (that's what an open connection is) can put an unnecessary strain on the stereo's output transistors.

The same is evidently true for your controller card. Just as it doesn't want to see a direct short on the control lines, it doesn't want to see too high a resistance either.

I'm a bit surprised that an external termination is required since it would have been easy for the card's designers to include it on the card itself. Most motors and relays have fairly low winding resistances, so the addition of a 50-ohm resistor is pretty silly—kind of like putting a 10-amp fuse on a line that will draw a maximum of only 1 amp. Remember that adding a 50-ohm resistor in parallel to a motor winding with a resistance of 3 ohms or so isn't going to add much to the equivalent total resistance of the pair.

You can buy 50-ohm terminators or just solder a 50-ohm resistor on

the line. By the way, for all intents and purposes, a 47-ohm resistor is close enough.

 


FIG. 1—CRYSTAL OSCILLATOR. If you use an inverting hex buffer like the 4049, powered from a 5-volt supply, the circuit will work with crystals as high as 14 MHz.

#### CRYSTAL OSCILLATOR

I'm building a circuit that requires a crystal oscillator, but I'm not sure which design to use. I don't have to worry about any extreme temperatures, and I have a bunch of spare gates left over on the board. Most of the crystal oscillator designs I've seen require the addition of special chips, and I don't have a lot of room left on the board. Have you got a simple circuit that will

do the job?—J. Gillan, Hendon, NH

If your requirements are as simple and straightforward as you say, the circuit in Fig. 1 is exactly what you need. It can be made from the extra gates you have, is self-starting, and is also extremely reliable.

The circuit will work well with as little as a 5-volt supply, and the crystal frequency limit really depends on the amount of gain there is in the gate you use. Something like a 4049 will work with crystals as high as 14 MHz. If you use more than 5 volts for the supply, you should be able to go even higher.

One interesting variation on this circuit is to use a two-legged gate instead of a simple inverter. That will let you turn the design into a gated oscillator so you can turn it on and off under circuit control. I don't know if that's important in your application, but it's a good thing to keep in the back of your mind.

#### SCAN RATES

I know this information has probably been printed somewhere before, but could you tell me what the scan rates are for the various kinds of IBM video? I have several monitors available, and I'm not sure which ones can be used with which graphics cards.—S. Heller, New York NY

The variety of IBM video standards has always caused confusion.

IBM VIDEO STANDARDS

VIDEO TYPE	ACRONYM	COLOR	SCAN RATE
MONOCHROME DISPLAY ADAPTER	MDA	B&W	18432 kHz
HERCULES GRAPHICS ADAPTER	HGA	B&W	18432 kHz
COLOR GRAPHICS ADAPTER	CGA	8	15750 kHz
ENHANCED GRAPHICS ADAPTER	EGA	16	21800 kHz
PROF. GRAPHICS ADAPTER	PGA	256	30480 kHz
VIDEO GRAPHICS ARRAY	VGA	256	31500 kHz

It's usually a problem when people want to upgrade their video. In any event, the IBM standards are listed in Table 1. Notice that it doesn't include any of the super VGA frequencies. The reason for that is simply because super VGA frequencies can be anywhere from the regular VGA standard to as high as 50 kHz with a 70-Hz vertical refresh rate. That usually shows up when you get into super VGA with interlaced or non-interlaced video.

#### QIC AND EASY

**I have a QIC-40 tape backup in my computer, and I have just increased the size of my hard drive to 120 megabytes. I know I can back up the drive on several different tapes, but it's a pain in the neck to tag a bunch of files, back them up, then tag another bunch, back them up, and so on. Is there an easier way or will I have to buy a tape drive with a larger capacity?—D. Tunn, Tenafly, NJ**

I can't accept the idea that having to use a couple of tapes to back up your new, larger, drive is such a chore. You've obviously forgotten what it was like to back stuff up on floppies. But there are several alternatives you can try.

The first, and most obvious, is that the software that drives the tape usually gives you a way to build a tag list and, by specifying that you want to back up everything in the listed directories, you should be able to avoid having to tag the files individually.

Most tape software also allows you to compress the files on the tape so you can effectively turn a 40-megabyte tape into a larger one. The number of extra files you can get on the tape depends on what kind of files you have to back up, and how effective the software's compression algorithm is. Text and other data files will squeeze down by at least 70%. That is only an estimate, but you should be able to get a substantial savings by compressing the files as you back them up.

If the software that came with your tape drive doesn't have any of those features, there are other programs that will provide them. QIC-40 is a standard that allows a

tape recorded on any QIC-40 drive to be read on any other QIC-40 drive.

Another alternative to shelling out bucks for a new tape drive is to use a DC 2120 cartridge rather than the standard DC 2000 that you're probably using now. Those cartridges are compatible with your drive and, because thinner Mylar is used for the tape itself, you can format it to about 60 megabytes. When you add data compression, you should be able to get over 100 megabytes on the tape.

If you are interested in buying a new tape drive, QIC-80 tape drives double the storage capacity of QIC-40 drives by packing twice as much data on the same tape. A QIC-80 drive formats a DC 2120 tape to 120 megabytes, and roughly doubles that to about 250 megabytes using software compression. A new drive won't even set you back by much—QIC-80 drives, such as the Colorado Memory Systems' Jumbo 250, sell for as little as \$250, mail order.

#### LESS THAN MTS

**I have an RCA stereo TV that I'm happy with for the most part. It's just that, on occasion, a stereo broadcast will sound like it's coming out of a seashell. I'd love to blame the cable company—and I usually can—but my VCR doesn't suffer the same problem. Friends have told me that the problem is because my TV isn't a true MTS-compatible set. Is this true?—M. Johnson, Lindenhurst, NY**

Many people have complained about problems similar to yours—including the folks over at dbx, whose noise-reduction circuitry *must* be incorporated into any stereo TV circuitry in order for it to be called MTS. Lots of manufacturers insist that they can meet the MTS specifications without using dbx, but that's usually done to avoid paying licensing fees to dbx. I suspect that your RCA TV does not have dbx, while your VCR does. If the noise really bothers you, and you're not ready to buy a new TV—with dbx noise reduction—then just use your VCR as the tuner for as long as you have to. **R-E**

## Earn Your B.S. Degree in ELECTRONICS or COMPUTERS



### By Studying at Home

Grantham College of Engineering, now in our 42nd year, is highly experienced in "distance education"—teaching by correspondence—through printed materials, computer materials, fax, and phone.

No commuting to class. Study at your own pace, while continuing on your present job. Learn from easy-to-understand but complete and thorough lesson materials, with additional help from our instructors.

Our Computer B.S. Degree Program includes courses in BASIC, PASCAL and C languages — as well as Assembly Language, MS DOS, CADD, Robotics, and much more.

Our Electronics B.S. Degree Program includes courses in Solid-State Circuit Analysis and Design, Control Systems, Analog/Digital Communications, Microwave Engr, and much more.

An important part of being prepared to *move up* is holding the right college degree, and the absolutely necessary part is knowing your field. Grantham can help you both ways—to learn more and to earn your degree in the process.

Write or phone for our free catalog. Toll free, 1-800-955-2527, or see mailing address below.

•  
Accredited by  
the Accrediting Commission of the  
National Home Study Council

•  
**GRANTHAM**  
**College of Engineering**  
Grantham College Road  
Slidell, LA 70460

# LETTERS

Write to Letters, *Electronics Now*, 500-B Bi-County Blvd., Farmingdale, NY 11735


## DISTORTIONLESS POCKET STEREO AMP

I have some information regarding the "Pocket Stereo Amp" (*Ask R-E, Electronics Now*, August 1992) that might be helpful to the person who was having distortion problems when using an LM386. I've experimented extensively with that IC, and while simplicity has its merits, we must remember that a job worth doing is worth doing well. Because pocket stereos often have excellent sound quality, steps should be taken to maintain that quality when building an add-on amplifier for it.

The bare-bones design shown in Fig. 2 of the article might work, but

the inclusion of a few junk-box components will yield better results. I've been using the design shown to the right, which is the one that generally shows up in projects that incorporate an audio section. Though the values sometimes differ slightly, all of these components usually appear in the circuit.

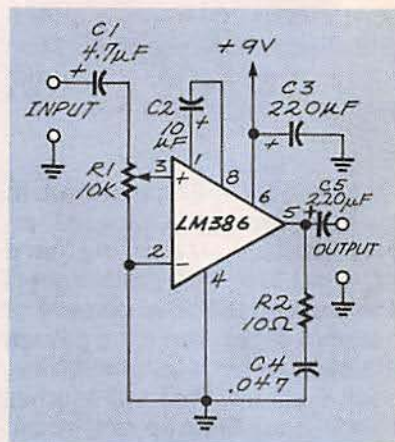The first time I built this amplifier, I omitted capacitor C3 thinking that it would be unnecessary with a battery supply that contains no ripple. That resulted in severe distortion even at low input signal levels. The amplifier even tended to oscillate at times. After some head scratching, I connected a large-value electrolytic capacitor between pin 6



(supply) and ground, which eliminated the problem completely.

The amplifier can be driven with a line-level signal from an auxiliary output or from the headphone jack of a pocket stereo. In the latter case, with R1 adjusted for maximum volume level, the pocket stereo's volume control should be adjusted to the minimum level that will provide adequate sound. That will prevent the possibility of overdriving any LM386's. Once that is done, R1 can be used to adjust the volume.

If two such amplifiers are being used for stereo, C3 can be connected between the common supply line and ground. If you use a power supply that contains a filter capacitor, C3 might not be necessary. C2 is optional as stated in the original article, depending on the need for gain. I recommend using it because even though the amplifier in the pocket stereo provides gain, most of that gain will be lost when the controls are adjusted to limit the level of the input signal.

Capacitor C1 can be omitted if there is no DC component on the input signal line. There probably is none if the source is an earphone jack or auxiliary output of a CD player or cassette player. I have occasionally seen pin 7 (bypass) connected to ground through a capacitor, but it doesn't seem to make

# SIMPLE

The RMS225 was built around simplicity. Instead of a barrage of buttons to push, you simply scroll through a menu of special functions. Minimums,



maximums and automatic reading hold are simple functions with Beckman Industrial's RMS225. It's simply the best meter for the money.

**BI**

any noticeable difference in this application, so I've never used it.

The design shown in Fig. 1 gives a surprisingly good sound considering the low cost of the IC.

As always, I'm grateful for the *Letters* column in **Electronics Now** that allows the exchange of information among readers.

STEVE BABBERT  
Worthington, OH

#### THEFT OF SERVICES

I fail to understand you guys. Is **Electronics Now** a socialist magazine, advocating ripping off cable companies because they are Robber Baron Capitalist Fat Cats, or something? Robert Grossblatt says, "If the cable companies put the signal on your wire, you should have the right to use it." Does he steal from coin newspaper boxes too? After all, his quarter has purchased him access to the box, right? Hasn't he ever heard of "implicit contracts?"

When he took his cable service, he agreed to take the services he paid for. I agree that he should have the right to experiment. But if he steals programming, he isn't just stealing from the Fat Cat Cable Company—he steals from a lot of other people: technicians who work for the cable company, artists who do the programming, electronics manufacturers who supply products to the cable companies, and ultimately from little electronics companies like mine. We design and repair cable, and that work keeps a technician and an engineer employed. That's how I see it. And I think that the law agrees with me.

P. MIHOK  
Don Mills, Ontario, Canada

#### TURN-SIGNAL FLASHER UPDATE

The circuit suggested by Timothy Brooks in September's *Letters* column, designed to augment the too-faint click of the automobile turn-signal flashers (a 47- $\mu$ F capacitor in series with a small speaker connected across the flasher unit) works fine. However, there must be a current-limiting resistor in the circuit. Without it, the speaker's voice coil soon opens up.

F.G. HUTCHINSON  
Redwood City, CA

#### ANOTHER FLASHER UPDATE

The letters in the September issue of **Electronics Now**, suggested different complicated electronic solutions for amplifying an automobile's turn-signal sound. There is a much simpler solution to the weak turn-signal sound problem; I have been using it for a number of years. Many automotive departments of retail stores stock replacement flashers. Look for an Ideal Loud Turn-Signal Flasher No. 577V (Ideal Division, St. Augustine, FL 32084).

It can replace any 12-volt, two-terminal flasher. Only one problem might be encountered: The loud-flasher's case is slightly more than twice as long as a regular flasher's case. That becomes a problem only if there is a lid covering the terminal box containing the flasher. In that case, you can cut a hole in the lid to accommodate the new flasher, or leave the lid off entirely.

VINCENT M. SARITI  
Dover, NJ

#### DISKETTE CONVERSION

In the Q&A column in the September issue of **Electronics Now**, there was a discussion of double- and high-density diskettes, and whether or not there really is a difference between them I have converted 3.5-inch "floppy" disks from double-density to high-density by forming a hole in their cases, and I have found that the converted disks work fine without problems. However, *be very careful not to let any small material chips get inside the disk case.*

When a hole is made in the proper place, a small opening into the disk case is created. If a chip from the drilling or punching gets into that hole, it could cause serious damage to the disk—or, even worse, to the disk drive. I consider drilling the hole to be out of the question, and recommend using a very sharp and sturdy punch. Several of these are now on the market.

EMERSON M. HOYT  
Beaverton, OR

R-E

# TRUTH

If your meter doesn't have True RMS, it's lying to you. Those nasty nonsinusoidal and noisy sinusoidal wave forms fool even the best "averaging" meters. The problem was, True RMS used to be expensive. Good news. The RMS225 is half the price of similar meters.

Call (800) 854-2708, (800) 227-9781 in CA.

**Beckman Industrial**

An Affiliate of Emerson Electric Co.  
Beckman Industrial Corporation, San Diego, CA 92123-1898.



CIRCLE 190 ON FREE INFORMATION CARD


# EQUIPMENT REPORTS

## Beckman Industrial HD160 Digital Multimeter

**M**any people who use digital multimeters—even those who use one every day—consider DMM's to be little more than commodity items. Other people, especially those whose livelihoods depends on the DMM, know the importance of a well designed meter. They'll want to know about a new DMM from Beckman Industrial Corporation (Instrumentation Products Division, 3883 Ruffin Road, San Diego, CA 92123-1898): the *HD160* heavy duty digital multimeter.

The *HD160* is the latest entry in Beckman Industrial's "HD" line of heavy-duty DMM's. It is housed in a sleek, bright yellow case that measures about 6.8×2.8×1.3 inches. A black rubber holster is supplied with the DMM to provide extra protection. Although the holster adds significant bulk to the meter, it can actually make handheld operation easier, thanks to two probe holders on the holster. The user can hold the meter with one attached probe in one hand, and the remaining probe in the other. The probe holders also provide a secure, safe place to store the probes when the meter is not in use.

The holster also provides a tilt stand that is particularly convenient for bench-top use; a tilt bale provides fixed tilt angles of 20 or 60 degrees from perpendicular. We would expect the *HD160* to be used away from the benchtop as often as not. If you've ever used a DMM while at the top of a ladder or while perched on the service platform of a large industrial machine, you've undoubtedly found that three hands could come in very handy. The *HD160* offers what might be the next best thing: a "Flex-Strap." The Flex-Strap is a Velcro-covered fabric strap that lets you hang the meter vertically from a wide variety of pipes, beams, and the like. Pipes up to about three inches in diameter will serve just fine.

 

*A meter for heavy-duty professionals*

CIRCLE 10 ON FREE INFORMATION CARD

The face of the meter is agreeably uncluttered. A large, 7-position rotary control sets the main function selections: AC volts, DC volts, resistance, diode test/continuity, DC current, and AC current. Below the rotary control are four input jacks: a common, one for voltage and resistance measurements one for current measurements of 40 milliamps or less, and one for current measurements up to 20 amps.

At the top of the meter's face, below the 4-digit (10,000-count) LCD readout, are three round push-buttons: MENU, SELECT, and CLEAR. The sensible menu system is what helps keep the meter face so uncluttered. When the meter is first powered up, it is in its autoranging mode. To change the range, you would press the menu key; a four-item menu (RANGE, HOLD, REL, and MIN MAX) flashes above the digits. With the first press, the menu cursor is on the range selection. Successive

pushes of the SELECT button changes the range. Successive pushes of the MENU button changes the cursor position. The CLEAR button can clear a given entry, or it can clear the entire menu, resetting the meter. We found the menu system to be intuitive.

The meter's hold mode, which Beckman Industrial calls "Probe Hold," automatically freezes the meter's display when a stable reading is reached. That means the meter user can keep his hands on the probes, not on the meter—an important feature if you work around dangerous voltages.

The relative mode lets the meter measure values with respect to a reference other than zero. The feature works in the voltage, resistance, current, and diode-test modes.

The max min mode lets the meter measure and record the minimum and maximum values of input signals. The feature works with all functions except diode test. The mode is not useful for capturing transients, but it can be used to measure the operating parameters of a circuit. The automatic power-down feature does not, fortunately, operate in max min mode.

An analog bar graph, made up of forty LCD segments, is useful for peaking circuits; they respond faster than the digital display (20 updates a second as opposed to 2 updates a second), and—as with an analog moving-coil meter—small changes are more obvious.


The *HD160* offers true-rms measurement capability depending on the input signal's crest factor. The crest factor is the ratio of a signal's peak voltage to its rms value. A sine wave has a crest factor of 1.414, a full-wave rectified sine wave has a crest factor of 3.247. Signals with crest factors up to 5.0 can be measured when the display is at or below 2500 counts. At half scale

*Continued on page 96*


 
# ELIMINATES SEARCHING, SCANNING, TUNING **INTERCEPTOR™**

**INTERCEPT, DETECT & CAPTURE  
Near Field Transmissions with  
Optoelectronics' New  
INTERCEPTOR™**



MADE IN THE U.S.A.

## NEW TECHNOLOGY

- Follows & Locks on even when frequency changes.
- Intercepts ALL FM Two-Way Transmissions without gaps in coverage.
- Does Not have to tune through RF Spectrum to find signals.

## FCC Classified as Communication Test Instrument for:

- Deviation, FM, FMN
- Relative Signal Strength
- Signaling Tones (CTCSS)
- Modulation Monitor
- Great for testing VHF, UHF & Cellular transmitters

## A New Dimension in Recreational Monitoring - Intercept the Two-Way Communication that Surrounds You.

Increase Your RF Security.



## Hand Held/Shirt Pocket Size

**INTRODUCTORY OFFER**  
Interceptor™ R10 FM Communications Interceptor (Includes NiCads, AC/Charger Adapter, Antenna, Earphone) .....\$359.

### OPTIONS

Headphones (Lightweight personal headphones).....	\$ 15.
Antenna Pak 2 (Five assorted rubber duck antennas - save \$32.).....	\$ 99.
TC200 Tone Counter (CTCSS signalling tones).....	\$ 179.
APS-104 (Extends RF detection distance 10x).....	\$ 995.
CF800 Cellular Band Pass Filter/Amplifier.....	\$ 299.

# OPTOELECTRONICS

FACTORY DIRECT ORDER LINE **1-800-327-5912**

305-771-2050 • FAX 305-771-2052 • 5821 NE 14th Ave., Ft. Lauderdale, FL 33334  
5% Ship/Handling (Max\$10.) U.S. & Canada. 15% outside continental U.S. Visa & Master Card accepted

CIRCLE 182 ON FREE INFORMATION CARD

# No other training to troubleshoot computers

Only NRI walks you through the step-by-step assembly of a powerful 386sx computer system you train with and keep—giving you the hands-on experience you need to work with, troubleshoot, and service today's most widely used computer systems. Only NRI gives you everything you need to start a money-making career, even a business of your own, in computer service.

No doubt about it: The best way to learn to service computers is to actually build a state-of-the-art computer from the keyboard on up. Only NRI, the leader in career-building at-home electronics training for more than 75 years, gives you that kind of practical, real-world computer servicing experience.

Indeed, no other training—in school, on the job, *anywhere*—shows you how to troubleshoot and service computers like NRI.

**Get inside the West Coast 386sx computer system... and experience all the power and speed of today's computer technology!**

With NRI's exclusive hands-on training, you actually build and keep the powerful new West Coast 386sx/20 MHz mini tower computer system.

You start by assembling and testing your computer's 101-key "intelligent" keyboard, move on to test the circuitry of the main logic board, install the power supply and 1.2 meg high-density floppy disk drive, then interface your high-resolution monitor.

What's more, you now go on to install and test a powerful 40 meg IDE hard disk drive—today's most-wanted computer peripheral—included in your course to

**NEW!**  
**386sx/20 MHz  
Mini Tower  
Computer!**

#### DIAGNOSTIC HARDWARE AND SOFTWARE

R.A.C.E.R. plug-in diagnostic card and QuickTech menu-driven software, both from Ultra-X, give you hands-on experience with today's professional diagnostic tools

#### MONITOR

High-resolution, nonglare, 14" TTL monochrome monitor with tilt and swivel base

#### DIGITAL LOGIC PROBE

Simplifies analyzing digital circuit operation

#### DIGITAL MULTIMETER

Professional test instrument for quick and easy measurements

#### SOFTWARE

Train with MS-DOS, GW-BASIC, and popular Microsoft Works applications software

#### DISCOVERY LAB

Complete breadboarding system lets you design and modify circuits, diagnose and repair faults

#### LESSONS

Clear, illustrated texts build your understanding of computers step by step



dramatically increase your computer's data storage capacity while giving you lightning-quick data access. But that's not all!

**Professional diagnostic hardware and software makes troubleshooting fast and accurate**

Your NRI training now includes a remarkable diagnostic package that allows you to quickly locate and correct defects in IBM XT, AT 80286/80386, and

# shows you how and service like NRI!

**NEW! 40 MEG HARD  
DISK DRIVE!**  
You install this 40 meg IDE  
hard disk drive internally, for  
greater data storage capacity  
and data access speed

**NEW! 386sx/20 MHz  
MINI TOWER COMPUTER!**  
Features 32-bit 80386sx CPU, 1  
meg RAM, 64K ROM, 1.2 meg  
high-density floppy disk drive



NRI gives you the confidence and the know-how to step into a full-time, money-making career as an industry technician, even start a computer service business of your own!

## No experience necessary... NRI builds it in

With NRI, you learn at your own pace in your own home. No classroom pressures, no night school, no need to quit your present job until you're ready to make your move. And all throughout your training, you have the full support of your personal NRI instructor and the NRI technical staff, always ready to answer your questions and give you help whenever you need it.

## FREE catalog tells more. Send today!

Send today for NRI's big, free catalog that describes every aspect of NRI's innovative computer training, as well as hands-on training in TV/video/audio servicing, telecommunications, industrial electronics, and other high-growth, high-tech career fields.

If the coupon is missing, write to NRI School of Electronics, McGraw-Hill Continuing Education Center, 4401 Connecticut Avenue, NW, Washington, DC 20008.

IBM is a registered trademark of International Business Machines Corp.  
QuickTech and R.A.C.E.R. are registered trademarks of Ultra-X, Inc.  
West Coast is a member of the Syntax Group.

compatible computers.

You'll use your Ultra-X QuickTech diagnostic software to test the system RAM and such peripheral adapters as parallel printer ports, serial communications ports, video adapters, and floppy and hard disk drives. You'll go on to use your R.A.C.E.R. diagnostic card, also from Ultra-X, to identify individual defective RAM chips, locate interfacing problems, and pinpoint defective support chips.

This ingenious diagnostic package is just one more way

## **NRI** School of Electronics

McGraw-Hill Continuing Education Center  
4401 Connecticut Avenue, NW  
Washington, DC 20008



For career courses approved  
under GI Bill  
 check for details

- Check one **FREE** catalog only
- MICROCOMPUTER SERVICING
  - TV/Video/Audio Servicing
  - Industrial Electronics & Robotics
  - Telecommunications
  - Basic Electronics

- Computer Programming
- Security Electronics
- Electronic Music Technology
- Desktop Publishing
- Programming in C++ with Windows

Name \_\_\_\_\_ (Please print) \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City/State/Zip \_\_\_\_\_ Accredited Member, National Home Study Council 0003-1292

## NEW PRODUCTS

Use the Free Information Card for more details on these products.

### PROGRAMMABLE PC-BOARD TESTER.

You can test more than 600 TTL and CMOS digital IC's with as many as 28 pins with a new *Model 560A B+K-Precision* tester. Said to be able to perform in- and out-of-circuit tests, it was designed for both speed and accuracy.

The tester's vacuum fluorescent display and front-panel LED's prompt the user through the test procedures for a device, and clearly indicate test results and the IC pins where failure has occurred. The "loop test" continuously checks the device under test until a failure is encountered. This technique detects intermittent failures before the components are assembled in a product.

A memory stores responses from a known to be good PC-board for in-circuit testing.

Responses are permanently stored in one of two internal EEPROM's or any of the four EEPROM's located behind the instru-



CIRCLE 16 ON FREE INFORMATION CARD

ment's front-panel access door. In out-of-circuit testing, the device to be tested is inserted into the zero-insertion-force socket on the instrument, and a button is pressed so a display shows either a "pass" or "fail" and the pin numbers that have been identified as faulty.

The *Model 560A* includes a device data library that contains data on more than 90% of existing 14- to 28-pin IC's. That library will be updated free of charge as new IC's are introduced. Optional *AK-560A* custom programming software,

which does require a processing by a personal computer, allows users to organize tests for non-standard and custom TTL and CMOS IC's.

The *Model 560A* is sold complete with an instruction manual, condensed instructions, IC library list, power cord, in-circuit IC test clips and cables, EEPROM for board-test routines, ground cable, and a spare fuse. It has a price of \$3500.—**B+K-Precision**, 6470 est Cortland Street, Chicago, IL 60635; Phone: 312-889-1448.

### RADAR-DETECTOR TESTER.

When you are out driving, do you worry that your radar detector might not be working correctly—and you could get caught in a speed trap?

*Dynaspek* eases your worries with its *Leash*, just what you need to be sure that your radar detector (and those of your friends and neighbors) are up to snuff. A handheld radar transmitter, it simulates the



CIRCLE 17 ON FREE INFORMATION CARD

feared signal of an X-band police radar gun. Used to test detectors, the unit activates when a button is pressed. A single red LED

indicates that it's transmitting. A full signal intensity reading will appear on your police radar detector if it is functioning properly. The "Leash" has an effective range for test purposes of up to a mile.

The size of an audio cassette tape, (4.5 x 2.75 x 1 inch), *The Leash* transmits at least 12 milliwatts of power at 10.525 GHz. The manufacturer specifies an 8 dB antenna gain and a 36

x 72 antenna beamwidth. A 9-volt alkaline battery will keep it on the air for about six hours of continuous use, and will power it for several months of intermittent use.

*The Leash* has a list price of \$99.—**Dynaspek**, Box 564, Westmont, IL 60559; Phone: 708-325-7450.

### CABLE SCANNER LAN TESTER.

It is now possible to eliminate local-area network faults and decrease network downtime when malfunctions occur with the *Cable Scanner* LAN tester from *Contact East*. The tester works with Ethernet, ARCnet, StarLAN, Token Ring, Twisted-Pair and other networks.



CIRCLE 18 ON FREE INFORMATION CARD

A stand-alone tester, *Cable Scanner* permits system analysis to determine if the fault is within the cabling. It then assists in pinpointing the location of the faults or breaks. The scanner provides measurements of cable resistance and noise level, and gives audible continuity checks. It can accommodate a line printer to log activity.

After the fault has been located with *CE's Cable Scanner*, an internal "Tracer" circuit indicates

exactly where the cable is located in the wall or above the ceiling. It picks up signals introduced into the cable by the scanner. The *Cable Scanner* can also be coupled to a personal computer or oscilloscope for system analysis while the LAN is operating. The complete *Cable Scanner* system includes the Tracer, three adapters (Ethernet, ARCnet, and twisted-pair), printer cable, a PC program disk, printer test connector, six AA nickel-cadmium rechargeable batteries, and an operator's manual. The tester is in a case measuring 1 x 4 x 7.5 inches and weighs 2 pounds.

The LAN *Cable Scanner* is priced at \$1495.—**Contact East**, 335 Willow Street South, North Andover, MA 01845; Phone: 508-682-9844.

**SOLDER PASTE EVALUATION KIT.** Solder cream, powdered solder mixed with flux, has many advantages over conventional flux-core wire solder or preforms in electronics manufacturing. The cream can be applied more precisely to the parts to be soldered, less solder is needed, there is better control of metal deposition, and the wetting of metals to be bonded is more uniform.




CIRCLE 19 ON FREE INFORMATION CARD

ESP is offering its *Kit-5*, containing five pre-packaged containers of ESP solder cream, molded dispensing tips, and a reusable hand dispenser for

precise solder application to help you evaluate its product. The kit includes two tubes each of 60% tin, 40% lead solder paste alloy and lead-free 96% tin and 4% silver solder. Each 35-gram tube is supplied with both an activated rosin flux and a water-washable flux. Also included in the kit is a prepackaged tube of ESP's activated rosin paste flux for evaluating its desoldering effectiveness.

The *Kit-5* evaluation kit is priced at \$89.—**ESP Solder Plus**, 14 Blackstone Valley Place, Lincoln, RI 02865-1145; Phone: 1-800-338-4353; Fax: 401-333-4954.

 **DIAGNOSTIC CARD.** A faulty power supply can introduce errors into a computer. The *Power Good* from *Sibex* is said to be the first diagnostic card dedicated to the test of PC power



CIRCLE 20 ON FREE INFORMATION CARD

supplies. It is intended to assure the user that quality power at the specified voltage is being drawn by the computer.

The user plugs the card

## Electronics Workbench® The electronics lab in a computer™

**Powerful software to build and simulate analog and digital circuits.**

Building and testing circuits is fast and easy with *Electronics Workbench*. Just click-and-drag with a mouse to add parts, run wires, and adjust instruments. The traces on the simulated instruments are the same as you'd get on real equipment.

*Electronics Workbench* really is an electronics lab in a computer. It's ideal for learning about electronics, experimenting, and prototyping circuits.

"*Electronics Workbench* is pretty amazing." — Jerry Pournelle, Ph.D., *InfoWorld*

DOS Professional Version — \$299  
Macintosh Version — \$199

*Electronics Workbench* includes:


- **Analog Module** with passive and active components including transistors, diodes, and op-amps; a function generator, an oscilloscope, a multimeter, and a Bode plotter.
- **Digital Module** with gates, flip-flops, adders, a word generator, a logic analyzer, and a unique logic converter and simplifier.

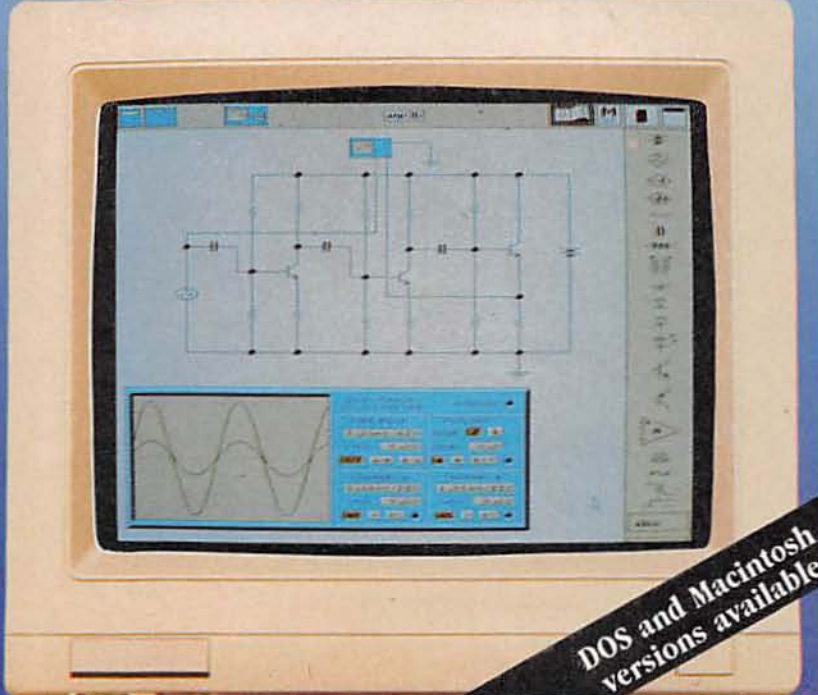**(416) 361-0333**

**Interactive Image Technologies Ltd.**  
908 Niagara Falls Boulevard  
North Tonawanda, NY  
14120-2060  
Fax (416) 368-5799



Prices are in US dollars. Offer valid in the USA and Canada only. Macintosh Version is monochrome only. All trademarks are the property of their respective owners.



**DOS and Macintosh versions available**

CIRCLE 188 ON FREE INFORMATION CARD

Rest assured, no scope was injured in the making of this ad.

After all, the volunteer is a member of our new TAS 400 family of analog oscilloscopes. And every TAS has its entire acquisition system (including the vertical, horizontal and trigger functions for each input channel) housed on a proprietary hybrid circuit.



The result is a kind of scope on a chip.

One with 75% fewer parts and far greater reliability. In fact, the TAS is three times more reliable than previous scopes.

What's more,  
each and every  
TAS

**To demonstrate the value and durability of this amazing**

comes with smashing features like AutoSet, on-screen cursors and readout, dual timebases, and save and recall settings. Plus a unique user interface that makes the 60 MHz TAS 455 and 100 MHz TAS 465 easier to use and dramatically unlike any other analog scope.

A claim that is further backed up by their remarkably affordable price.

But then a lot of performance for not a lot of money is exactly what the TAS is all about.

Scopes that add to a long list of low-cost Tektronix products. Like our handheld 60 MHz 224



digitizing oscilloscope.



Our fully programmable,

analog/digital 2212 scope. And our family of affordable and



stackable basic test gear.

Now that's a lot to

drop on you in one ad. So to learn more

about these and other economical

Tektronix products, call your


authorized Tektronix distributor today.

Or call us at (800) 426-2200, ext. 140

to place your order or for the

name of the distributor

nearest you.

 

**new analog scope, we dropped it.**

**Tektronix**

Test and Measurement

## Clean Without CFCs or 1,1,1-Trichloroethane With New HCFC Blend

Tech Spray has developed a fast-acting and highly effective cleaner called Envi-Ro-Tech™ 1677 (1677) that uses a formulation of HCFCs and other non-CFC chemicals.

This extremely pure product is non-corrosive, making it safe for use on most electronic equipment. Envi-Ro-Tech 1677 is effective in removing oils, greases, dirt, silicone, fluxes and similar soils.

Although Envi-Ro-Tech 1677 has universal cleaning power, its low surface tension makes it ideal for precision and microscopic cleaning.

For a sample of this, or any Tech Spray cleaner, defluxer, duster or freeze spray, contact our Technical Assistance Department toll free at 1-800-858-4043.



Envi-Ro-Tech™ 1677 (1677)



**TECH SPRAY, Inc.**  
P.O. Box 949  
Amarillo, TX 79105-0949  
(806) 372-8523

©1992 TS

CIRCLE 178 ON FREE INFORMATION CARD



\$429

## AN ECONOMICAL KEYBOARD-CONTROLLED KEPCO BENCH POWER SUPPLY 75 WATTS

Choose from four Digital Power Supplies: 0-12.5V @ 6A, 0-24V @ 3A, 0-40V @ 2A or 0-125V @ 0.5A. Each one offers precise, repeatable voltage control with two current ranges. Fully protected for overvoltage or overcurrent.

**Bonus:** You can program the output from your PC's serial port (RS232 software included) and read back too!

The DPS is an affordable professional instrument and belongs on your bench.

Want more info? Ask for "DPS" brochure, 146-1768. Call-write-fax: Dept. MXS-87. Kepco Inc. 131-38 Sanford Avenue, Flushing, NY 11352 USA • Tel: (718) 461-7000 • Fax: (718) 767-1102. Use your VISA or MASTERCARD. Immediate delivery, 5-year warranty.



CIRCLE 180 ON FREE INFORMATION CARD

into an expansion slot on his PC and observes the included LED lamps. Green LED's indicate a good power supply. Red or yellow LED's indicate problems. The unit tests each of the four voltages for high- or low-voltage conditions and the presence of ripple or noise. A built-in latch detects spikes and transients. A connector on the card allows the user to test power supplies before they are installed in the user's computer.

The *Power Good* card is priced at \$139.95.—**Sibex Inc.**, 1040 Harbor Lake Drive, Safety Harbor, FL 34695; Phone: 813-726-4343; Fax: 813-726-4434.

**FM COMMUNICATIONS RECEIVER.** A small handheld FM radio receiver is now available for security, communications, and recreational monitoring. The Model R10 FM Communications Interceptor from *Optoelectronics* is classified by the FCC as a communications test instrument. It can measure deviation (wide and narrow band), relative signal strength, signaling tones (CTCSS), and other demodulated FM. The receiver can also test VHF, UHF, and cellular radio transmitters.

According to its manufacturer, Model R10, unlike conventional radio receivers or scanners, receives any strong signal present, and is actually stabilized by the received signal. The company says the Model R10 does not have to be tuned to a specific frequency to receive a signal. Any FM signal from 30 MHz to 2 GHz can be intercepted without any gaps in coverage.

The *Interceptor* works best in the near-field, the



CIRCLE 21 ON FREE INFORMATION CARD

region surrounding a transmitter where signal strength is high but falls off rapidly with increasing distance. The receiving range varies, depending on the presence of strong signals in adjacent bands. But distances of 200 to 400 feet from a 5-watt UHF or VHF transmitter are typical for Model R10.

The unit is completely automatic for hands-free operation, and is small enough to be carried in a shirt pocket. For test applications, demodulated audio output is available from a stereo phone jack. The R10 also has a built-in speaker.

A lock-release pushbutton frees the unit to lock onto a different signal. This feature is handy when several relatively large signals are present. Dual ten-segment bargraphs indicate deviation and relative signal level. A pushbutton switch selects wide- or narrow-band bargraph calibration. An internal rechargeable battery pack provides up to six hours of operation.

The *Model R10 FM Communications Interceptor* is priced at \$359.—**Optoelectronics Inc.**, 5821 NE 14th Avenue, Fort Lauderdale, FL 33334; Phone: 800-327-5912 or 305-771-2050; Fax: 305-771-2052.





FROM

\$19<sup>95</sup>

Standard

\$199<sup>95</sup>

High Performance

GREAT  
VALUE!**Standard Features - Models 100, 150, 200 & 400**

- AC & DC VOLTAGES ● DC CURRENT ● RESISTANCE
- CONTINUITY TESTER - Buzzer ● DIODE TEST ● 3 1/2 Digit LCD
- LOW BATTERY INDICATOR ● ACCURACY +/- 0.5% RDG

Kelvin Meters backed by a  
2 Yr Warranty - Parts & Labor

PRO 400



100 Basic

150 Basic+

200 Advanced

BATTERY TEST

TRANSISTOR hFE

TRANSISTOR hFE

20MHz FREQ

KELVIN

KELVIN

KELVIN

KELVIN

# 990087

# 990090

# 990091

# 990092

100 Basic

150 Basic+

200 Advanced

\$19<sup>95</sup>\$29<sup>95</sup>\$39<sup>95</sup>

PRO 400

\$69<sup>95</sup>**Protective Cases**For Models 100, 150, 200 ..... \$4.<sup>95</sup> (990088)Case For Model Pro 400 ..... \$9.<sup>95</sup> (990094)Model 92  
PERFORMANCE PLUSModel 93  
DIAGNOSTIC PLUSModel 95  
ENGINE ANALYZER PLUS**Standard Features - Models 92, 93, 94 & 95**

- DC/AC VOLTMETERS ● AC/DC CURRENT ● OHM METER
- FREQUENCY COUNTER to 4 MHz ● AUDIBLE CONTINUITY TESTER
- DIODE TESTER ● MAX/MIN AVERAGE MEMORY RECORD
- RELATIVE MODE ● 10A HIGH-ENERGY FUSE PROTECTION
- DATA HOLD ● AUTO SLEEP & AUTO POWER OFF

PERFORMANCE PLUS

Model 92 # 990109

\$119<sup>95</sup>Complete with above **Standard Features** plus  
WATER RESISTANT (92 & 94 Models only),  
2 YEAR WARRANTY, YELLOW HOLSTER,  
PROBES, BATTERY, FUSE, STAND

DIAGNOSTIC PLUS

Model 93 # 990110

\$149<sup>95</sup>Complete with **Standard & Model 92 Features** plus  
LOGIC PROBE, CAPACITANCE TESTER,  
TRANSISTOR TESTER, TEMPERATURE  
TESTER & K-TYPE PROBE, HIGH VOLTAGE  
WARNING BUZZER

ENGINE ANALYZER PLUS

Model 95 # 990112

\$199<sup>95</sup>Complete with **Standard & Model 92 Features** plus  
TEMPERATURE, TACHOMETER & DWELL  
ANGLE TESTER, DUTY CYCLE, 10 MEGA  
OHM IMPEDANCE, ANALOG BAR GRAPH,  
K-TYPE TEMP PROBE, ALLIGATOR CLIP  
TEST LEADS, INDUCTIVE PICKUP CLIP,  
6' TEST LEADS & CARRY CASE**KELVIN**10 HUB DRIVE  
MELVILLE, NY  
11747

M/C &amp; VISA

(800) 645-9212

Established 1945

(516) 756-1750

(516) 756-1763/FAX

**The Ultimate Meter**  
TRUE RMS - LCR - Hz - dBm12 INSTRUMENTS IN ONE - DC VOLTMETER, AC VOLTMETER,  
OHMMETER, AC CURRENT, DC CURRENT, DIODE TESTER, AUDIBLE  
CONTINUITY TESTER, dBm, FREQ COUNTER, CAPACITANCE METER,  
INDUCTANCE METER, LOGIC PROBE0.1% ACCURACY  
on DC VoltagesWater  
Resistant\$199<sup>95</sup>MODEL 94  
#990111COMES COMPLETE WITH  
YELLOW HOLSTER, PROBES,  
BATTERY, FUSE, STAND

Freq Counter to 20 MHz

10 MEGA OHM IMPEDANCE  
RELATIVE MODE / DATA HOLD  
MAX/MIN AVERAGE MEMORY RECORD  
10A HIGH-ENERGY FUSE PROTECTION  
AUTO SLEEP & AUTO POWER OFF with Bypass

Cases for 90 Series Meters

Regular Padded Zippered ... \$9.<sup>95</sup> (#990116)Deluxe Padded Zippered ... \$14.<sup>95</sup> (#990115)This meter is designed in  
accordance with relevant safety  
requirements as specified in IEC-  
348, UL-1244 and VDE-0411.

**ELECTRONICS WORKBENCH SOFTWARE.** *Interactive Image Technologies Ltd.* calls its *Electronics Workbench* software "the electronics lab in a computer." The program in a computer is said to allow users to design, assemble, and test analog and digital circuits by simulation. The company recommends its software for teaching electronics, electronics experimenting, and the prototyping of circuits. The patterns on the computer screen are identical to those that would be displayed on an oscilloscope in an actual test procedure.



CIRCLE 22 ON FREE INFORMATION CARD

The program consists of two modules: the analog module permits the simulation of electronics components and transistors as they would be done with hardware in a real lab. The digital module provides simulated ideal digital components and instruments needed to build and test logic circuits. The analog module includes SPICE simulation. This permits both transient and steady-state analysis.

Among the components that can be simulated with the software are resistors, capacitors, inductors, transformers, diodes, LED's, bulbs, fuses, Zener diodes, and transistors. Both AC and DC voltage and current sources can be

simulated. A function generator provides square, triangular, and sinusoidal waves for test purposes, and a multimeter, dual-trace oscilloscope, and a bode plotter can be called up for making simulated on-screen measurements.

The digital module permits the simulation of ideal logic: and, OR, XOR, NOT, NAND, and NOR gates. Also available in the program are RS, JK, and D-flip-flop functions, a half adder, and a seven-segment LED display. The user can call up a voltmeter and an eight-channel logic analyzer to check out his work. Both logic conversion and simplification can be performed with the software.

Three versions of *Electronics Workbench* are available:

- IBM-compatible Professional—a color version that supports a math coprocessor.
- Personal Plus—for IBM PC's and compatibles, a monochrome alternative.
- Macintosh Program—available in monochrome only.

The Professional Version of *Electronics Workbench* is priced at \$299.—**Interactive Image Technologies Ltd.**, 908 Niagara Falls Boulevard, North Tonawanda, NY 14120-2060; Phone: 416-361-0333; Fax: 416-368-5799.

#### DC-TO-AC POWER INVERTER.

Progress is still being made in the development of DC-to-AC power inverters, according to *Statpower Technologies*. The company says its new *PROwatt 800* 12-volt DC to 115-volt AC power inverter is designed for industrial applications and has a power output of 1000 watts for 10 minutes, 900 watts for 30 minutes and 800 watts continuous.



CIRCLE 23 ON FREE INFORMATION CARD

The *PROwatt* inverter is packaged in a small case measuring 3 x 9 x 10 inches and weighs five pounds. It can produce very high temporary power levels to run loads with high starting surge requirements (such as compressor motors). An LED bar-graph display provides continuous information on battery voltage and power draw. The unit can be easily connected to any deep-cycle storage battery.

*PROwatt's* low no-load current draw easily permits the conversion of most of a vehicle's battery power to usable AC power. Solid-state circuits regulate the output voltage and frequency. *PROwatt's* modified sine wave output is suitable for most electric motors and inductive loads. The output waveform does not change as the input voltage rises or falls. This permits it to power computers, test equipment, TV's, VCR's, and CCTV equipment from an automotive supply.

*PROwatt 800* shuts down if the battery voltage exceeds its high and low limits. Audible alarms and LED indicators warn of faults so that corrective action can be taken. Once a fault is corrected, the unit will automatically restart.

The *PROwatt 800* is priced at \$499.—**Statpower Technologies Corporation**, 7725 Lougheed Highway, Burnaby, BC, Canada, V5A 4V8; Phone: 604-420-1585; Fax: 604-420-1591.

#### RGB VIDEO GENERATOR.

This programmable RGB video generator is intended for use in the design, production, service, and quality control of the most advanced computer-driven CRT and LCD monitor displays. The *Leader model 1605* handles pixel rates to 300 MHz. Its graphic user interface uses on-screen menus and graphic displays with mouse control to provide visual guidance in raster assembly, pattern selection and design, signal drive options, storage, and retrieval. Waveforms are displayed to help in organizing rasters, and patterns are assembled on the screen with a palette of 256 colors from a range of 16.7 million colors. As



CIRCLE 24 ON FREE INFORMATION CARD

many as 100 addresses can be stored in both RAM and ROM and storage capability can be expanded to 1800 addresses on the built-in floppy disk. EPROM's can be programmed by the this video generator without additional equipment, and it will accept data from all earlier *Leader* RGB video generators. High-speed data transfer can be carried out with analog, TTL, and ECL outputs. Those outputs have a wide range of sync options including tri-level sync, half-line equalizers, and serrations.

The *Model 1605* RGB video generator is list priced at \$18,500.—**Leader Instruments Corporation**, 380 Oser Avenue, Hauppauge, NY 11788; Phone: 800-645-5104 (in NY, 516-231-6900). **R-E**

# Graduate as a Fully Trained Electronics Professional!

If you want to learn about electronics, and earn a good income with that knowledge, then CIE is the best educational value you can receive.

CIE's reputation as the world leader in home study electronics is based solely on the success of our graduates. And we've earned our reputation with an unconditional commitment to provide our students with the very best electronics training.

Just ask any of the 150,000-plus graduates of the Cleveland Institute of Electronics who are working in high-paying positions with aerospace, computer, medical, automotive and communications firms throughout the world.

They'll tell you success didn't come easy...but it did come...thanks to their CIE training. And today, a career in electronics offers more rewards than ever before.

## CIE'S COMMITTED TO BEING THE BEST...IN ONE AREA...ELECTRONICS.

CIE isn't another be-everything-to-everyone school. CIE teaches only one subject and we believe we're the best at what we do. Also, CIE is accredited by the National Home Study Council. And with more than 1,000 graduates each year, we're the

largest home study school specializing exclusively in electronics. CIE has been training career-minded students like yourself for nearly sixty years and we're the best at our subject...ELECTRONICS...BECAUSE IT'S THE ONLY SUBJECT WE TEACH!

## CIE PROVIDES A LEARNING METHOD SO GOOD IT'S PATENTED.

CIE's AUTO-PROGRAMMED® lessons are a proven learning method for building valuable electronics career skills. Each lesson is designed to take you step-by-step and principle-by-principle. And while all of CIE lessons are designed for independent study, CIE's instructors are personally available to assist you with just a toll free call. The result is practical training...the kind of experience you can put to work in today's marketplace.

## LEARN BY DOING...WITH STATE-OF-THE-ART EQUIPMENT AND TRAINING.

CIE pioneered the first Electronics Laboratory Course and the first Microprocessor Course. Today, no other home study school can match CIE's state-of-the-art equipment and

training. And all your laboratory equipment, books and lessons are included in your tuition. It's all yours to use while you study and for on-the-job after you graduate.

## PERSONALIZED TRAINING...TO MATCH YOUR BACKGROUND.

While some of our students have a working knowledge of electronics others are just starting out. That's why CIE has developed twelve career courses and an A.A.S. Degree program to choose from. So, even if you're not sure which electronics career is best for you, CIE can get you started with core lessons applicable to all areas in electronics. And every CIE Course earns credit towards the completion of your Associate in Applied Science Degree. So you can work toward your degree in stages or as fast as you wish. In fact, CIE is the only school that actually rewards you for fast study, which can save you money.

## SEND FOR YOUR CIE COURSE CATALOG AND WE'LL SEND YOU A FREE 24-PAGE CIE ELECTRONIC SYMBOLS HANDBOOK.

**YES!** I want to get started. Send me my CIE course catalog including details about the Associate Degree Program. (For your convenience, CIE will have a representative contact you - there is no obligation.)

AE45

Please print clearly

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Zip \_\_\_\_\_ Age \_\_\_\_\_

Phone No. (\_\_\_\_) \_\_\_\_\_

Check box for G.I. Bill Benefits

Veteran  Active Duty



1776 East 17th Street  
Cleveland, Ohio 44114

A School of Thousands.  
A Class of One. Since 1934.

# FREE!

SEND FOR YOUR CIE HOME STUDY COURSE CATALOG AND RECEIVE A FREE 24 PAGE CIE ELECTRONIC SYMBOLS HANDBOOK!

Includes hundreds of the most frequently used electronic symbols. Published exclusively by CIE for our students and alumni. Yours free when you request a CIE Course Catalog.

electronics



# NEW LIT

Use The Free Information Card for fast response.

**1993 CATALOG;** from Radio Shack, 700 One Tandy Center, Fort Worth, TX 76102; free at local Radio Shack Stores.

Radio Shack's 1993 catalog has a redesigned layout and organization as well as a lot of new products. The 172-page, full-color, magazine-sized catalog now has a "Quick Index" up front, and a complete index at the end. New products highlighted in this edition include the Duofone ET-499 voice-scrambling cordless telephone. It scrambles the transmission between the handset and the base so



**CIRCLE 40 ON FREE INFORMATION CARD**

people with nearby scanners can't eavesdrop on your conversations.

Others are the Memorex Model 800 8mm home VCR with stereo sound and the portable Model 17 8mm VCR/TV combination, both with 179-channel TV tuners. Tandy is offering

a 25-MHz, 486-based multimedia PC that includes a wide selection of software for voice mail, communications, travel planning, and more.

Also included in the 1993 catalog are telephones and accessories, pagers, scanners, world-band transceivers, VHS VCR's, remote controls, and automotive sound systems. There are also entries on home-control products, batteries, flashlights, multi-use testers, remote-controlled toys, computer based language and information sources, calculators, personal organizers, and notebook PC's.



**CIRCLE 39 ON FREE INFORMATION CARD**

ther for or against the theories that are the subjects of his experiments. However, the underlying concepts are fully explained.

**1992/1993 DISCOUNT TEST EQUIPMENT CATALOG.** Print Products International, 8931 Brookville Road, Silver Spring, MD 20910; Phone: 1-800-638-2020 or 1-301-587-7824; Fax: 1-800-545-0058 or 1-301-585-5402; free.

Here is another discount equipment catalog. This one has 68 pages filled




**CIRCLE 38 ON FREE INFORMATION CARD**

with entries on bargain-priced test and measurement equipment from such well-known manufacturers as Kenwood, B + K, Avcom, Pace, Philips, Hitachi, and Leader. Included in the catalog's coverage are oscilloscopes, power supplies, meters, and spectrum analyzers. In addition, the catalog describes new lines of closed-circuit TV systems for security and monitoring.

R-E

## Go ahead, put on some weight

 

Introducing the improved 372 Circuit Board Holder. A longtime favorite for circuit board work, the 372 now comes with our redesigned 300 base. A new, patented, internal modification to the 300 split ball locking mechanism allows it to hold twice as much weight as its predecessor. Of course, the 372 still comes with the industry's best circuit board holder, the PanaVise 315, which can hold PCBs up to 12 inches wide (up to 28" with 30" 318 Accessory Cross Bars.) You can even handle multiple boards when you use additional 316 Circuit Board Arms. The new PanaVise 372 Circuit Board Holder. When circuit boards are your business.

**PANA VISE**

1485 Southern Way • Sparks, NV 89431 • (702) 353-2900 • FAX (800) 395-8002


**CIRCLE 197 ON FREE INFORMATION CARD**

**21ST-CENTURY ELECTRONIC PROJECTS FOR A NEW AGE;** by Delton T. Horn. TAB Books, Division of McGraw-Hill Inc., Blue Ridge Summit, PA 17294-0850; Phone: 1-800-822-8138; \$16.95.

The term "New Age," usually associated with mysticism, music, and cultural fads, has now been applied to electronics projects by Mr. Horn in his new book. This volume—from a well known and prolific writer—presents an array of unusual electronic projects intended to test and demonstrate theories underlying New Age beliefs.

Included among the projects in the book are a dual-LED visual hypnotic aid, an alpha-wave biofeedback monitor, a two-choice ESP tester, a negative-ion generator, a biorhythm clock, a Kirlian photography experimental circuit, and a magnetic-field tester. Mr. Horn does not take a stand ei-
 
# Master Electronics with TAB/McGraw-Hill, Inc.



## INTERNATIONAL ENCYCLOPEDIA OF INTEGRATED CIRCUITS—2ND ED.

Find the circuits you need fast. This all-in-one reference gives you complete descriptions of: circuit functions and uses, pinout diagrams with external connections, tables and charts, and manufacturer data. 1,168 pp., 4,000 illus. #3802H, \$84.95...NOW ONLY \$44.95

## MICROWAVE OVEN REPAIR—2ND ED.

Save hundreds of dollars in microwave oven repair. Service low- and high-voltage problems • locate and replace the magnetron • repair oven motors and control circuits • and test for microwave leakage. 368 pp., 366 illus. #3457H, \$29.95

## TROUBLESHOOTING AND REPAIRING SOLID-STATE TVs

—2ND ED. Zero in on solid-state TV problems with this hands-on guide. You'll be able to repair virtually any malfunction, including: remote controls, power supplies, sweep circuits, chassis, picture tubes, and tuners. 624 pp., 698 illus. #3700H, \$36.95

Pass the CET exam with ease!

## CET EXAM BOOK—3RD ED.

Use the many sample tests in this brand-new edition to increase your knowledge of repairing and maintaining electronic equipment. 304 pp., 180 illus. #4199H, \$27.95

## CET STUDY GUIDE—3RD ED.

Identify the gaps in your electronics know-how—and learn about the theories and principles involved—with this new guide's sample questions and advice. 320 pp., 200 illus. #4076H, \$27.95

**SAVE** Order both guides (#586274-3) for only \$49.00 (regularly \$55.90)

## PRACTICAL ANTENNA HANDBOOK

Get the step-by-step instructions you need to install and utilize a variety of antennas, including • mobile • shortwave • dipole • multi-band • long-wire directional • marine radio • VHF/UHF • microwave • and more. 439 pp., 351 illus. #3270H, \$32.95

## HOME VCR REPAIR ILLUSTRATED

Save hundreds of dollars in repair bills by fixing your own VCR—no expensive equipment or experience required! You'll repair • picture and sound • fast forward and rewind • dc motors • roller guides • audio heads • and more! 400 pp., 459 illus. #3711H, \$29.95

## MAINTAINING AND REPAIRING VCRS—2ND ED.

Get the details on repairing all types of VCRs: VHS HQ, 8mm, and camcorders. You get in-depth coverage of: every mechanical system and electronic circuit used in VCRs, the use of test equipment including Sencore SC61 and VC63, high-quality (HQ) camcorders, and special VCR circuits. 352 pp., 370 illus. #3103H, \$27.95

## SIMPLIFIED PRACTICAL FILTER DESIGN

Easy-to-follow techniques show you how to lay out and assemble practical, working filters. You'll easily design all these filters: low-pass, high-pass, band rejection, M-derived, composite, crystal, and even crossover networks. 200 pp., 137 illus. #3355H, \$26.95

To Order Call Toll-Free **1-800-822-8158** 24 Hours A Day

FAX orders: 1-717-794-2080 • Or mail coupon to: TAB/McGraw-Hill, Inc. Blue Ridge Summit, PA 17294-0840

Please cut along dotted line

**Satisfaction Guaranteed**—Within 30 days, pay the stated amount (plus shipping, handling, and state and local sales tax) or return book(s) and owe nothing.

Please send me the book(s) below for a FREE 30-Day exam:

Book#	Title	Qty.	Price

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_

Signature \_\_\_\_\_

Orders outside the U.S. must be prepaid in U.S. funds drawn on U.S. banks and include \$5.00 for postage and handling. Prices subject to change. Limit 3 books on a 30-day trial only. Orders of 4 books or more must include payment. Shipping and handling charges will be billed to your account. Order invalid without signature.

RE1228

Please Print



# THE PARTS PLACE

**Come in for Your FREE Radio Shack Catalog!**

The most important part of your next project is the all-new, 172-page 1993 Radio Shack catalog. It's yours for the asking at our store or dealer near you. Hurry in today—supplies are limited!



## TECHLINE™ Tools—The new standard in strength and precision!



- Precision-crafted with top-quality materials
- Designed for long life and ease of use
- Backed by Radio Shack's 1-Year Limited Warranty

New TECHLINE tools represent Radio Shack's uncompromising dedication to quality. Each is precision-crafted of long-lasting, hard-working materials and employs the latest design innovations for comfort and ease of use. And, each is backed by our full 1-year limited warranty.

## Speedy service and low prices on thousands of parts and accessories!



- FREE delivery to Radio Shack on orders \$5 and up
- Semiconductors and ICs ■ Hard-to-find batteries
- CB and scanner crystals ■ Long-life vacuum tubes
- Phono cartridges/styli ■ SAMS® service books

Why pay more for mail-order? Your Radio Shack stocks 1000 electronic components, and another 15,000 are available *fast* from our special-order warehouse. Ordering is easy! Bring in the exact part number (or old part). We'll check availability and order by phone. Delivery time to your nearby Radio Shack for most items is a week.



(1) PicoFarad 50-Pack. Delight for tweakers. 50 ceramic capacitors, assorted 1 to 33 pF values. 50 WVDC. #272-806 ..... 2.99

(2) Efficient PC-Mount Piezo Buzzer. Tiny yet has 70 dB output and requires only 7 mA at 12VDC. #273-074 ..... 2.99

(3) Omnidirectional Electret-Type Mike Element. 30-15,000 Hz. 4 to 10 VDC. #270-092, 2.99




Test-Equipment Adapters. Great for use with scopes, frequency counters and multimeters. Hook up with the best.

(1) Binding Posts to BNC Plug. 50 ohms impedance. #274-715 ..... 8.95

(2) Binding Post to Banana Plug. #274-716 ..... Set of 2/4.95

 (3) Stackable Dual-In-Line Banana Plug. #274-717 ..... 2.99



Resistor Assortments. Popular values—stock up and save.

Description	Cat. No.	Set of	Price
Metal-Film 1/4W	271-309	50	2.29
Carbon 1/4W	271-308	100	2.99
Carbon-Film 1/2W	271-312	500	7.95
Carbon 1/2W	271-306	100	3.49

Mini Audio Amp With a Built-in Speaker. Many uses! Tough 3 3/8" high case. Low Radio Shack price. #277-1008 ..... 11.95




(1) Magnet Wire Assortment. For custom coil winding. Includes 40 feet of 22-gauge, 75 feet of 26-gauge and 200 feet of 30-gauge on spools. #278-1345 ..... 4.99

 (2) Dial Cord Fix-It Kit. Our exclusive! Includes six feet of high-strength cord and three tension springs. Put a radio back into action! #274-435 ..... 99¢




High-Speed 12VDC Mini-Motor. Produces an amazing 15,200 RPM at no load. Ideal for projects, robotics, fun! About 2" long (with shaft). #273-255 ..... 2.99



PC/XT Circuit Card. Epoxy. Fits computer expansion bus. 10 1/16" long. #276-1598 ..... 29.95

 Right-Angle D-Sub 25 Female Connector for Above. #276-1504 ..... 2.69



Infrared Project Box. Ideal for a remote. Has removable infrared-transparent end panel and space for 9V battery. 7/8 x 2 3/8 x 4 1/4". #270-294 ..... 4.49



100-Watt Soldering Gun. For big jobs! Reaches full temperature in seconds. Built-in work light. Replacement tips in stock. UL listed. #64-2193 ..... 11.95

**Radio Shack** SINCE 1921  
**AMERICA'S TECHNOLOGY STORE** SM  
 A DIVISION OF TANDY CORPORATION

Prices apply at participating stores and dealers.

CIRCLE 78 ON FREE INFORMATION CARD

# GLITTER GLOBE

WE'D LIKE TO PRESENT ONE OF THE most unusual construction projects you're likely to build. Calling the Glitter Globe simply a construction project does not do it justice—calling it an *electronic sculpture* is more accurate. This is a challenging project, and not for the inexperienced builder. Building the Glitter Globe is a lot like building a model airplane or car, because the quality of your workmanship will be very evident in the finished appearance of the circuit. You can't hide sloppy construction inside a case!

The Glitter Globe is perhaps the world's most sophisticated Christmas ornament: it's constructed entirely of electronic components and very small circuit boards. Each circuit board holds a pair of LED's that chase each other around the globe, creating the illusion that the globe is spinning. The LED's can be the same or different colors, and at least 12 LED's light up at each step. One diagonal line of LED's is always one step ahead of another, creating the illusion that the Glitter Globe is spinning.

Two different animations are possible depending on the value of a resistor (R2): the globe can appear to accelerate and decelerate smoothly over a time period of about 20 seconds, or it can slow gently until almost stopping, and then accelerate quickly. The cycle then repeats. The globe can hang from its power cord in a Christmas tree or lie on any flat surface.


The small PC boards used to make the Glitter Globe can also be hidden in various places (other than as part of the Glitter Globe), such as in clothing or behind photographs, to add lights at strategic places. Art forms of this kind are rather popular.

The Glitter Globe is a geodesic sphere; the particular shape is a star-dodecahedron with twenty

vertices, which is one of two star-dodecahedra known as the star polyhedra of Kepler. The other star polyhedra has twelve vertices, and could also be constructed from the Glitter Globe's board set.

varies the acceleration of the globe's apparent rotation by integrating a DC voltage to the trip point of a Schmitt trigger (IC1-b). After IC1-b trips, IC1-a integrates in the opposite direction until the other trigger

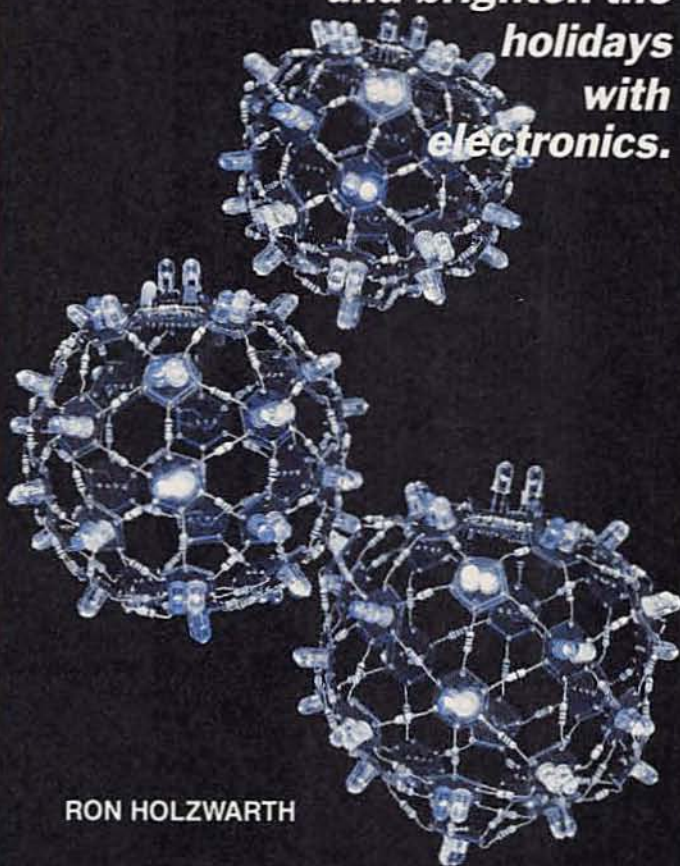**Build the Glitter Globe,  
and brighten the  
holidays  
with  
electronics.**



RON HOLZWARTH

## Circuit description

Figure 1 is the schematic for the Glitter Globe, which is powered from a 12-volt DC supply. (It can therefore be powered from a car's cigarette lighter.) The first stage of the circuit is a triangle/sawtooth waveform generator made from IC1-a and -b, which are part of an LM3900 quad-amplifier chip. This stage

point is reached. Increasing the value of C1 will lengthen the time period between accelerations. Resistor R2 is set at 2 megohms for a triangle wave output and 200 kilohms for a negative-ramp sawtooth output.

The output of the waveform generator goes to the input of IC1-c, a voltage-controlled os-

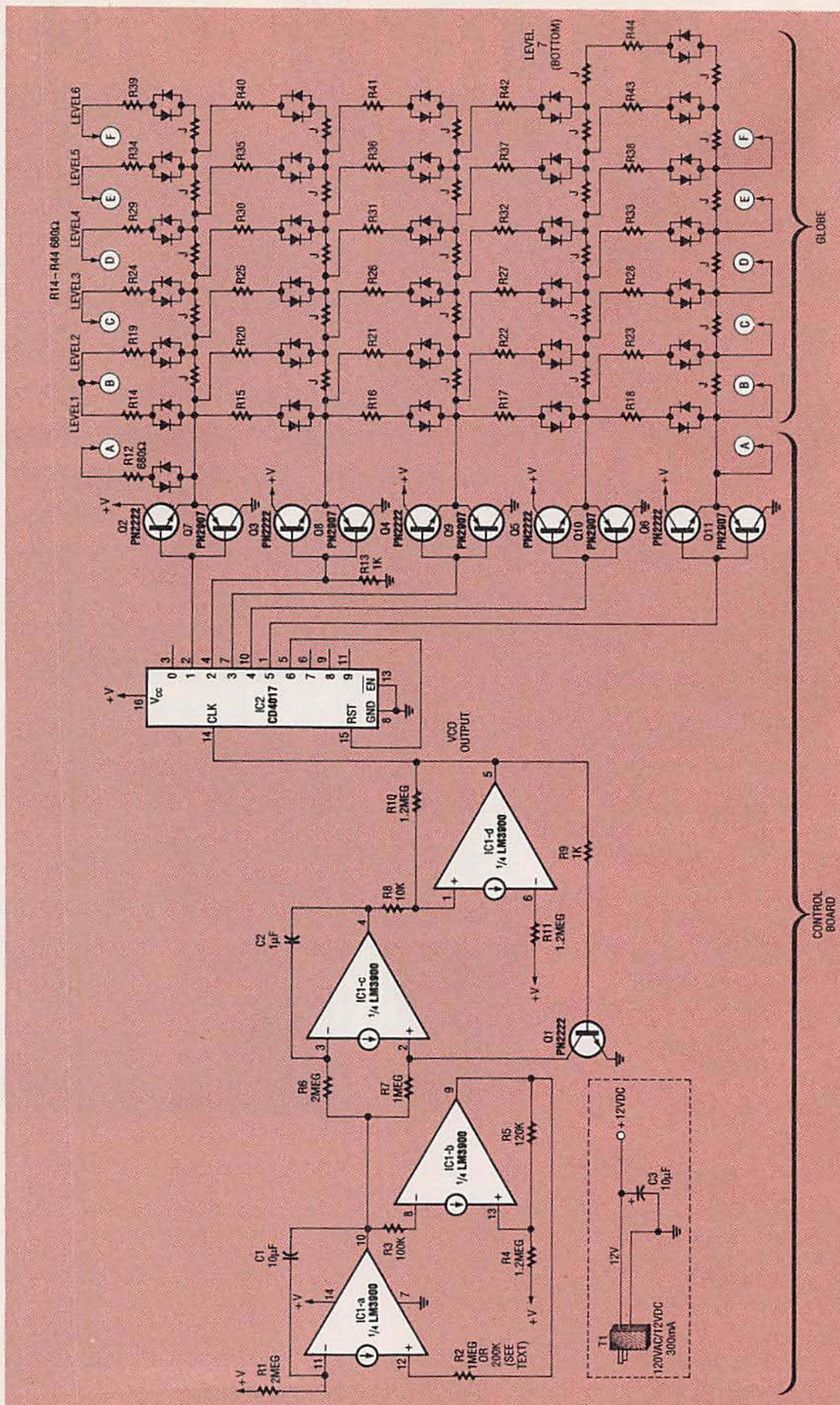


FIG. 1—GLITTER GLOBE SCHEMATIC. The first stage of the circuit, a triangle/sawtooth waveform generator, varies the speed of the Glitter Globe's apparent rotation. All horizontal resistors marked with a "J" are zero-ohm jumpers.



 


FIG. 2—THE GLITTER GLOBE'S BOARDS are supplied on a breakout panel.

 


FIG. 3—CONTROL BOARD PARTS PLACEMENT. Capacitors C1 and C2, and all of the transistors, except Q1, are installed on the solder side of the board. The "c" silkscreened on the board indicates the collector lead of each transistor.

 


FIG. 4—YOU CAN MAKE a softball-sized star dodecahedra by forming all the structural resistors and jumpers approximately 3/4-inch long. The pentagon boards stick out a little more than the hexagon boards.

cillator (VCO). The VCO operates very much like the waveform generator except that its voltage reference is the output of the waveform generator in-

stead of the power supply. When transistor Q1 conducts, it grounds pin 2 of IC1-c and the output voltage of the integrator decreases. When the trip point is reached, Q1 ceases conduction, and the output then rises again. The value of C2 (as well as the voltage from the function generator) determines the speed of rotation. To decrease the speed of the spin action, simply increase the value of C2.

The output of Schmitt trigger IC1-d is the input for IC2, a CD4017 decade counter. Only five outputs of the counter are used; after a count of five, the counter resets, resulting in continuous "motion" around the globe.

Since the outputs of IC2 cannot provide enough current to

 


FIG. 5—YOU CAN MAKE a hardball-size star dodecahedra by keeping all the structural resistors and jumpers approximately 1/2-inch long.

drive a dozen or more LED's, transistor pairs (a PN2222 and a PN2907) are used to drive them. A high output from IC2 turns on the NPN transistors (the PN2222's) and a low output turns on the PNP transistors (the PN2907's). The output of IC2 that is high will turn on the PN2222 transistor connected to it, which sources the LED current. The current is then drained through the two PN2907 transistors on the adjacent outputs.


Zero-ohm resistors (jumpers) distribute power around the globe. Plain wire jumpers could be used, but the zero-ohm resistors look much better. Current-limiting 680-ohm resistors (one for each LED pair) ensure that less than 20 milliamperes passes through each forward-biased LED during conduction.

The LED's are all connected back to back so that current flow in one direction lights one, and current flow in the other direction lights the other. That way a color orientation is maintained as the Glitter Globe steps around its five outputs.


Conduction through one LED limits the reverse voltage across the opposite LED. That's not a concern, except with blue LED's which have a reverse-voltage limit of only 5 volts.
 
#### Assembly

Before beginning assembly, have the following tools on hand: a small vise or clamp to hold the globe steady as you work, a pair of needle-nose



 COMPONENT SIDE of the Glitter Globe's breakout panel.



SOLDER SIDE of the Glitter Globe's breakout panel.

GG 02  
Dec 92  
Electronics Now

## PARTS LIST

All resistors are 1/4-watt, 5%.

R1, R6—2 megohms  
R2—1 megohm for triangle wave,  
200,000 ohms for sawtooth wave  
R3—100,000 ohms  
R4, R10, R11—1.2 megohms  
R5—120,000 ohms  
R7—1 megohm  
R8—10,000 ohms  
R9, R13—1000 ohms  
R12, R14—R44—680 ohms

### Capacitors

C1—10  $\mu$ F, 16 volts, nonpolarized electrolytic  
C2—1  $\mu$ F, 16 volts, nonpolarized electrolytic  
C3—10  $\mu$ F, 25 volts, tantalum electrolytic

### Semiconductors

IC1—LM3900 quad amplifier  
IC2—CD4017 decade counter  
Q1—Q6—PN2222 NPN transistor  
Q7—Q11—PN2907 PNP transistor

**Miscellaneous:** 64 LED's (any color), 28 structural resistors (680-ohm units will match the rest of the resistors), 25 zero-ohm jumpers, 12-volt DC 300-mA wall transformer, PC board set, solder, etc.


**Note:** The following items are available from Art Works, 415 E. Emerson Street, Saint Francis, Kansas 67756:

- Set of 32 PC boards, supplied on a breakout panel—\$30.00 each, three or more are \$25.00 each
  - Complete Glitter Globe kit (includes PC board, 300-mA wall transformer, 64 LED's, and all components)—\$65.00 each, three or more are \$55.00 each
- All prices include taxes, shipping, and handling. Please state LED color preference (red, green, or yellow); colors can be mixed. Visa/Mastercard orders (800) 486-6862. For technical assistance call (913) 332-2726. Blue LED's are not available with the kit.

pliers, a small file, a pair of clippers, and a desoldering tool or desoldering braid.

All of the Glitter Globe's boards are supplied on a breakout panel (see Fig. 2). The control board should be assembled first; its parts-placement diagram is shown in Fig. 3. Remove the control board from the breakout panel and file off the excess material.

Insert the components into the control board, making sure that the IC's are inserted correctly and that the tantalum capacitor (C3) is inserted with the proper polarity. Capacitors C1 and C2, and all of the transistors, except Q1, are installed on the solder side of the board. The "c" silkscreened on the board indicates the collector

 


**FIG. 6—TO MAKE A SPHERICAL GLOBE,** all of the resistors and jumpers that connect to any five-point board (levels 2, 5, and 7) must be preformed to 5/8-inch, with the rest remaining 3/4-inch.

lead of each transistor. Looking at the flat side of the transistors with the leads pointed down, the leads are, from left to right, emitter, base, and collector.

In the center of the control board there is a hole for soldering a loop of wire that acts as a strain relief for the power leads. Strip and tin the ground and power wires from the transformer, and then insert them through the center support loop before soldering them into the PC board. The transformer included with the kit (see the Parts List) has the positive lead marked with a white stripe—other transformers can be marked with the opposite convention, so be sure to check the polarity before soldering!

Test the control board to make sure that it works correctly before building the rest of the globe. When powered up, the two LED's on the control board should light sequentially, and then stay off for a brief time. The flash rate change will be

 

**FIG. 7—THIS "COMPONENT MAP" shows how the level 1-4 pieces connect together.** All connections marked "J" are zero-ohm jumpers, all connections showing a resistor symbol must be 680 ohms, and all unmarked connections can be made using any material you like.

very obvious. Unplug the transformer before continuing.

The LED boards are numbered on one side in groups from 1 to 7. Groups 1-6 contain five boards each; group 7 is just a single board. The numbers represent the levels away from the controller board in which the LED boards are installed. For example, level-1 boards are installed immediately around the controller board, level 2 surrounds level 1, 3 surrounds 2, and so on. All boards in each level are identical. Locate the numbered side of each board on the inside of the globe, with the LED's on the outside. Putting the numbers on the outside of

the globe will result in the diagonal power busses (and thus the lighting pattern) running the other way, although the spin direction will remain unchanged. Also, always position the LED boards so that the numbers on their inside surfaces are pointing away from the control board.

Solder the LED's into the small PC boards before removing them from the breakout panel. If you are making a globe with two colors, one color should always be on the left, and the other on the right. Because changing a defective LED can be very difficult after the globe is assembled, test all LED's before soldering. Some multimeters can quickly check LED's; otherwise set up a DC power supply and current-limiting resistor to make sure all the LED's work. The LED's are installed in the boards with their cathodes facing each other (with the flat sides toward each other). Clip excess leads after soldering.

It's much easier to keep the small boards oriented correctly while adding them to the globe

if you remove them from the panel only as needed. When you remove the boards from the breakout panel, use a small file to remove any excess material.

### Shapes

The least difficult shape to complete is the star dodecahedron. That's the shape that results if all the structural resistors and jumpers are preformed to the same length—approximately  $\frac{3}{4}$ -inch. Their actual lengths are not critical, as long as they are all equal. That results in the pentagon (five point) boards sticking out a little more than the hexagon (six point) boards (see Fig. 4). With  $\frac{3}{4}$ -inch spacing, the globe will be about the size of a softball.

It is possible to construct a globe with a uniform resistor spacing of  $\frac{1}{2}$ -inch, but this should be attempted by only the most skilled assemblers. That results in globe the size of a baseball (see Fig. 5). Once you decide on the proper lead spacing for the globe you wish to build, use a bending jig to make all components the same length. If you don't have a real bending jig, cut a piece of wood to the proper width ( $\frac{1}{2}$ -inch,  $\frac{3}{4}$ -inch, etc.), and make a depression in it for the body of the component. You can do that by pressing an unneeded resistor into the wood to leave an impression. (Try to center the impression within the width of the wood.)

Although it might seem to be easier to loop the resistors and jumpers through the boards, it is not recommended because they are difficult to remove later, in case of an error. It's best to put the lead straight through the PC board, and then snip it off after soldering. If a repair is necessary, the lead can then be lifted straight out after remelting the solder.

To make the globe into a spherical shape about the size of a softball, all of the resistors and jumpers that connect to any five-point board (levels 2, 5, and 7) must be preformed to  $\frac{5}{8}$ -inch, with the rest remaining  $\frac{3}{4}$ -inch (see Fig. 6).

*Continued on page 85*

 


FIG. 8—IF YOU USE  $\frac{3}{4}$ -inch spacing, level 1 mounts as shown in a; for  $\frac{1}{2}$ -inch spacing, level 1 mounts as shown in b.

 


FIG. 9—LEVEL 5-7 COMPONENT MAP. The letters surrounding the two halves in Figs. 7 and 9 indicate the connections between them. Install each level in order from 1 to 7.

More  
Lessons!

More  
Services!

# A Shocking Offer!

Now you don't have to be enrolled at CIE to receive our introductory Electronic and Electricity Lesson Modules. This program is available for a limited time to non-students for the shockingly low price of only \$99.50.

With CIE's patented AUTO-PROGRAMMED method of learning you will quickly learn and then master the basics of electronics and electricity and then move on to... DC/AC circuit theories, fundamentals of bi-polar junction transistors (BJT), field effect transistors (FET), wiring, diagram and schematic readings, component identification, soldering techniques... and much, much, more. This introductory offer includes the first 39 lessons in CIE's Associate in Applied Science in Electronic Engineering Technology Degree.

Your commitment to CIE ends with your payment, but CIE's commitment to your success just begins when you receive your lessons, exams, binder and equipment. This special introduc-

tory price includes all the benefits and assistance CIE normally extends to its full time students. You'll be entitled to unlimited access to CIE's faculty and staff to assist you in your studies via a toll free 800 number six days a week, 24-hour turnaround on grading your submitted exams, CIE bookstore privileges, a patented learning method, reference library, access to CIE's electronic bulletin board and a free issue of CIE's school newspaper The Electron.

**And best of all, when you decide to continue your electronics education in any of CIE's programs you'll receive full academic credit for successful lessons submitted and a \$100.00 Tuition Credit Certificate.**

All this knowledge and support will put you on the road to understanding digital electronics, automotive and industrial electronics, microprocessing principals, computer systems, telecommunications and much, much, more.



All This For Only!

# \$99.50

- \$100.00 Tuition Credit
- Academic Credit
- Free issue of The Electron
- Build your personal burglar alarm
- Toll Free Instructor Assistance
- 24-hour grading
- CIE bookstore privileges

- 39 theory and hands-on training lessons and exams.
- Patented learning method
- CIE electronic bulletin board privileges

**Yes! Send me CIE's Introductory Electronic and Electricity Lessons and Equipment.** A7316

Name: \_\_\_\_\_  
 Street: \_\_\_\_\_ Apt#: \_\_\_\_\_  
 City: \_\_\_\_\_  
 State: \_\_\_\_\_ Zip: \_\_\_\_\_  
 Age: \_\_\_\_\_ Phone: (\_\_\_\_\_) \_\_\_\_\_



**BOOKSTORE**  
1776 East 17th Street  
Cleveland, Ohio 44114

Total Merchandise: \_\_\_\_\_ \$99.50

Ohio Residents add 7% Sales Tax: \_\_\_\_\_

California Residents add 6 1/2% Sales Tax: \_\_\_\_\_

Total This Order: \_\_\_\_\_

Shipping and Handling Charge: \_\_\_\_\_ \$5.00

Method of Payment/Amount Enclosed: \_\_\_\_\_ \$

Personal Check or Money Order

Master Card  Visa  Discover

Card Expiration Date: \_\_\_\_\_

Signature: \_\_\_\_\_



**CHARGE BY PHONE!**

9 AM to 4:30 PM Eastern Time:  
1-800-321-2155 ext. A7316

48 HOUR SHIPPING

# ELENCO & HITACHI & B+K PRODUCTS AT DISCOUNT PRICES

TO ORDER  
CALL TOLL FREE  
1-800-292-7711  
1-800-445-3201 (Can.)

## ELENCO OSCILLOSCOPES



**S-1325 25MHz \$349**  
Dual Trace Oscilloscope

**S-1340 40MHz \$495**  
Dual Trace Oscilloscope

**S-1360 60MHz \$775**  
Dual Trace, Delayed Sweep

- Automatic beam finder
- Built-in component tester
- 1mV sensitivity
- Dual time base

## B+K OSCILLOSCOPES

2120 - 20MHz Dual Trace	\$395
2125 - 20MHz Delayed Sweep	\$539
1541B - 40MHz Dual Trace	\$749
2160 - 60MHz Dual Trace, Delayed Sweep, Dual Time Base	\$949
2190 - 100MHz Three Trace Dual Time Base, Delayed Sweep	\$1,395
2522 - 20MHz / 10MS/s Storage	\$869
1442 - 20MHz Portable	\$1,229
1443 - 40MHz Battery / AC operated with Cursor & Readouts	\$1,439

## 1.0GHz PORTABLE SPECTRUM ANALYZER Model 2610 \$2,595.95

- AC/DC operation (battery included)
- 70dB dynamic range
- Resolution bandwidth of 10kHz
- 50Ω and 75Ω input impedance (switch selectable)
- Fixed bandwidth setting for viewing TV signals
- Field calibratable with internally generated 100MHz, 80dB signal

## Hitachi Compact Series Scopes

V-212 - 20MHz Dual Trace	\$409
V-525 - 50MHz, Cursors	\$975
V-523 - 50MHz, Delayed Sweep	\$949
V-522 - 50MHz, DC Offset	\$849
V-422 - 40MHz, DC Offset	\$749
V-222 - 20MHz, DC Offset	\$625
V-660 - 60MHz, Dual Trace	\$1,095
V-665A - 60MHz, DT, w/cursor	\$1,325
V-1060 - 100MHz, Dual Trace	\$1,375
V-1065A - 100MHz, DT, w/cursor	\$1,649
V-1085 - 100MHz, QT, w/cursor	\$1,995
V-1100A - 100MHz, Quad Trace	\$2,195
V-1150 - 150MHz, Quad Trace	\$2,695

## Hitachi RSO Series

RSO's feature; roll mode, averaging, save memory, smoothing, interpolation, pretriggering, cursor measurements.

VC-6023 - 20MHz, 20MS/s	\$1,650
VC-6024 - 50MHz, 20MS/s	\$1,950
VC-6025A - 50MHz, 20MS/s	\$2,350
VC-6045A - 100MHz, 40MS/s	Call
VC-6145 - 100MHz, 100MS/s	Call

## Digital Capacitance Meter



**CM-1550B \$58.95**  
9 Ranges  
.1pF-20,000uF  
5% basic acy.  
Zero control w/ Case  
Big 1" Display

## Digital LCR Meter



**LC-1801 \$125**  
Measures:  
Coils 1uH-200H  
Caps .1pF-200uF  
Res .01-20M

## Multimeter with Capacitance & Transistor Tester



**\$55 CM-1500B**  
Reads Volts, Ohms  
Current, Capacitors,  
Transistors and  
Diodes / with case

## FLUKE MULTIMETERS

<b>Scopemeters</b>	(All Models Available Call)
Model 93	\$1,095.00
Model 95	\$1,395.00
Model 97	\$1,695.00
<b>10 Series</b>	
Model 10	\$62.95
Model 12	\$79.95
<b>70 Series</b>	
Model 70II	\$65.00
Model 77II	\$145.00
Model 79II	\$169.00
<b>80 Series</b>	
Model 87	\$289.00

## Quad Power Supply XP-580



**\$69.95**  
2-20V @ 2A  
12V @ 1A  
5V @ 3A  
-5V @ .5A

Fully regulated and short circuit protected

## Triple Power Supply XP-620



**Assembled \$75 Kit \$50**  
2 to 15V @ 1A,  
-2 to -15V @ 1A  
(or 4 to 30V @ 1A)  
and 5V @ 3A

All the desired features for doing experiments. Features short circuit protection, all supplies

## AM/FM Transistor Radio Kit with Training Course

**Model AM/FM 108 \$27.95**

14 Transistors • 5 Diodes  
Makes a great school project



**True RMS 4 1/2 Digit Multimeter M-700T \$135**

.05% DC Accuracy  
.1% Resistance  
with Freq. Counter  
Data Hold

## Sweep/Function Generator with Freq. Counter



**\$259**  
Elenco  
Model GF-8026

Sine, Square, Triangle, Pulse, Ramp  
.2 to 2MHz, Freq Counter .1-10MHz  
Internal Linear & Logic Sweep

## Function Generator Blox



**#9600 \$28.95**

Provides sine, triangle, square wave from 1Hz to 1MHz  
AM or FM capability

## XK-500 Digital / Analog Trainer

A complete mini-lab for building, testing, prototyping analog and digital circuits. Elenco's Digital/Analog Trainer is specially designed for school projects, with 5 built-in power supplies. Includes a function generator with continuously variable, sine, triangular, square wave forms. All power supplies are regulated and protected against shorts.

### Power Supplies

- Variable Power Supply
- +1.25 to 20VDC @ .5 Amp (+1.25 to 15VDC @ 1 Amp)
- -1.25 to -20VDC @ .5 Amp (-1.25 to -15VDC @ 1 Amp)
- +12VDC @ 1 Amp
- -12VDC @ 1 Amp
- +5VDC @ 1 Amp
- 30VAC Center tapped @ 15VAC at 1 Amp

### Analog - Section

- Function Generator Sine, Triangular, Square wave forms
- Frequency adjustable in five ranges from 1 to 100kHz
- Fine frequency adjust
- Amplitude adjust
- DC offset
- Modulation FM-AM

### Digital - Section

- Eight data switches
- Two no bounce logic switches
- 8 LED readouts TTL buffered
- Clock frequency 1 to 100kHz
- Clock amplitude 5VPP square wave

### Breadboards

- 2 breadboards, each contain: 840 tie points (total 1,680)



**\$159.95**

Assembled

**\$129.95 Kit**

## Learn to Build and Program Computers with this Kit

Includes: All Parts, Assembly and Lesson Manual

**Model MM-8000**

**\$129.00**



Starting from scratch you build a complete system. Our Micro-Master trainer teaches you to write into RAMs, ROMs and run a 8085 microprocessor, which uses similar machine language as IBM PC.

## Elenco Wide Band Signal Generators



**SG-9000 \$129**  
RF Freq 100K-450MHz AM Modulation of 1KHz Variable RF output  
**SG-9500 w/ Digital Display & 150 MHz built-in Counter \$249**

**WE WILL NOT BE UNDERSOLD**

UPS SHIPPING: 48 STATES 5%  
IL RES 7.5% TAX (\$3 min \$10 max)

PROBES INCL ALL SCOPES & METERS

**C&S SALES INC.**

1245 ROSEWOOD, DEERFIELD, IL 60015  
FAX: 708-520-0085 • (708) 541-0710




**15 DAY MONEY BACK GUARANTEE**

**FULL FACTORY WARRANTY**

**WRITE FOR FREE CATALOG**

PRICES SUBJECT TO CHANGE

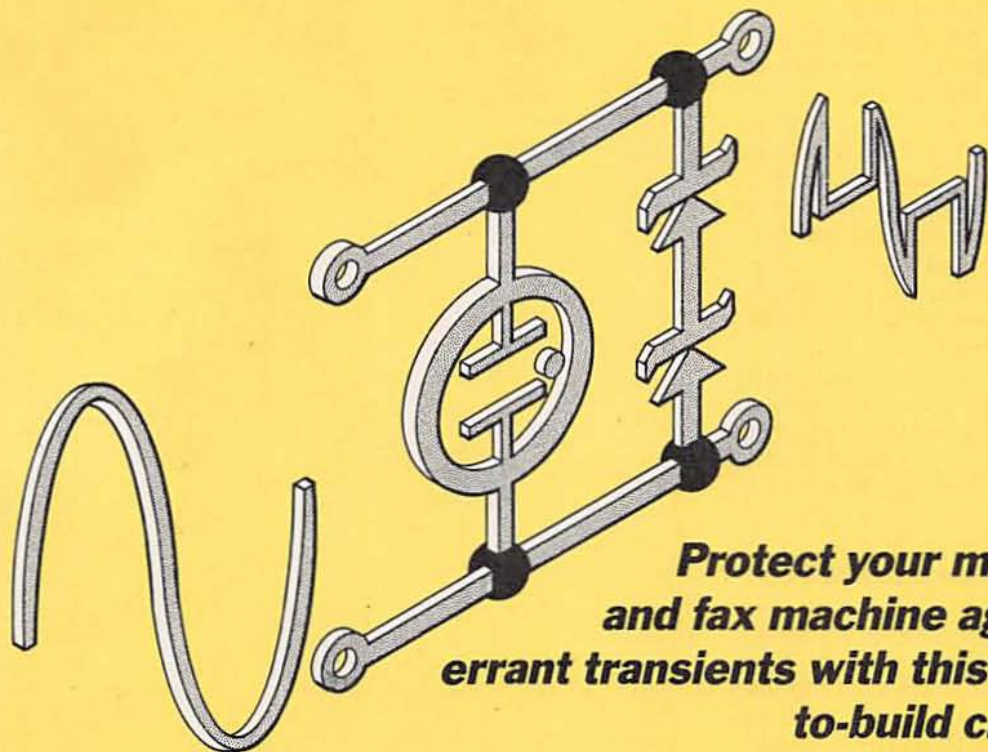

**Protect your modem  
and fax machine against  
errant transients with this easy-  
to-build circuit.**

# FAX / MODEM PROTECTOR

TOM PETRUZZELLIS

SHIELD YOUR MODEM, FAX, OR ANSWERING machine against harmful transients arriving over the phone line by building this fast-acting Modem/Fax Protector. Then you'll be able to relax when electric storms bear down on your home or office. It's an easy, inexpensive project, and low-cost insurance for your expensive telephone-dependent equipment.

Even people who plug their computers and entertainment electronics into power-line surge protectors (and wouldn't dream of leaving them unprotected) are likely to forget about protecting modems, faxes

and answering machines from transients arriving over the phone line. Then comes the first thunder storm of the season. Before they remember to do anything about it, the innards of that equipment could disappear in a puff of smoke.

You could, of course, disconnect your telephone gadgets with a switch when they're not in use. But will you remember to do it in time? Needless to say, the switch won't help much if the devices are running when the lightning starts to flash.

#### Telephone electrical values

When a telephone handset is

"on the hook" there is 48 volts DC across the two wires designated "tip" and "ring." The green tip wire is at ground potential, or zero volts, and the red ring wire is at negative 48 volts. Approximately 21 to 35 milliamperes of current flows in this condition.

When the handset is picked up, phone-line voltage drops to 6 volts DC. The 20- or 30-Hz telephone-ringing signal can be from about 100 volts to about 120 volts AC. It is superimposed across the normal 48-volt DC signal. That "ringing" voltage determines the voltage ratings of the protective devices.

## Telephone protection

Although the effects of lightning are well known, many people believe that only a direct strike on a nearby phone or power line will cause damage. However, most damage to electronic equipment is caused by voltages induced in those conductors by direct strikes elsewhere. Harmful voltages can be caused by strikes as far as 15 miles away!

Telephone circuits generally have resistive elements in each wire to protect the telephone handsets from transient spikes in excess of about 500 volts. However, this rather crude passive protection is inadequate for protecting more vulnerable electronics.

Spark-gap tubes or surge voltage protectors (SVP) have been used for many years to protect electronic circuits from manmade and natural surges arriving over either power or phone lines. They provide low-resistance paths for excessive voltage transients but appear open to normal voltages. The devices are hermetically sealed gas-discharge tubes. Typically made of ceramic with properly spaced electrodes, they are filled with a rare gas.

The main purpose of the SVP is to provide a conductive path for unwanted and excessive transients, thereby preventing the transient energy and associated voltages from damaging equipment and components—and harming people. They are designed to switch current at a pre-established breakdown voltage.

The breakdown voltage causes the internal gas to ionize and change from a non-conducting to a conducting state, thus permitting an arc to form and short the connected wires to ground. During conduction, the SVP can momentarily carry high currents. After the voltage transient has been discharged, the gas deionizes and the SVP is ready for another voltage transient.

The SVP is bipolar and has a symmetrical characteristic. In the restored or extinguished condition, it causes very little

 


FIG. 1—MODEM/FAX PROTECTOR packaged in a standard telephone jack box.

loss because of its high impedance. This characteristic contrasts with those of transient absorption Zener diodes and metal-oxide varistors that exhibit leakage. However, both of those devices have faster response times than SVP's.

The metal-oxide varistor (MOV or SIOV) has also been used to protect electronics connected to telephone lines. It is made from finely powdered zinc oxide mixed with binders and pressed into a disk. After firing, the disk becomes a matrix of conductive zinc-oxide grains separated by highly resistive boundaries. This property gives them a symmetrical electrical characteristic similar to the

SVP (or two back-to-back Zener diodes).

However, the MOV's breakdown time is too slow to protect connected electronics against the fastest voltage spikes caused by lightning. As a result, faster Zener diodes and SVP's have been combined in our Modem/Fax Protector.

### How the protector works

The Modem/Fax Protector (Fig. 1) is shown schematically in Fig. 2. It has a typical response time of about 10 nanoseconds—fast enough to protect your equipment against the speediest voltage spikes. Zener diodes D1 and D2 are connected back-to-back in parallel with



surge-voltage protector SVP1 between the ring and the PC board earth ground connection. Similarly, Zener diodes D3 and D4 are connected in parallel with SVP2 between the tip wire and the PC board earth ground. The SVP's are rated for a nominal DC voltage of 230 volts with breakdown voltage from 195 to 265 volts DC.

The Zener diodes break down at 180 volts DC within about 10 nanoseconds to protect the telephone circuits from the fastest initial voltage spikes, and then the SVP's ionize to ground the overcurrent. Note that the circuit has no batteries; all it really needs to protect your equipment is an effective ground.

### Construction

The prototype Modem/Fax Protector was built on a small square PC board measuring 1½ inches on a side (see Fig. 3). However, point-to-point wiring techniques can also be used. Note that the board has a hole drilled through it for the screw that clamps the enclosure together and provides the ground connection.

Refer to parts-placement diagram, Fig. 4. Install all of the components as shown, observing the polarities of the Zener diodes. Solder all components in position and trim excess leads.

Obtain a small modular plastic phone jack cover with an included jack. The jack should have a short section of 4-wire telephone cable attached. Cut off the black and yellow wires and connect the red ring and green tip wire pigtailed within the box as shown in Fig. 5. Cut a bottom plate from sheet mica, phenolic or other suitable thin but rigid insulating material slightly larger (about 1/16-inch) than the outer dimensions of the jack box. Carefully mark the location on the cover plate for a hole to accommodate the central screw so that it is opposite the hole in the jack box, and drill a hole of the same diameter through the cover.

Determine a suitable length for the four-wire telephone cable between your telephone outlet

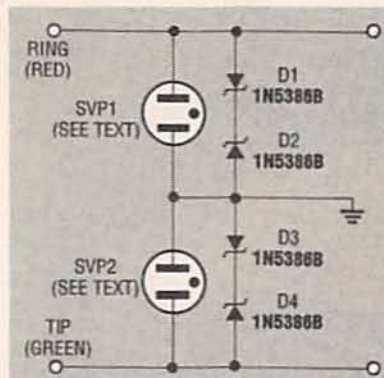


FIG. 2—MODEM/FAX PROTECTOR schematic showing Zener diodes in parallel with surge voltage protectors.

 


FIG. 3—MODEM/FAX PROTECTOR circuit board assembly shown actual size.


 


FIG. 4—PARTS-ASSEMBLY DIAGRAM for the Modem/Fax Protector circuit board.

 

FOIL PATTERN for the modem/fax protector.

or junction box and the Modem/Fax Protector, and attach a plug to one end of that cable. Carefully form a hole in the side wall of the jack box, as shown in Fig. 5, large enough to permit the bare end of the telephone cable

to be pulled through a distance of 3 to 4 inches. Clamp the cable with a plastic cable tie.

Strip the cable jacket back to about 1/8 inch from the cable tie, select out the red ring wire and green tip wire and strip their ends, and cut off the yellow and black wires close to the cable tie. Then strip the ends of the red and green wires from the jack. Solder both red and green wires to the circuit board, as shown in Fig. 4. Cut a short length of insulated 14 or 16 AWG wire, strip both ends, and solder one end to the ground pad on the PC board.

Apply four drops of silicone RTV adhesive to the inside of the jack box as shown, align the hole in the circuit board over the hole in the jack box, and bed the board down in the adhesive. Allow sufficient time for the adhesive to set up before proceeding. Determine a suitable length for a 14 to 16 AWG solid-copper ground wire based on the proximity of your telephone apparatus to a suitable location for a ground rod (to be discussed later).

Form a loop in one end of the heavy ground wire to accommodate the central screw in the Modem/Fax Protector. Then insert the screw through the loop in the ground wire, jack box, and circuit board. Tightly wrap the bare copper end of the ground wire on the circuit board several times around the screw to complete the ground connection. Then apply solder to the outside of the turns.

Plug your modem or fax into the jack, and plug the length of cable into your telephone wall outlet. The ring and tip wires of the telephone line must remain consistent throughout. The tip lead must be positive with respect to the ring lead.

After making sure that all connections have been made correctly, apply a thin layer of RTV adhesive to the rim of the jack box, assemble the cover over the screw, and clamp it in position with a washer and two nuts, as shown in Fig. 5.

### Good grounding

The necessity for a good

 


FIG. 5—MODEM/FAX PROTECTOR ASSEMBLY. Note the location of the hole formed for the 4-wire telephone cable. Only the red and green wires are used; the others are cut off near the cable clamp. The assembly is set on four spots of RTV adhesive, and the cover is held on with the central screw, nuts and washer.

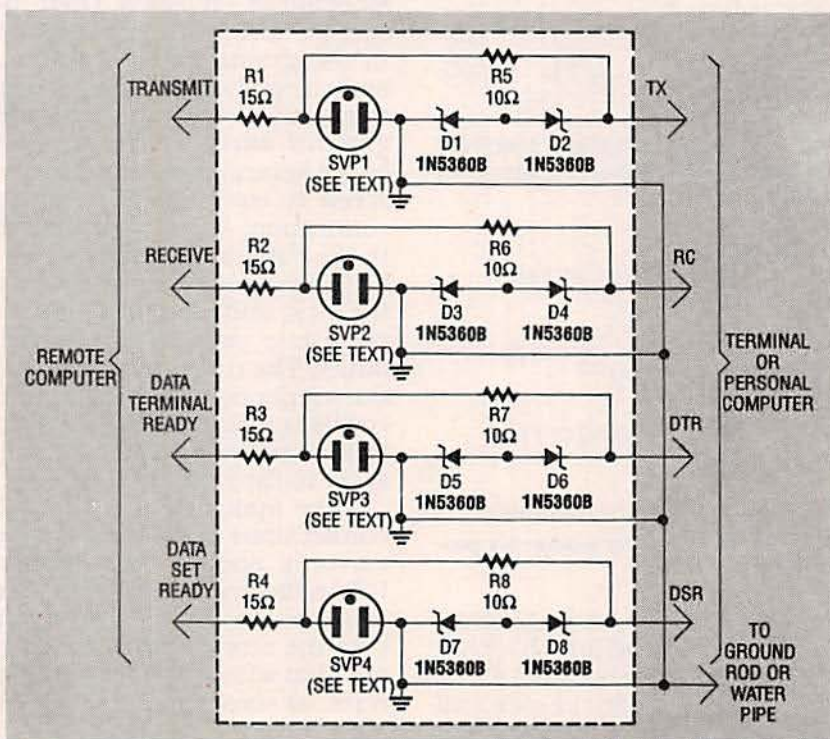


FIG. 6—VARIATION OF THE MODEM/FAX PROTECTOR for use in telephone line connections between PC or terminal and larger distant computer.

ground in protective circuits cannot be overstated; a bad ground is no ground at all! The most effective ground is achieved with a metal rod, preferably copper, at least four feet long, driven into moist soil. Connect the ground rod to the Modem/Fax Protector with the other end of the insulated solid copper ground wire. It can be led to the ground strap through a window opening or a hole drilled through the wall. Suitable grounding rods with wire-connecting clamps are available from electronics supply stores.

The next best grounding

#### PARTS LIST

##### Surge voltage protector

SVP1, SVP2—gas surge arrester, 250-volt, CG-230L (C.P. Claire) or equivalent

##### Semiconductors

D1–D4—1N5386B Zener diode, 180-volt, 5-watt.


**Miscellaneous:** PC board, modular plastic phone jack box with jack, phenolic or micarta cover, length of 4-wire telephone cable, modular phone jack, length of insulated 14 to 16 AWG solid copper wire, copper ground rod (at least 4 feet long), nuts, bolt, washer, silicone RTV adhesive, solder.

method is to connect the 14 to 16 AWG wire to a cold-water pipe. The third, and least satisfactory method (not recommended), is to connect the ground wire to the ground of the 120-volt AC outlet. (This ground can actually be at a higher potential than true earth ground by many millivolts!)

#### Variations on a theme

Figure 6 shows the Modem/Fax Protector concept applied to the protection of remote computer terminals or personal computers connected to a larger computer over long-distance phone lines. The schematic shows a typical four-channel protective circuit.

 The SVP's and transient absorption Zener diodes in Fig. 6 differ from those in the Modem/Fax Protector. The SVP's are C.P. Claire C675L's or equivalent, and the Zener diodes are 1N5360B units. Resistors R1 through R4 are 2-watt wire-wound units, and resistors R5 through R8 are 1/2-watt. R-E



# INRUSH CURRENT LIMITER

**Protect sensitive electronics with an easy-to-build inrush-current limiter that can be embedded in host equipment or be a stand-alone unit.**

THE INRUSH-CURRENT LIMITER described here can protect sensitive line-powered electronics against normal current surges that occur when that circuitry is powered up. The limiter gives a "soft start," to any product or system it protects, and it can be expected to lengthen the operating life and improve the reliability of the host. A thermistor and relay protect against normal "turn-on" overcurrent, and a metal-oxide varistor protects against unwanted overvoltages and overcurrents occurring after startup.

Our inrush-current limiter, shown packaged in an enclosure in Fig. 1, can protect any equipment operated from 120-volt, 60-Hz AC. It can also protect non-electronic circuits such as lighting networks and appliances, provided that they do not include motors. (Many appliance motors depend on surge current for starting.) The circuit can be modified for protection at higher or lower AC voltages or DC voltages.

## Current limiting

Most power supplies for electronic equipment that are em-

 


FIG. 1—INRUSH-CURRENT LIMITER circuit as a stand-alone component.

 


FIG. 2—SIMPLIFIED SCHEMATIC for a linear power supply with a full-wave rectifier and capacitor filter.

bedded within the enclosure (typically sharing a PC board with other circuitry) are conventional linear circuits. As

shown in Fig. 2, they consist of a transformer, bridge rectifier circuit, and one or more filter capacitors. When AC power is applied to such equipment, there is no charge on its capacitors, and the circuit components present an extremely low impedance to the line voltage.

As a result, a large inrush current surge with a fast rise time occurs, and it decays exponentially only as the filter capacitors charge. The peak inrush current is orders of magnitude greater than the circuit's steady state current. It is limited primarily by the short circuit characteristics of the power transformer and rectifier, which are determined by their internal resistance and inductance values and the wiring, as shown in Fig. 3.

An inrush-current limiter, as its name implies, limits inrush current and allows the voltage to rise gradually across the protected circuit. The limiter was designed for high-power stereo amplifiers to avoid the excessive current surges that occur at turn-on. The current drain of large stereo amplifiers is high enough to dim the lights in an

average home when it is turned on.

Electronic-equipment and power-supply manufacturers typically limit inrush current by placing a momentary switching device with a fixed resistance at the power input terminal of the circuitry to be protected. After a predetermined time interval, relay contacts close, shorting out the input resistor so that full voltage is applied to the load.

Our inrush-current limiter circuit takes that conventional approach one step further. The fixed-value protective resistor is replaced by a temperature-variable resistor whose resistance value declines with increasing inrush current. A negative temperature-coefficient (NTC) thermistor optimized for inrush-current protection, its manufacturer refers to it as an *inrush-current limiter*.

A typical temperature vs. resistance curve for an inrush current limiter device is shown in Fig. 4. These devices are widely used in AC/DC switching power supplies. The unit specified for this project has a resistance of 120 ohms  $\pm$  25 % at 25°C, a maximum steady state current of 2 amperes, and an approximate resistance of 1.18 ohms at maximum current.

### Inrush-current limiting

Refer to the simplified block diagram, Fig. 5. The hot side of the AC line is fed through the inrush-current limiter (shown as a resistor with the letter "T.") Actual resistance change depends on the magnitude and duration of the current drawn. With a nominal resistance of 120 ohms, the maximum instantaneous current through any connected circuit will be limited to 120 volts/120 ohms = 1.0 ampere. (The current drawn will be less than the theoretical value because of the impedance of other components.)

At the end of a preset elapsed time after power is applied, a relay is actuated and it shorts out thermistor R9; that applies full power to the protected circuitry. The time delay is adjustable and determined by the value of a single resistor or po-

 


FIG. 3—EFFECTIVE RESISTANCE and inductance of transformer primary and secondary are represented by R1, L1 and R2, L2, respectively; R3 and R4 are the effective resistances of the rectifier bridge and circuit wiring, respectively. The dotted line across filter capacitor C1 represents zero resistance at power turn-on.

 


FIG. 4—INRUSH-CURRENT LIMITER device shows negative-temperature coefficient (NTC) characteristics. A thermistor optimized for circuit protection, its resistance declines as temperature increases due to current flow.

 


FIG. 5—BLOCK DIAGRAM OF INRUSH-current limiter circuit shows relay power supply and an inrush-current limiter component to protect against current surges at turn-on.

tentiometer; it can range from less than a second to more than a minute.

### How the limiter works

The schematic of the inrush-current limiter circuit is given in Fig. 6. The 24-volt DC for the timer circuitry and relay are de-

rived from a regulated power supply made up of resistor R1, capacitors C1 and C2, and diodes D1 to D3. The 120-volt input voltage is dropped primarily by C1, and applied to the two series-connected Zener diodes, D1 and D2.

When the polarity of the hot (upper) AC line is positive with respect to the neutral (bottom) AC line, a positive voltage is developed across the Zener diodes. That voltage charges filter capacitor C2 through diode D3. Resistor R1 and parallel metal-oxide varistor MOV1 limit the peak current in the circuit. Resistor R2 discharges C1 and resistor R3 discharges the filter and timing capacitors when power is removed, readying the circuit for immediate restart.

The relay power supply in Fig. 6 is popular in isolated electronics products where only small DC currents are needed to power circuitry. It eliminates the bulk and expense of a power transformer. However, appropriate safeguards must be taken because the supply is not isolated from the AC line. The timing circuit consists of resistors R4 to R7, capacitors C3, diode D4, transistors Q1 and Q2, and relay RY1. Timing capacitor C3 charges through timing resistor R4. (With a value of 150 K, the time delay will be 11 seconds.)

The PC board provides three holes for 1 megohm board-mounted potentiometer R9. Its adjustment will give a continuous range of time delays from about 1 second to 60 seconds. As an alternative, Table 1 lists the values of resistor R4 needed to obtain time delays from 1.5 to 180 seconds in discrete increments. The time delays given in the table can vary because of the wide tolerances of electrolytic capacitors.

When the voltage on C3 reaches the 12-volt breakdown threshold of Zener diode D4, it conducts and applies base drive to turn on NPN Darlington transistor Q1. When Q1 conducts, its collector voltage decreases, turning on PNP Darlington transistor Q2, whose collector current actuates relay RY1. The

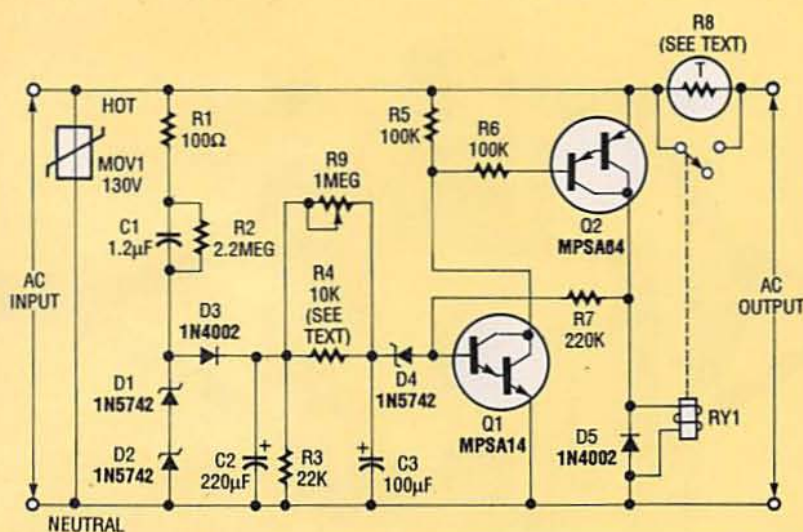


FIG. 6—SCHEMATIC OF INRUSH CURRENT LIMITER. Note that Q1 is an NPN Darlington and Q2 is a PNP Darlington. MOV1 is a metal-oxide varistor and R8 is an NTC thermistor for limiting inrush current.

relay's normally open contacts are connected across the inrush current limiting device. When closed, the contacts apply full power to any connected load. Resistor R7 provides positive feedback to Q1's base, ensuring positive turn-on of the relay.

Diode D5 protects the circuit from the inductive "kickback" of the relay coil when it is de-energized. The resistance of the relay's coil must be at least 1.3 K for effective relay operation. The metal-oxide varistor MOV1 will protect the load against voltage spikes and transients, but it is not a requirement for the operation of this circuit. It has symmetrical bidirectional "break-down" characteristics similar to those of back-to-back-connected Zener diodes.

#### Construction

All of the circuitry fits on a PC board measuring 2.5 x 2.5 inches. However, you might want to make the PC board's outer dimensions larger or smaller. If you plan to mount the circuit in a case, the board size and the hold-down screw spacing will depend on the case selected. The complete circuit assembly can also be mounted within the enclosure of its host equipment with mounting holes and insulating standoffs, if desired.

The PC board for this project


 


FIG. 7—PARTS-PLACEMENT DIAGRAM for the inrush-current limiter circuit.

 

FOIL FOR INRUSH-CURRENT LIMITER PC board.

is simple enough for an amateur to make, so its foil pattern is included here. However, because there are no critical components on the board, the

components can be assembled on prepunched insulating board and connected by point-to-point wiring. Before doing any assembly work, drill the four corner holes in the board for the screws to mount the board to the case or inside the host's enclosure with standoffs.

Figure 7 is the parts-placement diagram. Install the resistors, capacitors and diodes first, observing the proper polarities for the capacitors and diodes. If you elect not to use the 1 megohm potentiometer R9, the value of R4 should be 150 K ohms rather than the 10 K shown on Fig. 6, and a jumper should be installed across two of the holes as shown. (Table 1 gives values of R4 for specific time delays.) After all the components are assembled on the board (see Fig. 8), solder them, and trim all excess leads. Re-check your work, carefully examining the circuit for shorts before continuing with the checkout.

#### Checkout procedure

**Warning:** This is a line-operated device, so perform all testing and troubleshooting with a line-isolation transformer. Never operate the circuit outside of an insulating housing and never make adjustments or any kind of modifications to it when it is directly connected to the AC line.

An isolation transformer is recommended for testing this circuit. If you cannot obtain a commercial unit, you can build one by connecting the secondaries of two identical transformers back-to-back as shown in

TABLE 1  
TIME DELAY VS. RESISTANCE

Resistance (R4) (ohms)	Time delay (seconds)
22 K	1.5
47 K	3.0
68 K	5.0
100 K	7.0
150 K	11.0
220 K	17.0
470 K	40.0
1.0 MEG	80.0
2.2 MEG	180.0

Fig. 9. (It can also be used to test other transformerless electronic circuits.) The 120-volt line is stepped down, and then stepped back up to 120 volts. Use only transformers with the same secondary voltages, and do not exceed the current or power ratings of each of the transformers.

With no power applied to the circuit, perform the following resistance checks:

- Measure the resistance between the AC inputs, the hot AC line connected to R1, and the neutral AC line connected to the anode of D2. The readings should be greater than 10 megohms—anything less could indicate a problem.

#### PARTS LIST

All resistors are 1/4-watt, 5%, unless otherwise stated

- R1—100 ohms, 2 watt, 5%, metal-oxide
- R2—2,200,000 ohms
- R3—22,000 ohms
- R4—10,000 ohms (see text)
- R5, R6—100,000 ohms
- R7—220,000 ohms
- R8—120 ohms inrush-current limiter (NTC thermistor) 2-ampere (Keystone) CL-90 or equivalent
- R9—1,000,000 ohms potentiometer, 3-pin, PC board-mount, insulated knob.

#### Capacitors

- C1—1.2  $\mu$ F, 250-volt, polyester-film
- C2—220  $\mu$ F, 35-volt, aluminum electrolytic
- C3—100  $\mu$ F, 16-volt, aluminum electrolytic

#### Semiconductors

- D1, D2, D4—1N5742, Zener diode, 12-volt, 1-watt
- D3, D5—1N4002, 1 ampere, 100 peak volts
- Q1—MPSA14, NPN Darlington transistor, (National Semiconductor) or equivalent
- Q2—MPSA64 PNP Darlington transistor, (National Semiconductor) or equivalent

#### Other components

- MOV1—metal-oxide varistor, 130-volt AC, (Panasonic) 20K201U, or equivalent
- RY1—SPST relay, coil: 24-V, contact: 5 A, 250-V AC, 30-V DC, coil resistance 1300 ohms, PC-mount, (Omron) G5L-112P-Ps or equivalent
- S1—toggle or rocker switch, panel-mounted, 350-volt, 3 amp

**Miscellaneous:** circuit board, panel-mounted receptacle (three-prong), length of 3-conductor power cord 18 AWG with 3-prong plug, four 1/4-inch insulated standoffs (see text), insulated case with cover, cable grommet, screws as needed, and solder.

 


FIG. 8—ASSEMBLED INRUSH-CURRENT LIMITER circuit.

 


FIG. 9—SCHEMATIC FOR AN ISOLATION transformer to be used in testing the circuit. All turns ratios must be equal.

- Measure the resistance between the same end of R1 and the end of R2 connected to D1. The readings should be 2.2 megohms. Those measurements assure that there are no shorts or low resistances across the AC line.

- Connect the circuit to the isolation transformer and apply power. If the circuit is operating properly, you should hear the faint click of the relay contacts closing after the appropriate time delay.

- Check for proper operation of the power supply by measuring the voltage across filter capacitor C2. The reading should be about 22 volts DC when the relay is energized.

When testing and experimenting with loads connected to the inrush-current limiter, allow several minutes for the circuit to cool down to room temperatures and the nominal resistance values to be restored. The allowed time should de-

pend on the magnitude and duration of the current drawn through the device. In normal operation, allow about a minute after power is removed for timing capacitor C3 to discharge before initiating a new time delay sequence.

#### Installation

The inrush current limiter can be installed within the enclosure of the host equipment. Connect the circuit to the AC line after the host equipment power switch and preferably after the line fuse or circuit breaker. Install the circuit so that the hot leg of the AC line is connected to the surge limiter, as shown in Fig. 6. Cut the AC line to the host and install the circuit in series, as shown in Fig. 8. Be sure the circuit board for the inrush-current limiter and all components are insulated from the equipment's chassis and all other components with insulated standoffs.

As an alternative, install the inrush-current limiter in a suitable insulated case with a line cord, power receptacle, and ON-OFF power switch as shown in Fig. 9. The prototype case measured 4 $\frac{3}{8}$   $\times$  3 $\frac{1}{4}$   $\times$  1 $\frac{1}{2}$  inches deep.

It might be necessary to cut down the four standoff posts within the case to accommodate

*continued on page 76*

# LIGHT BEAM COMMUNICATOR

*Build the Air Hop,  
an inexpensive system that  
communicates with light.*

RODNEY A. KREUTER

IMAGINE YOU WERE CHALLENGED TO build a device that could send an optical audio signal—with a bandwidth of 300 to 3000 Hertz—as far as possible. To make the contest as fair as possible, the rules would require that only commonly available parts could be used. Also, because optics would play a large role in determining the range of such a device, no optics with a collection area greater than seven square inches could be used.

A dozen years ago, the author lost just such a contest by achieving a communications distance of a little over two and a half miles. The winning entry achieved a distance of 6 miles!

The optical communications system presented here is a somewhat modified version of the author's original Air Hop. The circuits have been redesigned in order to use common parts and provide a decent link at a reasonable cost. The unit has an output power of about 10 milliwatts peak and 5 milliwatts average. It uses frequency modulation on a 50-kilohertz carrier and has a bandwidth of 300–3000 Hertz. Without optics, the Air Hop can communicate about 40 feet—with 3-inch diameter optics (a magnifying glass), the range is increased to over a mile.

Air Hop can be used as a simple point-to-point audio communications system or to transmit digital data. Since its bandwidth is the same as a phone line, modems can be used to send and receive digital data. It can also be used as a link for a remote control such as that used in a TV receiver, perhaps with a tone encoder/decoder combination. A remote link to a repeater or a long-distance "broken beam" security system can also be made. Whether you need a link from a house to a barn or a short jump across the commotion of Wall Street, Air Hop can do it.

## Electro optics

Before we get into the design and construction of the Air Hop, let's explain some optical terms.

**PIN Diode.** A photosensitive di-



ode with a response time of a few nanoseconds. It can be used in a photoconductive mode where the current through it is a function of light, or in a photovoltaic mode where the voltage across it is a function of light (see Fig. 1).

**Phototransistor.** A transistor whose base current is a function of light. The collector current is the base current times the gain of the device. Response time is a few microseconds.

**Photodarlington.** Two transistors in the same package connected in a Darlington configuration. The first transistor is a phototransistor and the second is an ordinary transistor. Response time is tens to hundreds of microseconds.

**Detector area.** The area (in square inches or millimeters) of the light-gathering detector. Most PIN diodes have a plastic case that acts as a simple lens and provides a collection area of 0.01 to 0.025 square inches. This area is important when you're calculating lens gain.

**Inverse square law.** This is the "killer" in nearly all communications systems. Very simply stated, it means that if you increase the distance between the transmitter and the receiver, the signal strength will drop in proportion to the square of the distance. For example, if you receive 9 microwatts of power when the distance between the transmitter and receiver is ten feet, you will receive only 1 microwatt of power if you increase the distance to thirty feet.

**Transimpedance amplifier.** An amplifier with a very low input impedance. Sometimes called current-to-voltage converters, these special amplifiers are often used in optical systems because their low impedance load will ensure maximum current from a photodiode. They can provide a bandwidth up to a few hundred megahertz.

**Lens gain.** The ratio of the lens area to the detector area. Since the area of a lens is larger than the area of the detector, more light is gathered by the lens. Lens losses and focusing errors (which together should be about 15%) must be included in

 


FIG. 1—A PHOTOSENSITIVE PIN diode has a response time of just a few nanoseconds.

 


FIG. 2—THE LIGHT FROM AN LED diverges or spreads out as it leaves the LED. A lens will then collimate the light so that it travels in parallel beams.

 


FIG. 3—THE *f* NUMBER or lens speed is the ratio of the focal length to the diameter. You can think of this as an optical acceptance angle.

a rigorous calculation of lens gain.

**Infrared.** The region of the light spectrum next to the color red (about 800 nanometers). Most infrared LED's emit at either 880 nanometers or 940 nanometers. Most silicon detectors have their maximum response at about 900 nanometers. Infrared is used because most red (visible light) LED's have trouble producing a half a milliwatt of power, while many IR LED's have an output of 10 milliwatts or more.

**Collimate.** To direct in a straight line. When light from a source travels in parallel beams

instead of a divergent cone, it is said to be collimated. Although you can't form a truly collimated beam, the lens on the transmitter attempts to do that (see Fig. 2).

**Divergence.** The "spreading out" of an optical beam. In other words, a divergent beam is the opposite of a collimated beam. All optical beams diverge, some more than others. If you could form a beam with zero divergence (you can't), it would not obey the inverse square law. In other words, you could send your beam an infinite distance because the energy wouldn't spread out. Laser beams have small divergence compared with other light sources. Spot lights are built to have a small amount of divergence, whereas flood lights are built to have a great deal of divergence (see Fig. 2).

**Responsivity.** A measure of the relationship between the optical and the electrical signal of a detector. A rule of thumb for PIN diodes is 0.4 to 0.6 amps per watt. This means that if 1 milliwatt of light strikes a PIN diode, a current of 0.4 to 0.6 milliamps will flow through the diode. To put that in perspective, Air Hop will work at levels of about 100 picoamps of current or about 200 picowatts of optical power.

**AC and DC light.** If you pulse an LED on and off it becomes an AC-light source. If you simply apply DC though it, it becomes a DC-light source. This concept is important because most light sources contain some AC and some DC light. Normal tungsten-filament light bulbs contain a lot of DC and some AC light (because of the thermal time constant of a hot filament). The sun contains a lot of DC and a lot of AC. Fluorescent lights contain some DC and a lot of AC. The only reason that this is important is that if you build a DC-coupled optical receiver and operate it outdoors where there is a lot of sunlight, the receiver can easily "saturate" and your AC signal will not be amplified correctly. Some kind of "light shield," such as those that are used on some



camera lenses, will help. That's why the Air Hop uses an AC-coupled detector.

**f number or lens speed.** In lenses, the ratio of the focal length to the diameter is called the "f" number ( $f = fl/d$ ). The smaller the number, the "faster" and more expensive the lens. It is convenient to think of this as an optical "acceptance" angle (see Fig. 3). This will be important in choosing the transmitter's collimating lens. In cameras, where the focal length is fixed, a lens with a larger diameter than another lens has a smaller "f" number, and is said to be faster. That's because the larger lens gathers more light and the shutter can be set to a faster speed than the smaller lens. Table 1 shows f numbers vs. acceptance angles.

**Thermal noise.** Although thermal noise is not applicable to optical devices such as lenses, the electronic performance of your optical system will be limited by thermal noise. Thermal noise is caused in an electrical device by the random movement of molecules. The thermal current noise ( $i_N$ ) of a resistor is given by:

$$(i_N)^2 = 4KT/B$$

where

K = Boltzmann's constant ( $1.38 \times 10^{-23}$ )

T = temperature in Kelvin (300)

B = bandwidth in Hertz

R = resistance in ohms

A 300K resistor operated at near room temperature in a receiver with a bandwidth of 20 kilohertz will have a thermal noise current of 33 picoamps

Although 33 picoamps might not sound like a lot of current, the noise it will cause at the output of the transimpedance amplifier will be about 10 microvolts (RMS). Converting to peak-to-peak noise gives about 60 microvolts peak-to-peak.

In the Air Hop, the only amplifier between the transimpedance amplifier and the comparator is a differential amplifier with a gain of about 50. That amplifies the 60 microvolts of noise and produces about 3 millivolts of noise at the output of the optical amplifier. Actual measurements showed 5

TABLE 1  
f NUMBER VERSUS  
ACCEPTANCE ANGLE

f	Angle (in degrees)
0.5	90
0.75	67.4
1.0	53.2
1.5	36.8
2.0	28
2.5	22.6
3.0	19
3.5	16.2
4.0	14.2

#### FM TRANSMITTER PARTS LIST

All resistors are 1/4-watt, 5%.

R1, R5, R9, R15, R16—1000 ohms

R2—22,000 ohms

R3—10,000 ohms

R4—1000 ohms, potentiometer

R6—100 ohms

R7—5600 ohms

R8, R13—2200 ohms

R10—470 ohms

R11—50,000 ohms, potentiometer

R12—33,000 ohms

R14—15,000 ohms

R17, R18—22 ohms (see text)

#### Capacitors

C1—C3, C6—1  $\mu$ F, 16 volts, electrolytic

C4—100  $\mu$ F, 16 volts, electrolytic

C5, C9—10  $\mu$ F, 16 volts, electrolytic

C7—0.001  $\mu$ F, ceramic

C8, C10, C11—0.01  $\mu$ F, ceramic

#### Semiconductors

IC1—NE555 timer

Q1—Q4—2N3904 NPN transistor

LED1—LED4—IR LED (Optek OP293A

880nm, Optek OP295A 880nm narrow beam, Lytron 940nm, see text)

#### Other components

MIC1—electret microphone

Miscellaneous: 4 "AA" batteries and

holder, PC board, PVC pipe and plastic

disks, hardware, wire, solder, etc.

millivolts of noise. That is reasonable because there are other noise-producing devices in the system such as the current noise of the first transistor. Although every transistor produces some noise, the first one produces more because of its higher signal amplification.

One reason it's important to present equations like this is that they give us insight into system improvement. If there were no noise, virtually unlimited distances could be achieved. However, when the strength of the signal is less than the noise, we're out of luck. We can control temperature to some extent, and the

equation shows that at a lower temperature, the noise is lower. But lowering the temperature of the transimpedance resistor even by 100 degrees Kelvin will decrease the noise power only by a factor of about 1.2.

If a system requires only a small amount of bandwidth, say a few hertz, as in a television remote control, we could decrease the bandwidth from 20 kilohertz to 20 Hertz and decrease the noise by a factor of about 30. Even with the inverse square law working against us, that would improve the range by a factor of about 5. Such a bandwidth reduction would require a good tunable filter, but it certainly can be done. Of course, audio signals sent over a link with a 20-Hertz bandwidth wouldn't be recognizable as audio. It would, however, permit Morse-code communication.

**Photodetector.** Any device that can convert light into an electrical signal. Phototransistors, photo SCR's, phototriacs photocells, solar cells, and photodiodes are all examples. Even photoresistors and thermocouples can be loosely considered as forms of photodetectors.

Phototransistors and photodarlington detectors are often used to detect light. Both work well if you don't require high speed. Typical phototransistor rise and falls times are 1 to 5 microseconds; for Darlington's they are hundreds of microseconds. In electronics that is equivalent to measuring bandwidth with a stop watch and a calendar, respectively.

The author prefers to use PIN diodes in the photoconductive mode as detectors. Rather than being limited by the gain and bandwidth of a phototransistor, PIN's give us the choice of both by allowing us to design our own amplifiers. PIN diodes are also very "quiet." Their noise is almost unmeasurable.

**LED's.** A light-emitting diode is a semiconductor device that emits light when forward biased. You would think that choosing an LED for a system such as this would be a simple matter, but it's not. Characteristics such as power output,

wavelength, speed, and beam angle all come into play.

The first consideration is usually the power output. However, if you can't get the power into your lens, it's simply wasted, and if it's at the wrong wavelength, your detector won't see it.

Wavelength is important. The most widely used wavelengths for infrared devices are 880 nanometers and 940 nanometers. The first choice is to find a detector and emitter that match. We used 940 nanometers, which is further into the infrared than 880. Many detectors made for 940 nanometers have a built-in visible-light filter. Filters are not often put on the 880-nanometer devices because that wavelength is near the visible spectrum and such a narrow filter would be difficult to produce in large quantities.

If you wish to produce a hundred thousand Air Hop systems with optics, you would want to buy emitters with wide but uniform beams. Then you would have a custom lens designed and produced at a small cost in plastic material. That would produce the most uniform beam and would be reproducible in large quantities. In applications such as remote control, you might want to use an emitter or many emitters to "flood" an area. In that case, you would want an emitter with a wide beam.

If, on the other hand, you're just trying to see how far you can "air hop" a signal, you will want something totally different. Narrow beam angles are necessary for efficient coupling to an off-the-shelf lens. As a

matter of fact, choosing the smallest beam angle available will save money when it comes to buying a lens. The smallest easily obtainable beam angle for an LED is about 20 degrees. When a manufacturer specifies that angle, he really means a "half angle" of 20 degrees, or a solid cone of 40 degrees.

The angle also specifies the half-power point. For example, if a manufacturer specifies 5 milliwatts and a beam angle of 20 degrees, that means that if you can capture all of the power contained in a 40-degree cone, you will get 2.5 milliwatts of optical power. In any case, purchase an LED with a small beam angle, as much power as possible, and a reasonable speed.

**Lenses.** Lenses are to the optical world what antennas are to the world of RF. The importance of even simple lenses cannot be over emphasized. If any high-frequency RF engineer could build an antenna with 60 dB of gain for less than ten dollars, we would see a lot of happy RF engineers! Since the optical world deals with very small wavelengths, 60 dB (a gain of 1000) is certainly possible.

Although at first it might be hard to believe, the size of the lens on the receiver is very important, but on the transmitter it isn't. That's because at the receiver you are trying to intercept as much light as possible, so the larger the lens, the better. The

## OPTICAL AMPLIFIER PARTS LIST

All resistors are 1/4-watt, 5%.

- R1—100,000 ohms
- R2—10,000 ohms
- R3, R9, R10, R16, R23—.5,000 ohms
- R4, R5—150,000 ohms
- R6, R17, R24—3300 ohms
- R7, R12—100 ohms
- R8—3900 ohms
- R13, R14—5600 ohms
- R11, R15, R18, R21—4700 ohms
- R19, R22—22 ohms (see text)
- R20—360 ohms

### Capacitors

- C1, C4, C8—10  $\mu$ F, 16 volts, electrolytic
- C2, C5, C9—0.1  $\mu$ F, ceramic
- C3, C12, C14—C16—0.01  $\mu$ F, ceramic
- C6, C7, C11—470 pF, ceramic, 10%
- C10—0.001  $\mu$ F, ceramic, 10%
- C13—100  $\mu$ F, 16 volts, electrolytic

### Semiconductors

- Q1—MPS918 NPN transistor (Motorola)
- Q2—Q6—2N3904 NPN transistor (Q5 and Q6 must be a matched pair, see text)
- D1—PIN diode (Siemens SFH205 940nm usable at 880nm, Panasonic PN323BPA 940 nm, Panasonic PN334PA 880 or 940 nm, see text)

### Other components

- SPKR1—8- to 45-ohm speaker
- Miscellaneous: PC board, wire, solder, etc.

purpose of the lens at the transmitter is to collimate the beam, so any lens with the right "f" number will work.

The "speed" of a lens, also called the "f" number, should be familiar to anyone with photography as a hobby. It's a measure of the angle of acceptance of a lens. On the transmitting end, any light from the LED that

TABLE 2—LENS GAIN

Lens Diameter/Area (inch/sq. inch)	Power Gain (at 0.01 sq. inch)	Distance Improvement (85% lens efficiency)
2/3.14	314	$\times 16$
3/7.07	707	$\times 24$
4/12.6	1260	$\times 33$
6/28.3	2830	$\times 49$

 


FIG. 4—THE AIR HOP IS BUILT FROM THREE MODULES: an FM transmitter, an optical amplifier, and an FM demodulator.

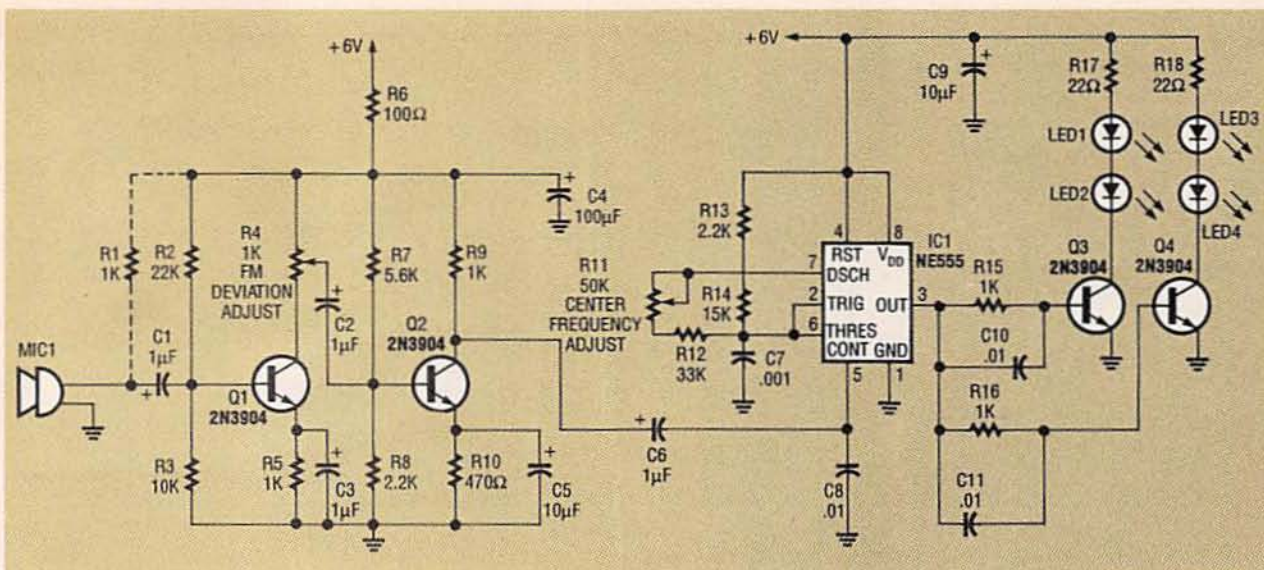


FIG. 5—FM TRANSMITTER MODULE. It provides a microphone amplifier and FM modulator.

#### FM DEMODULATOR PARTS LIST

All resistors are 1/4-watt, 5%.

- R1—100 ohms  
 R2, R3, R6, R11—R13, R16—10,000 ohms  
 R4, R5—100,000 ohms  
 R7—33,000 ohms  
 R8—50,000 ohms, potentiometer  
 R9, R14, R15—68,000 ohms  
 R17—4700 ohms  
 R18—10,000 ohms, potentiometer  
 R19—22,000 ohms  
 R20—470,000 ohms  
 R21—10 ohms

#### Capacitors

- C1, C6, C10, C16—1  $\mu$ F, 16 volts, electrolytic  
 C2, C5, C9, C12—0.1  $\mu$ F, ceramic  
 C3—100  $\mu$ F, 16 volts, electrolytic  
 C4, C7—0.001  $\mu$ F, ceramic, 10%  
 C8—470 pF, ceramic, 10%  
 C11—0.01  $\mu$ F, ceramic  
 C13—100 pF, ceramic  
 C14—4.7  $\mu$ F, 16 volts, electrolytic  
 C15—470  $\mu$ F, 16 volts, electrolytic

#### Semiconductors

- IC1—LM311 or LT1011 comparator  
 IC2—CD4046 phase locked loop  
 IC3—MC34119 audio amplifier (Motorola)  
 Q1—2N3904 NPN transistor  
 Miscellaneous: 9-volt battery and clip,

PC board, blank PC-board material and solder-wick straps for shield (see text), PVC pipe, plastic disks, hardware, wire, solder, etc.

Note: The following items are available from Q-Sat, P.O. Box 110, Boalsburg, PA 16827:

- Complete Air Hop kit including all three PC boards (does not include speaker, 10K volume control, lenses, PVC pipe and batteries), AIRHOP-KIT—\$30.00
  - Transmitter kit including one IR LED and PC board, AHTX-KIT—\$11.00
  - Transmitter PC board only, AHTX-PCB—\$5.00
  - Optical amplifier kit including PIN diode and PC board, AHOPTAMP-KIT—\$12.00
  - Optical amplifier PC board only, AHOPTAMP-PCB—\$6.00
  - FM demodulator kit including PC board (no speaker or 10K volume control), AHFDEMOM-KIT—\$12.00
  - FM demodulator PC board only, AHFDEMOM-PCB—\$6.00
- Add \$3.00 shipping and handling to all orders. Pennsylvania residents must add 6% sales tax. Please allow 3 to 4 weeks for delivery.

doesn't stay within that cone is lost. A 50-milliwatt LED will be of no value if the light "sprays" out at 90 degrees—any light that can't be coupled into the lens is lost.

The gain of a lens is basically the ratio of the area of the lens to the area of the detector. For example, the area of most PIN diodes is about 0.01 square inch. The area of a 2-inch diameter

lens is 3.14 square inches. Therefore, the gain of a 2-inch lens is about 3.14/0.01 or 314. Remember that this amplifier (the lens) consumes no power, has (for our purposes) infinite bandwidth, and adds no noise to the signal. A device of this kind in the electrical world would be nothing short of a miracle.

Table 2 shows the gain for

some different size lenses. The calculations assume that no light is absorbed or reflected by the lens, and the detector is at the exact focal point of the lens. Those assumptions are certainly not true. Even fine-quality camera lenses, which are coated with anti-reflective coatings, do not pass 100 percent of the light. There's plenty of room here for experimentation. Some crude experiments showed about 85% of the theoretical gain.

#### FM transmitter

The Air Hop is built from three modules. The first module is the FM transmitter. Two other modules (the optical amplifier and FM demodulator) comprise the receiver. A block diagram of the system is shown in Fig. 4.

The FM transmitter module, shown in Fig. 5, provides a microphone amplifier (Q1 and Q2) and an FM modulator built from a 555 timer (IC1). There are two adjustments, one for the FM center frequency (R11) and one for the amount of deviation (R4). Resistor R1 is for microphones that require an external power source, such as an electret type. For an external audio source, the input must be limited to a few millivolts.

The output of IC1 (pin 3) is adjusted via R11 so that the frequency is 50 kHz (20 microseconds). The output of the 555 can be frequency modulated by applying the upper trip-point

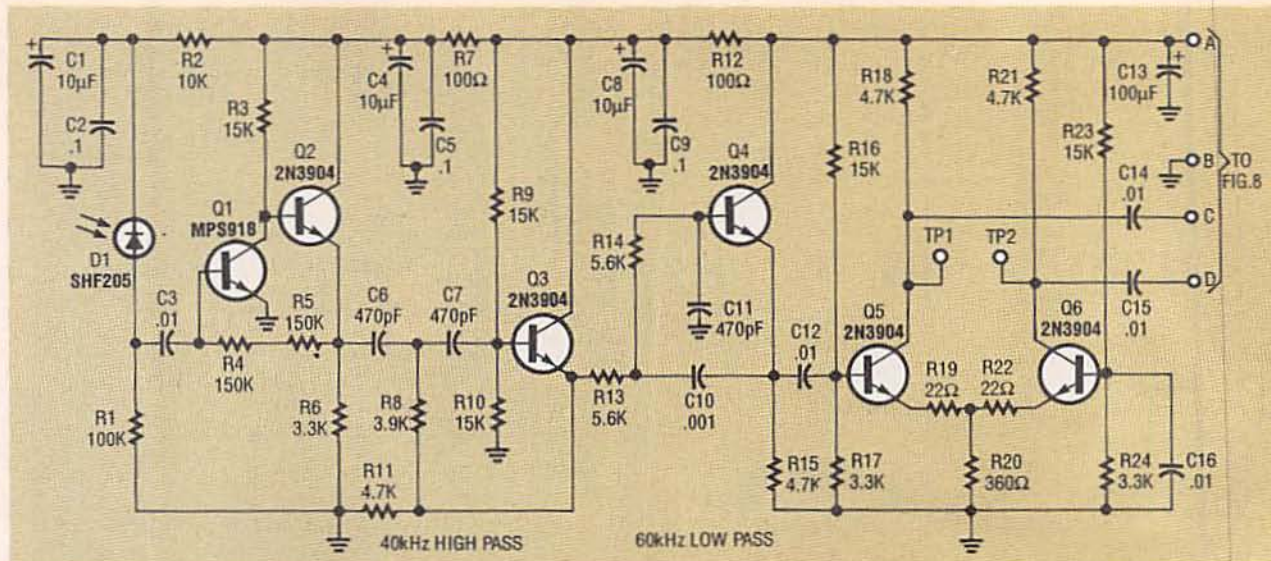


FIG. 6—THE OPTICAL AMPLIFIER MODULE converts the optical signal into an electrical signal, limits its bandwidth, and provides a differential drive to the comparator.

 


FIG. 7—YOU CAN MATCH transistors Q5 and Q6 using this circuit. Any transistor having less than about a volt between the collector and emitter has too much gain. Choose two transistors that have the closest match between collector-to-emitter voltages.

voltage reference to pin 5. Although you cannot sweep the frequency very far, deviations of 10 percent or so can be obtained easily. The FM deviation is a function of the amplitude of the signal applied to pin 5. If a DC voltage is applied to pin 5 and switched on and off, FSK (digital) data will result. Although the output of the 555 could drive a modest LED, transistor drivers are provided to drive multiple LED's.

Current-limiting resistors R17 and R18 are adjusted to limit the current for your particular LED. Currents of up to 200 milliamperes pose no problem for the LED's, but they will drain your batteries quickly. If you're using one LED, values of about 47 ohms will yield about 45 mil-

liamps, average. Systems using two LED's in series will require about 22 ohms for the same current.

The prototype system uses four AA alkaline type batteries for the transmitter power supply. Although they give reasonable life, you may want to use something a little larger, perhaps four D cells.

### Optical amplifier

The purpose of the optical amplifier module, shown in Fig. 6, is to convert the optical signal into an electrical signal, limit its bandwidth (to reduce noise), and to provide a differential drive to the comparator.

The PIN diode detector (D1) is AC coupled to a simple transimpedance amplifier consisting of Q1 and Q2. Even though the signal is AC coupled, the bias for the PIN diode must be DC coupled. That is done through resistors R1 and R2. If Air Hop is used in a high ambient light situation, resistor R1 might have to be reduced in value to prevent DC saturation of the PIN diode. If the DC voltage across R1 is greater than about 3 volts in operation, you should lower the value of R1.

The transimpedance resistors (R4 and R5) set the overall gain of the amplifier. Two resistors in series were used instead of just one because every resistor has some capaci-


tance across it. Using two resistors decreases the capacitance by a factor of two. All you have to do is join the two resistors above the PC board.

The output of the transimpedance amplifier is simply its input current times the transimpedance resistance. That's why it's sometimes called a current-to-voltage converter. As you increase the resistance, the signal increases, but the bandwidth decreases. Since the signal increases directly with the value of the resistance and the noise increases with the square root of the resistance, it makes sense to have the resistance as large as possible—it would, if you still had enough bandwidth. That's why Q1 is a VHF transistor.

Since the center frequency of the signal is at 50 kilohertz, it's desirable to limit the bandwidth of the optical amplifier to reduce the total noise. Transistor Q3 and the surrounding components form a two-pole high-pass filter at about 40 kilohertz. That eliminates such low-frequency noise as the 60-hertz optical noise given off by room lights.

Transistor Q4 and its associated circuitry form a 60-kilohertz low-pass filter. That eliminates high-frequency electrical noise such as that from AM radio stations.

When the low-pass and high-pass filters are cascaded, they form a bandpass filter centered

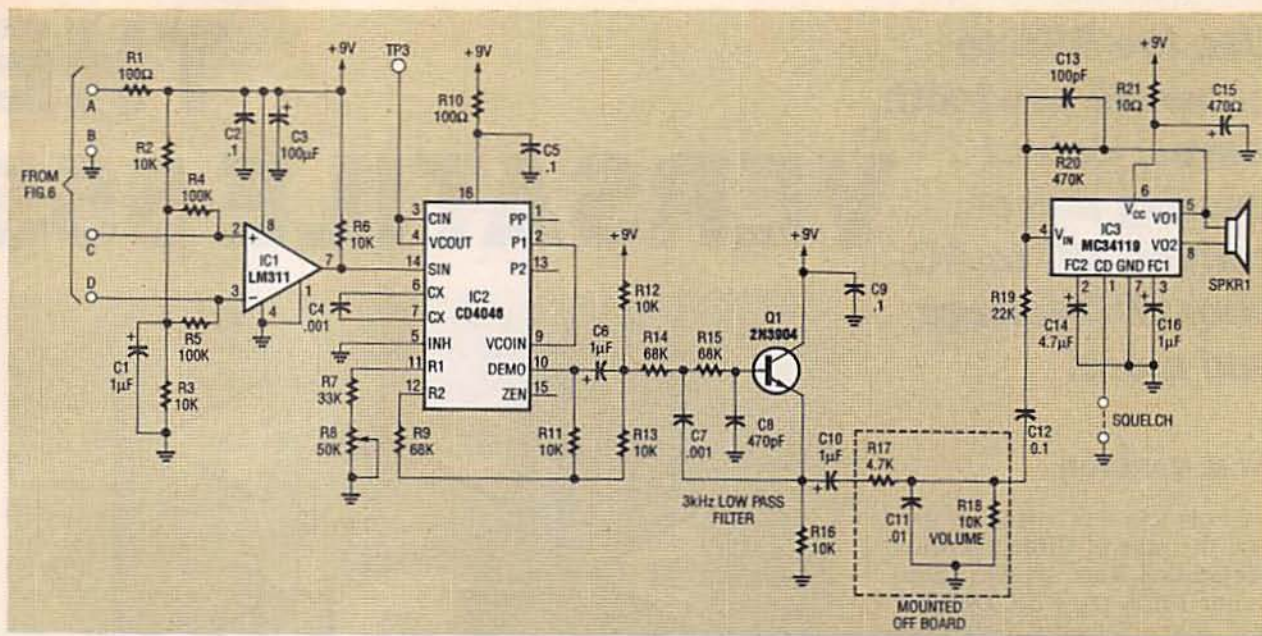

**FIG. 8—FM DEMODULATOR.** An LM311 comparator converts the small analog signal to a digital level for the CD4046 phase-locked loop, which is configured as a first-order FM demodulator.

on 50 kilohertz, with a pass band of about 20 kilohertz. You could reduce the noise by making the filter narrower, or by putting a narrower filter between the output of the optical amplifier and the input of the demodulation board. The disadvantage of doing that is that you would have to make the narrow filter tunable, and use a scope to adjust it.

Transistors Q5 and Q6 form a differential amplifier that is the only real gain stage in the optical amplifier besides Q1. The purpose of using a differential amplifier is so that a differential signal will be available to drive the voltage comparator. It's nice to drive a comparator differentially because you get twice the signal but not twice the noise. There is one problem with a differential amplifier: if you want a reasonable amount of gain, the transistors must be well matched. That prevents one transistor from "current hogging" and saturating.

The matching of transistors can be done a number of different ways—a curve tracer is best but most people don't have access to one. Next best is a meter that actually measures gain at a given base or collector current. As a last resort, the circuit in Fig. 7 can be used. Some

kind of socket, such as an IC socket with only three pins can be used to hold the transistor. Simply measure the voltage from the collector to emitter, and choose two transistors that have the closest match between the collector-to-emitter voltage. Any transistor having less than about a volt has too much gain.

It's also a good idea to use bias resistors that have nearly the same values. Try to match the values of R16 and R23 and R17 and R24 as close as possible. If the final amplifier isn't matched within a volt, you might want to adjust the values of R19 and R22. Those resistors were purposely put there to allow some "balancing" of the differential amplifier. Values from 10 to 33 ohms should be fine. (Potentiometers were not used because they are expensive.)

#### FM demodulator

The schematic for the FM demodulator is shown in Fig. 8. An LM311 comparator (IC1) converts the rather small analog signal to a digital level for the CD4046 phase-locked loop (IC2). Remember that the amplitude of the recovered audio has nothing to do with the amplitude of the received signal. The amplitude of the recovered audio depends only on the

amount of frequency deviation set by the transmitter and the amplitude of your voice.

The phase-locked loop (IC2) is configured as a first-order FM demodulator. With no input signal, the center frequency of the loop (pin 3 of IC2, which is also TP3) is adjusted by R8 for a frequency of 50 kilohertz. Because the variation from one CD4046 to another can be quite large, you might have to adjust R7 and, perhaps, R9 as well.

The demodulated output from IC2 is low-pass filtered at 3 kilohertz by Q1 and its associated circuitry, and then sent to audio power amplifier IC3, a Motorola MC34119. A wider bandwidth can be obtained by making the filter higher in frequency. Since the "carrier" frequency is only 50 kilohertz, don't try extending the audio bandwidth to more than 6 or 7 kilohertz. Pin 1 of the MC34119 can be used for squelch or in conjunction with a push-to-talk switch to silence the receiver while transmitting. If you don't need the squelch, simply jumper pin 1 of IC3 to ground.

Although you can use a standard alkaline 9-volt battery to power the receiver, the current draw can be quite high on voice peaks. Six AA cells would be a much better choice.

We'll finish up the project next month with complete construction details.

**Use the 555 to generate sawtooth waves, detect missing pulses, convert DC to AC, boost DC voltage and more.**

# THE VERSATILE 555

RAY M. MARSTON

THE POPULAR 555 TIMER IC HAS been the star of three previous **Electronics Now** articles (September 1992, page 58, October 1992, page 69 and November 1992, page 61.) Just when you thought that all possible applications for that versatile 555 had been exhausted—surprise! This article takes the 555 into new territory—a sawtooth generator, a “ramp” generator, a time-base generator, a frequency meter, and even a tachometer for your car.

But that's not all—there is a missing-pulse detector, and DC voltage doubler, tripler and quadrupler. There are also negative and high-voltage generators and a DC to AC inverter!

If you've been following the previous articles and (we hope) building some or all of the circuits presented in them, you'll be all set for the circuits presented here. Who said the microprocessor was the most versatile IC, anyway?

The last three articles on the 555 explained its basic operating principles. You would have learned (or refreshed your memory) about how to place external components so the timer functions either as a monostable or astable multivibrator. You might want to reread the introductory sections of those articles to brush up on the unusual features of the 555. A complete schematic of the circuitry contained in the 555 is given as Fig. 2 on page 64 of the September 1992 issue.

Figure 1 is another functional block diagram and pinout of the bipolar 555 with a different ar-

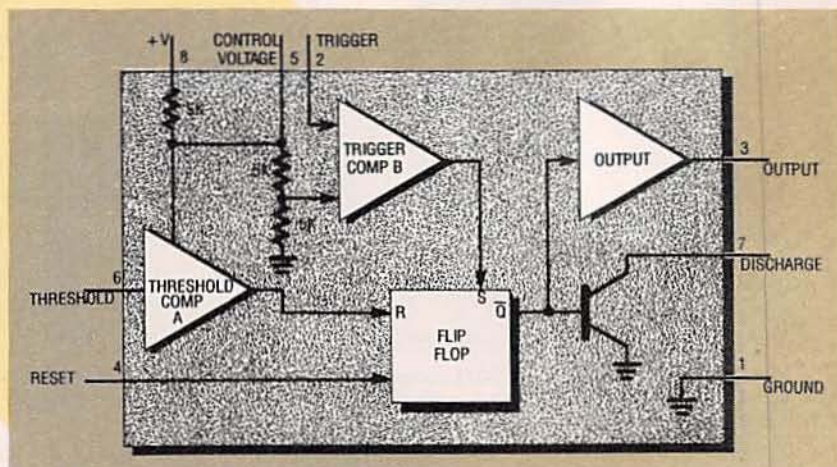


FIG. 1—FUNCTIONAL BLOCK DIAGRAM and pinout for the bipolar 555 timer IC.

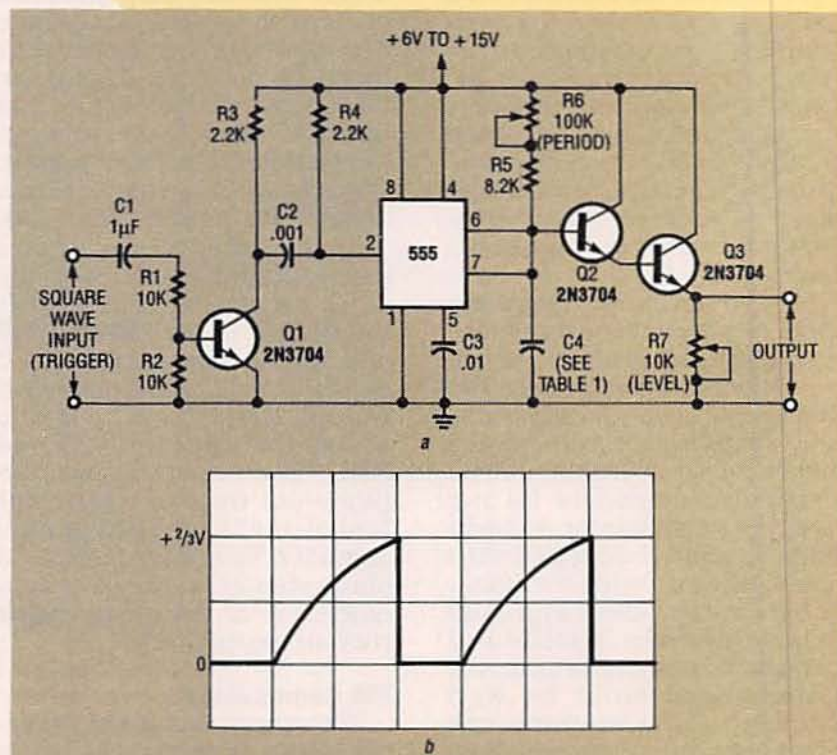


FIG. 2—TRIGGERED SAWTOOTH GENERATOR based on the 555, a, and typical output waveform, b.

range of functional blocks than the others given earlier, illustrating yet another manufacturer's preferred data book presentation. Neither diagrams nor data sheets on the 555 have been standardized.

## Sawtooth-wave generators

The 555 with external components can become a triggered nonlinear (exponential) sawtooth waveform generator, as shown in the schematic Fig. 2-a. The circuit is a modified

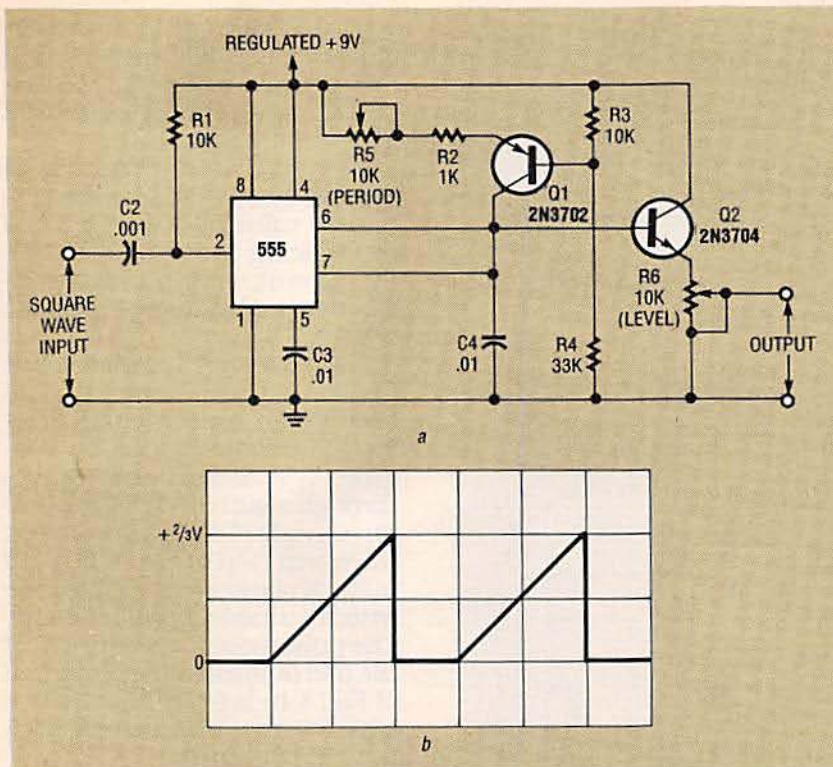


FIG. 3—LINEAR SAWTOOTH OR RAMP waveform generator based on the 555, a, and "ramp" waveform, b.

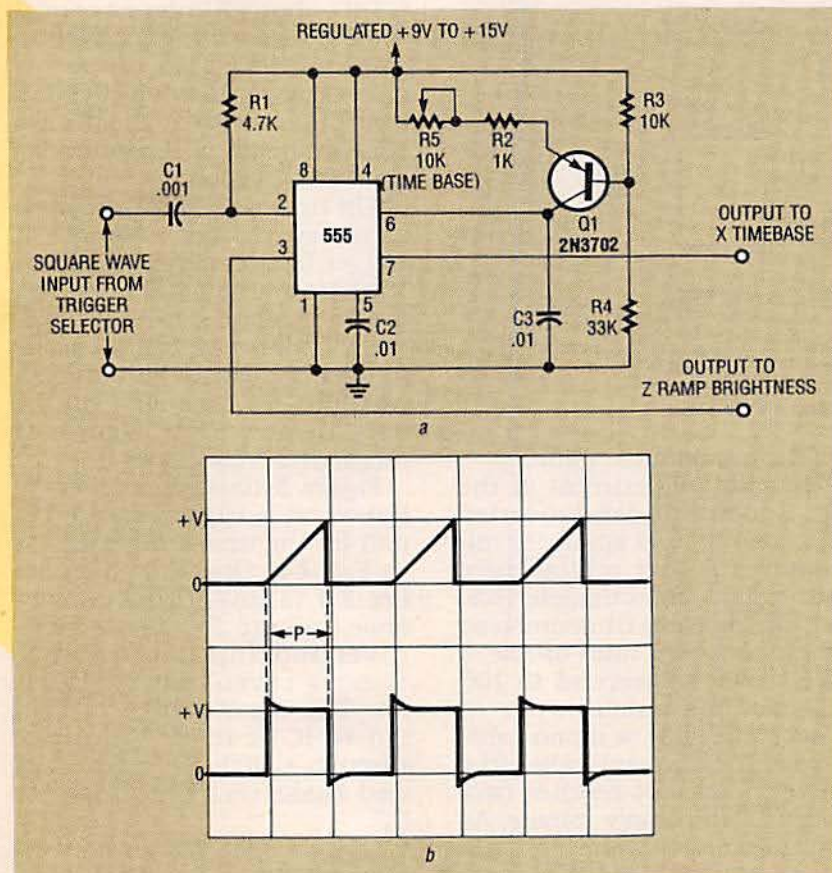


FIG. 4—OSCILLOSCOPE TIME-BASE GENERATOR circuit based on the 555, a, and ramp and ramp brightness pulse waveforms for an oscilloscope's X and Z axes.

monostable multivibrator that is triggered by an external square wave TRIGGER pin 2 obtained through capacitor C2 from the collector of transistor Q1. Note that OUTPUT pin 3 of the 555, used in most of the 555-based circuits presented earlier is unused here.

The voltage across C4 (the timing component) is normally zero, but whenever the circuit is triggered, C4 charges exponentially through resistor R5 and PERIOD potentiometer R6 to two-thirds of the supply voltage. At that time, the monostable period ends and the voltage across C4 drops abruptly to zero. The output sawtooth waveform (Fig. 2-b) is taken across capacitor C4 through buffer transistors Q2 and Q3 and LEVEL potentiometer R7.

The period of the sawtooth or width can be varied from 9 microseconds to 1.2 seconds with the capacitance values for C4 listed in Table 1. The circuit's maximum usable repetition frequency is approximately 100 kHz.

The generator must be triggered by rectangular input waveforms with short rise and fall times. Potentiometer R6 controls the sawtooth period over a decade, and potentiometer R7 controls the amplitude of the output waveform.

Figure 3-a shows a triggered linear sawtooth or ramp waveform generator. Capacitor C4 is charged by a constant-current generator that includes Q1. The output waveform (Fig. 3-b) is taken at the wiper of LEVEL potentiometer R6, which is coupled to the voltage across C4 through Q2. Note that the curved ramps of Fig. 2-b have been flattened.

When a capacitor is charged from a constant current source, its voltage rises at a predictable linear rate that can be expressed as:

Volts/second = amperes/farad  
By introducing more practical values, alternative expressions for the rate of voltage rise are:  
 $V/\mu s = A/\mu F$ , or  
 $V/ms = mA/\mu F$

Those formulas state that voltage rate-of-rise can be in-

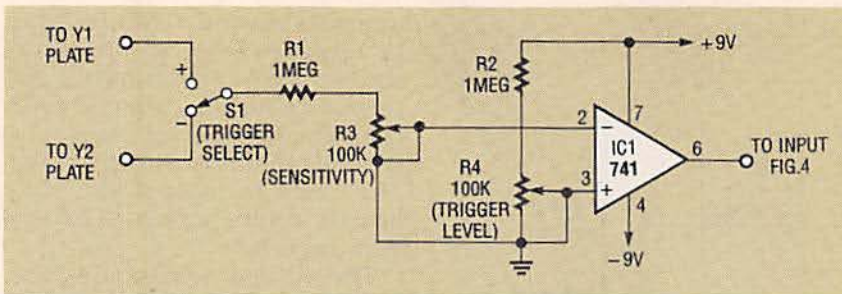


FIG. 5—TRIGGER SELECTION CIRCUIT for the Fig. 4 circuit

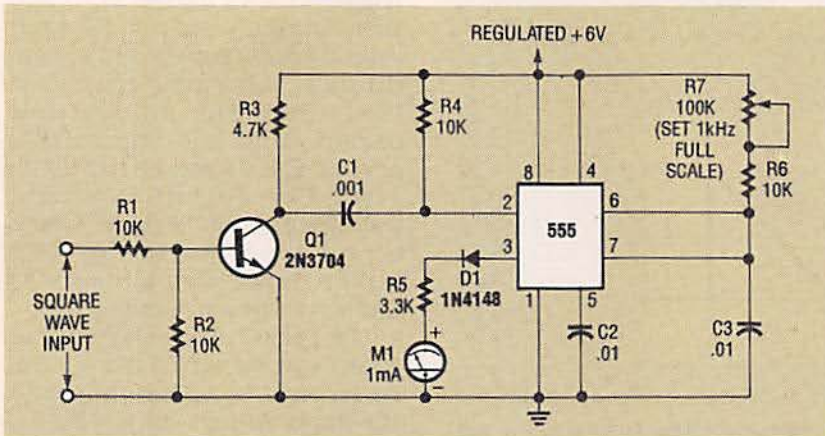


FIG. 6—A 1-kHz LINEAR-SCALE ANALOG FREQUENCY meter circuit based on the 555.

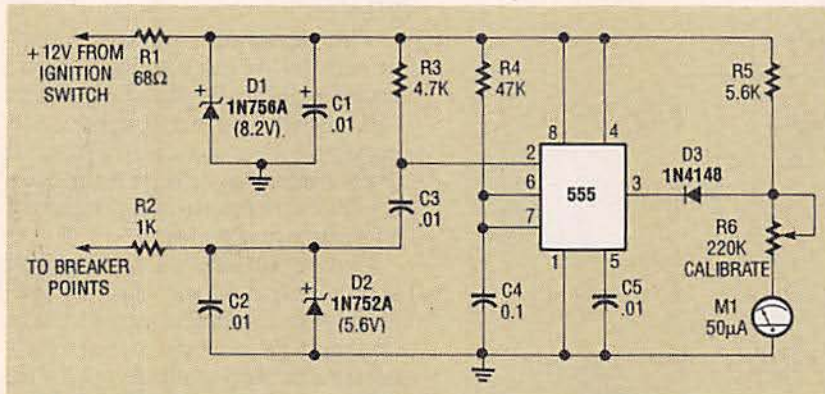


FIG. 7—VEHICULAR TACHOMETER CIRCUIT based on the 555.

 


FIG. 8—ALTERNATIVE ANALOG TACHOMETER CIRCUIT to Fig. 6.

creased either by increasing the charging current or by decreasing

The sawtooth cycles of the circuit have periods variable from 666 microseconds (2/3 millisecond) to 60 microseconds (6/100 millisecond).

Periods can be increased beyond those values by increasing the value of C4, or reduced by reducing the value of C4. In this circuit, stable timing periods depend on a stable voltage source.

Fig. 4-a shows how the circuit in Fig. 3-a can be modified to become an oscilloscope time-base generator. It can be triggered by external square waves through a suitable trigger selector circuit. The ramp output waveform (top of Fig. 4-b is fed to the X plates of an oscilloscope with a suitable amplifier stage. The pulsed output from pin 3 of the 555 (shown in the lower half of Fig. 4-b) is fed to the CRT's Z axis to trace the ramps with higher brightness.

The shortest useful ramp period that can be obtained from the circuit in Fig. 4-a (with a 0.001 microfarad capacitor C3) is about 5 microseconds. That value, when expanded to give full deflection on an oscilloscope with a ten-division graticule, yields a maximum timebase rate of 0.5 microsecond per division.

The timebase circuit of Fig. 4-a can synchronize signals at trigger frequencies up to about 150 KHz. At higher frequencies, the input signals must be divided by a single- or multi-decade frequency divider. With that approach, the timebase can be used to view input signals at megahertz frequencies.

Figure 5 illustrates a simple but versatile trigger selector circuit for the timebase generator in Fig. 4-a. Operational amplifier IC1 (a  $\mu$ A741) has a reference voltage fed to its non-inverting input pin 3 by TRIGGER LEVEL potentiometer R4. The signal voltage is then fed to IC1's inverting pin 2 through switch S1, resistor R1 and SENSITIVITY potentiometer R3.

Switch S1 selects either in-phase or out-of-phase input signals from the Y-driving amplifier of the oscilloscope, permit-

ing the capacitance value.

The charging current in the Fig. 3-a circuit can be varied over the range of about 90 microamperes to 1 milliampere with PERIOD potentiometer R5, thus giving the 0.01 microfarad timing capacitor rates-of-rise of 9 volts per millisecond to 100 volts per millisecond.

Each one-shot or monostable cycle of the 555 ends when the voltage across C4 reaches two-thirds of the supply voltage. As shown in Fig. 3-a, the supply is 9 volts, so two-thirds of 9 volts is 6 volts, the amplitude of the ramp waveforms in Fig. 3-b.



ting the selection of either the plus or minus trigger modes. The output of the circuit in Fig. 5 is coupled directly to the C1 input of Fig. 4.

### Analog frequency meters

Figure 6 shows the 555 IC organized as a linear-scale analog frequency meter with a full-scale sensitivity of 1 kHz. The circuit's power is obtained from a regulated 6-volt supply, and its input signals can be pulses or square-wave signals with peak-to-peak amplitudes of 2 volts or greater. Transistor Q1 amplifies this input signal enough to trigger the 555. The output from pin 3 is fed to the 1-milliampere full-scale deflection moving-coil meter M1 through offset-canceling diode D1 and multiplier resistor R5.

Each time the monostable multivibrator is triggered, it generates a pulse with a fixed duration and amplitude. If each generated pulse has a peak amplitude of 6 volts and a period of 1 millisecond, and the multivibrator is triggered at an input frequency of 500 Hz, the pulse will be high (at 6 volts) for 500 milliseconds in each 1000 milliseconds. Moreover, the mean value of output voltage measured over this period is  $500 \text{ milliseconds} / 1000 \text{ milliseconds} \times 6 \text{ volts} = 3 \text{ volts}$  or half of 6 volts.

Similarly, if the input frequency is 250 Hz, the pulse is high for 250 milliseconds in each 1000-millisecond period. Therefore, the mean output voltage equals  $250 \text{ milliseconds} / 1000 \text{ milliseconds} \times 6 \text{ volts} = 1.5 \text{ volts}$  or one quarter of 6 volts. Thus, the circuit's mean value of output voltage, measured over a reasonable total number of pulses, is directly proportional to the repetition frequency of the monostable multivibrator.

Moving-coil meters give mean readings. In the circuit of Fig. 6 a 1-milliampere meter is connected in series with multiplier resistor R5, which sets meter's sensitivity at about 3.4 volts full-scale deflection. The meter is connected to give the mean output value of the multi-

 


FIG. 9—MISSING-PULSE DETECTOR with LED or relay output.

 


FIG. 10—DC VOLTAGE-DOUBLER based on the 555.

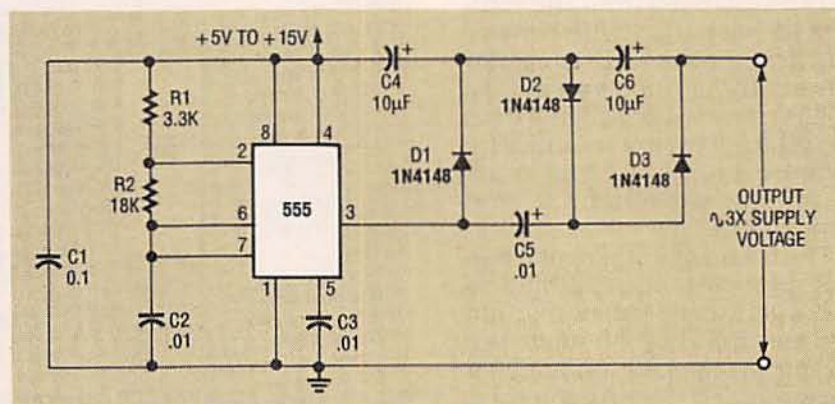


FIG. 11—DC VOLTAGE-TRIPLER based on the 555.

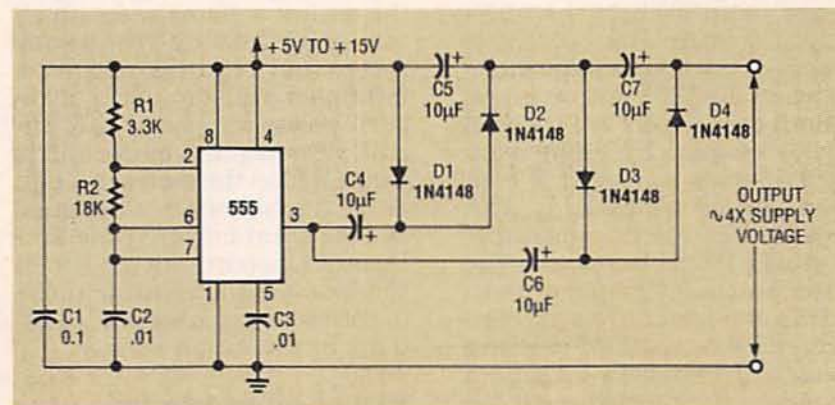


FIG. 12—DC VOLTAGE-QUADRUPLER based on the 555.

vibrator, and its reading is directly proportional to the input frequency.

With the component values shown, the circuit is organized to read full-scale deflection at 1 kHz. To set up the circuit initially, a 1-kHz square-wave signal is fed to its input, and full-scale-adjust potentiometer R7 (it controls pulse length) is set to give a full-scale reading on the meter.

The full-scale frequency of the circuit in Fig. 6 can be varied from about 100 Hz to 100 kHz by selecting the value of C3. The circuit can read frequencies up to tens of megahertz by introducing the input signals to the monostable multivibrator through either a single or multi-decade digital divider. The dividers can reduce the input frequencies to values that can be read on the meter.

Figure 7 shows how the circuit in Fig. 6 can be modified to become an analog tachometer or revolutions per minute (rpm) meter for motor vehicles. The circuit is powered by a regulated 8.2 volts derived from the vehicle's 12-volt battery with resistor R1, Zener diode D1, capacitor C1, and the ignition switch. The 555 is triggered by a signal from the vehicle's breaker points conditioned by the network of resistor R2, capacitor C2, and Zener diode D2.

The 50-microampere moving-coil meter M1, the rpm indicator, is activated from OUTPUT pin 3 of the 555 through diode D3. Current is applied to the meter through series-connected resistor R5 and CALIBRATE potentiometer R6 from the power supply when the 555's output is high. But current is dropped nearly to zero by diode D1 when the 555's output is low.

Both the circuits of Figures 6 and 7 are powered from regulated sources to ensure a constant pulse amplitude and provide accurate, repeatable readings from the meter. The meter is actually a current-indicating device, but it is connected as a voltage-reading meter with suitable multiplying resistors. They are R6 and R7 in Fig. 6 and R5 and R6 in Fig. 7.

 


FIG. 13—DC NEGATIVE-VOLTAGE GENERATOR based on the 555.

 


FIG. 14—NEON-LAMP DRIVER based on the 555, a, and DC-to-DC converter with rectifier and filter replacing lamp, b.

 


FIG. 15—DC-to-AC INVERTER based on the 555.

The diagram of Fig. 8 shows the outline schematic for an alternative analog frequency meter that requires neither a multiplier resistor nor a regulated power supply. In this circuit, OUTPUT pin 3 of the 555 is connected to the meter through JFET transistor Q1. Configured as a constant-current generator through potentiometer R3, it sends a fixed-amplitude pulse to the meter regardless of variations in the supply voltage.

#### Missing-pulse detector

Figure 9 illustrates how the

555 can become the key component in a *missing-pulse detector* that closes a relay or illuminates a LED if a normally expected event fails to occur. The 555 is connected as a monostable multivibrator except that Q1 is placed across timing capacitor C1, and its base is connected to TRIGGER pin 2 of the IC through R1.

A series of short pulse- or switch-derived clock input signals from the monitored event is sent to pin 2. The values of R3 and C1 were selected so that the natural monostable period of

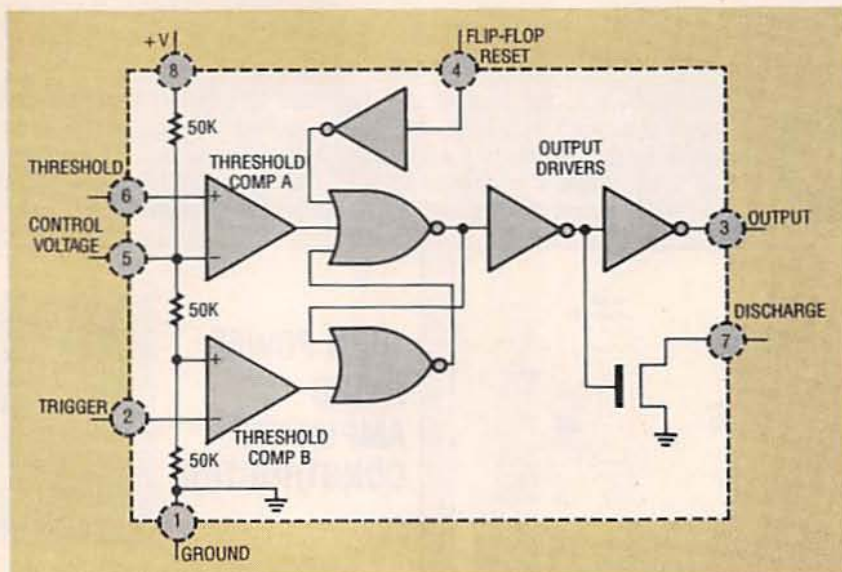


FIG. 16—FUNCTIONAL BLOCK DIAGRAM and pinout of the CMOS 7555.

the IC is slightly longer than the repetition period of the clock input signals.

Thus, each time a short clock pulse arrives, C1 is rapidly discharged through Q1, and simultaneously a one-shot timing period is initiated through TRIGGER pin 2 of the IC, forcing OUTPUT pin 3 high. Before each monostable period can terminate naturally, however, a new clock pulse arrives and starts a new timing period. Therefore OUTPUT pin 3 remains high as long as clock-input pulses continue to arrive within the preset time limits.

If a clock pulse is missing or its period exceeds the pre-set limits, the monostable period will end on its own. If that happens, pin 3 of the IC will go low and drive either the relay or LED "on." As a result, the circuit becomes a missing-pulse detector. It will produce a pulse output when an input pulse fails to occur within the timer delay.

Missing-pulse detectors like this can automatically warn of gaps or one or more missing pulses in a stream of pulses at the input. They are used in communications systems, continuity testers, and security systems. With the component values shown, the timer has a natural period of about 30 seconds. This period can be changed by changing R3 or C1 to satisfy specific needs.

### Voltage converters.

The 555 IC can be instrumental in converting a DC voltage to a higher DC voltage, reversing the polarity of a DC voltage or converting it to an AC voltage. Figures 10 to 15 show variations of those circuits.

Figure 10, for example, shows how the 555 functions in a DC voltage doubler. The 555 is organized as a free-running astable multivibrator or square-wave generator that oscillates at about 3 kHz. (The oscillation frequency is set by the values of R1, R2 and C2.) The circuit's output is sent to the capacitor/diode voltage-doubler network made up of C4, D1, C5, and D2. That network produces a voltage that is about twice the supply voltage. Capacitor C1, across the supply, prevents the 3-kHz output of the 555 from being fed back to the IC, and C3 stabilizes the circuit.

The voltage-doubler circuit of Fig. 10 will operate from any DC supply offering from 5 to 15 volts. As a voltage doubler it can provide outputs from about 10 to 30 volts. Higher output voltages can be obtained by adding more multiplier stages to the circuit circuit. Figure 11 is the schematic for a DC-voltage tripler that can supply from 15 to 45 volts, and Fig. 12 is the schematic for a DC voltage quadrupler that supplies from 20 to 60 volts.

The DC negative-voltage generator is a particularly useful 555-based converter circuit. It supplies an output voltage that is almost equal in amplitude but opposite in polarity to that of the IC supply. This circuit can provide both positive and negative voltages for powering op-amps and other IC's with dual power requirements from a positive supply. The DC negative-voltage generator in Fig. 13, like that shown in Fig. 10, is a 3-kHz oscillator that drives a voltage-doubler output stage made up of C4, C5, D1, and D2.

Figures 14-a and 15 show DC to AC inverters that change input DC voltage to output AC voltage by means of transformer coupling. The AC voltage from these inverters needs no further conditioning, and it can be converted back into higher DC voltages with the addition of only a half-wave rectifier and a capacitor filter.

The inverter shown in Fig. 14-a can drive a neon lamp with its AC output. If the lamp and resistor R4 are replaced by the diode and capacitor filter as shown in Fig. 14-b, the AC output can be converted back to a low-current, high-voltage DC output. For example, with a 5- to 15-volt DC input, the inverter can produce an output of several hundred volts DC.

The 555 in Fig. 14-a is configured as a 4-kHz oscillator and its square-wave output from pin 3 is fed back to the input of audio transformer T1 through resistor R3. Transformer T1 has the necessary ratio of primary to secondary turns to produce the desired output voltage. For example, with a 10-volt supply and a 1:20 turns ratio on T1, the unloaded output of T1 will be 200 volts, peak.

The DC-to-AC inverter schematic of Fig. 15 produces an AC output at line frequency and voltage. The 555 is configured as a low-frequency oscillator, tunable over the frequency range of 50 to 60 Hz by FREQUENCY potentiometer R4. The 555 feeds its output (amplified by Q1 and Q2) to the input turns of transformer T1, a reverse-connected filament trans-

# E-N Engineering Admart

Rates: Ads are 2 1/4" x 2 1/4". One insertion \$995 each. Six insertions \$950 each. Twelve insertions \$925 each. Closing date same as regular rate card. Send order with remittance to Computer Admart, Electronics Now Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-1-516-293-3000. FAX 1-516-293-3115. Only 100% Computer ads are accepted for this Admart.

## DR. "CHIP" MUNK SAYS



6805/68HC05/68HC11  
DEVELOPMENT TOOLS  
QUALITY and SERVICE  
AFFORDABILITY  
TECI

"Chip" experts agree with Dr. Munk. TECI's PC based microcontroller development tools are the most cost effective for veterans or beginners.

6805 PRIMER FOR BEGINNERS..... \$195.00  
6805/68HC05/68HC11 CROSS ASSEMBLERS..... \$99.00  
6805/68HC05 SIMULATOR / DEBUGGERS..... \$99.00  
68705P3,P5,U3,U5,R3,R5 PROGRAMMERS FROM \$349.00  
68HC705/68HC805 PROGRAMMERS FROM \$395.00  
COMPLETE PC BASED DEV. SYSTEMS FROM \$449.00  
68HC05/68HC11 REAL TIME EMULATORS FROM \$895.00

TECI


CALL TOLL FREE 1-800-336-8321  
The Engineers Collaborative, Inc.  
Rt #3 Box 8C, Barton, VT 05822 USA  
TEL:(802)525-3458 FAX:(802)525-3451

## MIDI PROJECTS



BP182—MIDI interfacing enables any so equipped instruments, regardless of the manufacturer, to be easily connected together and used as a system with easy computer control of these music systems. Combine a computer and some MIDI instruments and you can have what is virtually a programmable orchestra. To order your copy send \$6.95 plus \$2.50 for shipping in the U.S. to Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240.
 
## HIGH POWER AUDIO AMPLIFIER CONSTRUCTION



BP277—Here's background and practical design information on high power audio amplifiers capable of 300 ± 400 watts r.m.s. You'll find MOSFET and bipolar output transistors in inverting and non-inverting circuits. To order your copy send \$6.25 plus \$2.50 for shipping in the U.S. to Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240.

former with the necessary step-up turns ratio. Capacitor C4 and coil L1 filter the input to T1, assuring that it is effectively a sine wave.

### A CMOS version of the 555

The standard bipolar 555 timer IC is still one of the most popular and versatile IC's today, but it has some drawbacks that were overcome by a CMOS version. For example, the 555 will not operate from voltages less than about 5 volts. Moreover, it typically draws 10 milliamperes of quiescent current when run from a 15-volt supply. This rather large current drain makes it unsatisfactory for most battery-powered circuits.

In addition to those shortcomings, the 555 produces a massive 400-milliamperere current spike from the supply as its output is switched from one state to the other. A spike, lasting only a fraction of a microsecond, can cause lost bits in digital circuits near the 555 or powered from the same supply.

The CMOS version of the 555 timer, also able to operate in both monostable and astable modes, is known generically as the 7555. Figure 16 shows the functional block diagram and pinout of the 7555. This can be compared with the functional block diagram of Fig 1. Note that the pinout is identical.

Harris Semiconductor's version of the 7555, for example, is designated the ICM7555. In common with all other 7555's, it will run from a +2- to +18-volt DC supply. Notice that the resistors in its internal voltage divider are 50 K rather than the 5K of the 555. Other sources of the 7555 are Maxim (ICM7555) and Sanyo (LC7555).

Supply current to the 7555 is typically only 60 microamperes when run from an 18-volt supply. In addition, typical TRIGGER, THRESHOLD, and RESET currents are 20 picoamps, orders of magnitude lower than those of the bipolar 555. Those low currents permit the use of higher impedance timing elements for longer

RC time constants. The 7555 can be organized to time out in periods from microseconds to hours.

Table 2 compares the characteristics of the 7555 to those of the 555. The 7555 permits:

- Lower supply current
- Wider supply voltage range
- Lower power dissipation
- Lower current spikes in output transitions
- Higher switching frequency performance


These improvements must be balanced against the higher cost of the 7555. The 7555 should be specified only if:

- It is to be used in a battery-powered circuit where power economy is critical
- Available power is 5 volts or less (too low for the 555)
- It is to be in digital circuitry whose signal output could be degraded by noise.

The 7556 is the dual CMOS counterpart of the bipolar 556. The 7555 can directly replace any 555 in all the circuits presented in this series.

R-E

CIRCLE 184 ON FREE INFORMATION CARD

 

**High resolution and lots of color bring gorgeous images to your PC.**

STAN WARNER

TUMBLING PRICES AND SURGING power have brought computers into nearly every facet of our lives. Gone forever are the days when only large companies could afford computers. No longer does it take a mainframe that nearly fills an entire room to sort business records or do mind-bending arithmetic. Today's powerful yet affordable desktop machines are taking on exciting new chores in every phase of business—and the home.

According to the Electronic Industries Association (EIA), the computer and peripheral market more than doubled during the 1980's, from \$24.3 billion in 1980 to \$56.1 billion in 1990, as shown in Fig. 1. According to the EIA, the home computer market grew 50% in one three-year period, from \$4.5 billion in 1988 to \$6.4 billion in 1991. In addition, personal computers can be found in 33% of the homes in the United States.

Today's computers can crunch reams of data at blinding speeds, but improvements in monitor technology have also increased the number of computer applications. Desktop publishing systems that combine text and graphics are bringing print-shop quality to financial reports, company newsletters, and sales presentations. Surgeons create computer-generated, 3-D images of their patients' insides long before they pick up a scalpel. Landscape artists design life-like layouts with trees, shrubs, and flowers before turning a single spade of dirt.

Monitor manufacturers are continually working to improve graphics clarity and resolution, and large strides have occurred during the past decade. The monitors of the early eighties had poor resolution and fuzzy graphics compared to those on the market today. Today's mainstream monitors are capable of displaying crisp graphics and

text. High-end monitors produce fabulous pictures with crystal-clear resolution.

#### **Monitor improvements**

These improvements have come about as a result of enhancing four primary performance-defining characteristics: horizontal frequency, horizontal resolution, vertical frequency, and vertical resolution, as shown in Fig. 2. Each is defined below:

**Horizontal Frequency** The number of times per second the electronic beam travels horizontally across the CRT and back. Horizontal scan time is the inverse of horizontal frequency ( $1/f_h$ ).

**Horizontal Resolution** The number of dots or picture elements ("pixels") that can be displayed horizontally. A pixel is the smallest dot the monitor can display.

**Vertical Frequency** The number of times per second the electron beam travels from the

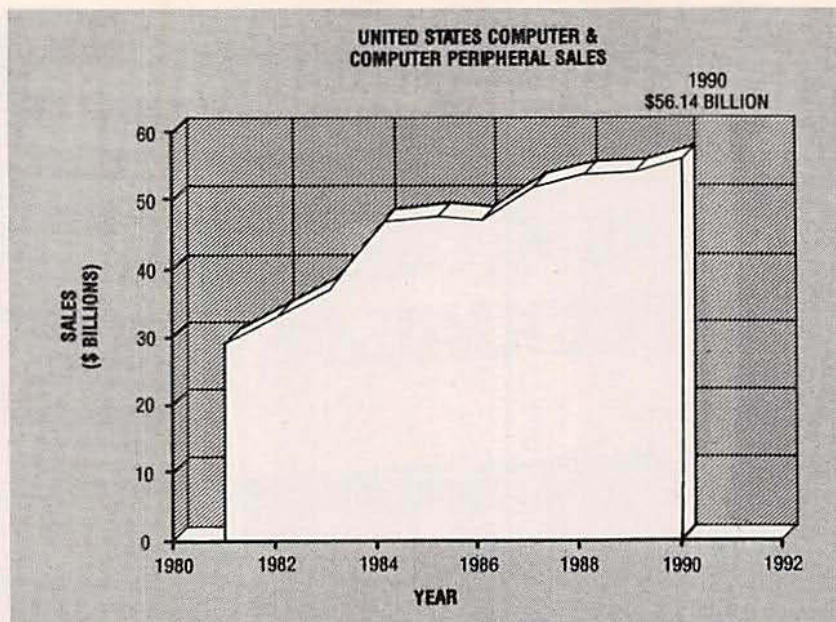


FIG. 1—SALES OF COMPUTERS AND PERIPHERALS surged in the 1980's, and continue to grow in the 1990's.

 


FIG. 2—COMPUTER MONITOR PERFORMANCE can be defined by four characteristics: horizontal frequency and resolution, and vertical frequency and resolution.

top of the CRT to the bottom and back. Vertical scan time is the inverse of vertical frequency ( $1/f_v$ ).

**Vertical Resolution** The number of picture elements displayed vertically on the CRT. Vertical resolution is comparable to the number of "lines" in

television terminology.

A fifth characteristic, dot pitch, also plays a role in determining the resolution of a monitor. Dot pitch is the distance between like colors in the shadow mask. Dot pitch determines the size of the smallest pixel a color CRT can display.

The smaller the dot pitch, the sharper the image. Typical values of dot pitch are between 0.26 and 0.50 mm. Figure 3 shows the distance between the centers of two red dots.

Today's high-resolution

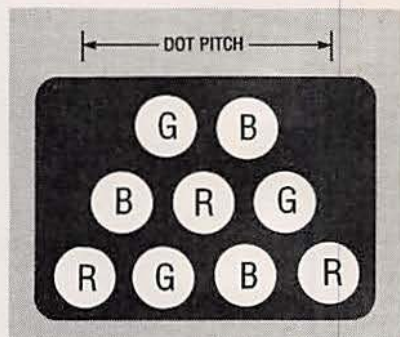


FIG. 3—DOT PITCH is the distance between like colors in a CRT shadow mask.

monitors represent improvements over their predecessors in several ways, including increased horizontal and vertical frequency and resolution, and decreased dot pitch. On early monitors, the electron beam typically took  $63.7 \mu\text{s}$  (corresponding to a frequency of 15.7 kHz) to scan one line. Today it is not uncommon for the beam to complete its trip in  $13.0 \mu\text{s}$  (76.9 kHz) or even less, as shown in Fig. 4.

In addition, more pixels are being displayed per horizontal line, and more lines are displayed per frame. Whereas early computer monitors had 640 horizontal pixels and 200 lines, common monitors today have 1,024 horizontal pixels and 768 lines—or more. A faster scan rate gives the monitor extra time to display additional lines and pixels.

#### Video bandwidth

Video bandwidth is the highest frequency the monitor's video circuits can pass. In general, higher resolution requires higher bandwidth. A visual indication of sufficient bandwidth comes from displaying a pattern that produces a single-pixel line, as shown in Fig. 5.

To get a basic understanding of the bandwidths required by high- and low-resolution monitors, let's calculate the bandwidth required by each.

 


FIG. 4—A HIGH-RESOLUTION MONITOR scans across the screen more than four times, while a low-resolution monitor does so once.

We'll analyze a high-resolution monitor that scans at 64 kHz and displays 1024 pixels per line, and a low-resolution monitor that scans at 15.7 kHz and displays 640 pixels per line.

#### High-Resolution Bandwidth

Inverting the horizontal scanning frequency (64 kHz) gives a total horizontal scan time of 15.6  $\mu$ s. As shown in Fig. 6, about 80% of that time is for active video (what's seen on the monitor) and about 20% is for blanking. Using the 80/20 ratio in the example translates into 12.5/3.1  $\mu$ s active/blanking. If it takes 12.5  $\mu$ s to display 1024 pixels, it therefore takes 12.5/1024 = 12.2 ns to display a single pixel. Inverting that figure gives a bandwidth of 81.9 MHz. So, to see a crisp, distinct line, one pixel wide, the bandwidth of the video amplifiers in a high-resolution monitor must be 81.9 MHz or greater.

#### Low-Resolution Bandwidth

A horizontal scan rate of 15.7 kHz gives a horizontal scan time of 63.7  $\mu$ s. Eighty percent of that is 51.0  $\mu$ s, during which 640 pixels will be displayed. Thus the time per pixel = 51/640 = 79.6 ns. Inverting that figure gives a low-resolution bandwidth of 12.6 MHz.

#### Computer monitors

Monitors can be divided into three basic categories: digital, analog, and ECL (emitter-coupled logic). Digital and analog monitors can be either monochrome or color. ECL monitors are always monochrome.

The video input signals to a

 


FIG. 5—A ONE-PIXEL VERTICAL LINE is a good indicator of a monitor's maximum bandwidth. A crisp, distinct line shows that the monitor has sufficient bandwidth.

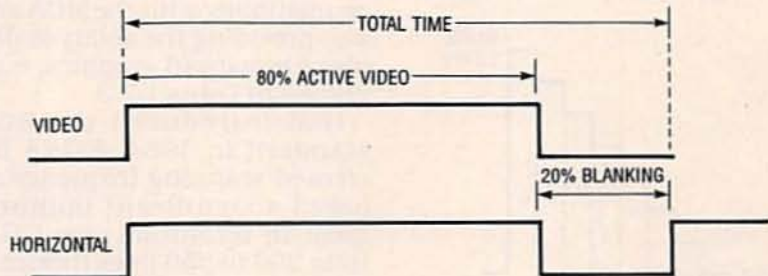


FIG. 6—A TYPICAL VIDEO SCAN LINE consists of 80% active video and 20% blanking.

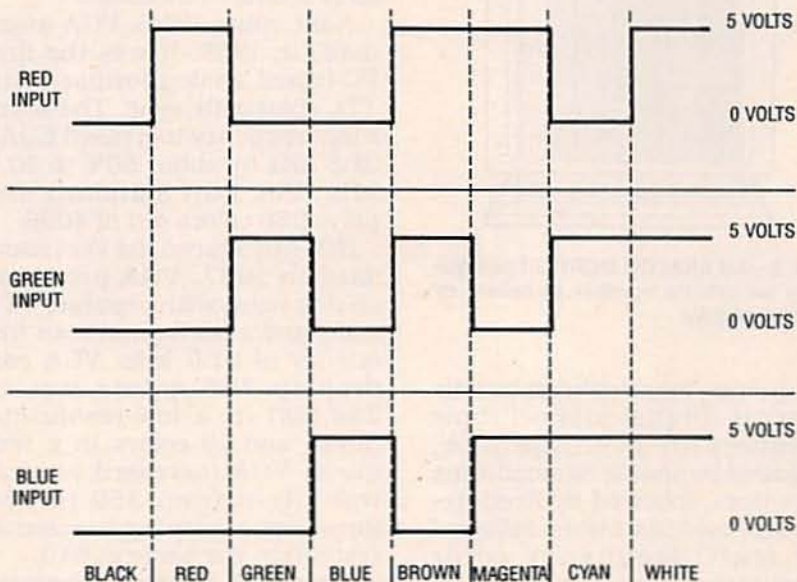


FIG. 7—A DIGITAL-INPUT MONITOR PRODUCES COLORS based on various combinations of signals. For example, the monitor displays magenta when red and blue are high and green is low.

digital monitor are TTL logic levels that are either high (great-

er than 2 volts) or low (less than 0.8 volts). A color digital monitor has red, green, blue and (usually) intensity inputs, and it can display as many as 64 colors, depending on the binary code on the RGBI inputs. Figure 7 shows how different combinations of 1's and 0's translate into different colors on a digital color monitor. A digital monochrome monitor can display as many as 64 shades of gray (or green or amber, depending on the phosphor), also by using combinations of logic levels.

An analog monitor can display an infinite number of colors (or shades of gray). The video signal fed to an analog monitor is usually 0.7 volts peak-to-peak (black to white).

Figure 8 illustrates the correspondence between analog in-

put voltage and gray level.

To achieve fast switching time and higher resolution, some high-end monitors use ECL IC's. ECL monitors are monochrome, can display only a limited number of shades of gray, typically have a 19-inch or larger screen, and horizontal resolutions greater than 1024 pixels.

### Video adapters

Most IBM-compatible personal computers have a video adapter card that is responsible for generating the video and sync signals used by the monitor. There are many standards for the different video formats, as shown in Table 1. Each format has a different resolution and scan rate. Fixed-frequency monitors are built to handle just one format; multi-

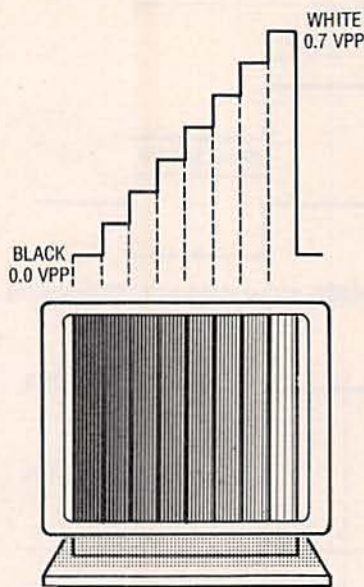


FIG. 8—AN ANALOG MONITOR can display an infinite number of colors or shades of gray.

frequency monitors can handle several. Digital monochrome monitors are least expensive, followed by analog monochrome monitors, followed by fixed-frequency color monitors, followed by multi-frequency color monitors.

IBM introduced the CGA and MDA formats in the early 1980's. Both are digital formats. CGA provides 16 colors and can display bit-mapped graphics at a resolution of 640 × 200. MDA

provides only two shades of a single color and cannot display graphics. The Hercules card met a need by providing total compatibility with the MDA and also providing the ability to display bit-mapped graphics, e.g., graphs in Lotus 1-2-3.

IBM introduced the EGA standard in 1984. EGA's increased scanning frequency allowed a significant improvement in resolution over CGA, from 200 to 350 lines (horizontal resolution remained the same). EGA is a digital standard that can simultaneously display 16 of a total of 64 colors.

Next came IBM's PGA standard, in 1985. It was the first PC-based analog format, with TTL composite sync. The scanning frequency increased EGA's 21.8 kHz by about 50% to 30.5 kHz. The PGA standard displays 256 colors out of 4096.

IBM introduced the VGA standard in 1987. VGA produces analog video with separate TTL sync, and a horizontal scan frequency of 31.5 kHz. VGA can display 256 colors out of 256,000 in a low-resolution mode, and 16 colors in a text mode. VGA increased vertical resolution from 350 to 480 lines, again keeping horizontal resolution the same at 640.

After VGA started to become popular, the market demanded even more resolution and color. IBM introduced the 8514, but prices were high, and at first only a model for the PS/2 was available. So video-card vendors

introduced a variety of Super VGA formats that typically max-out at 1024 × 768, with 256 colors. IBM later introduced XGA, the current version of which supports 1024 × 768 × 256. There are rumors that an upcoming 80x86 microprocessor from Intel will have a built-in XGA video processor.

The Macintosh II standard produces an analog video signal with separate composite TTL sync. Other MAC standards place the composite sync on the green video line. Some Macintosh video cards are capable of producing 256 colors from more than 16 million. These cards are also available for PC's.

The video formats shown in Table 1 illustrate the vast changes that have occurred in the PC side of the computer market during the past ten years. But the chart doesn't tell the entire story; these are only the monitors sold for mainstream applications (e.g. word processing, spreadsheets, and home finance). In other areas (e.g., engineering workstations, medical imaging devices, high-end publishing equipment), it is not uncommon for monitors to have resolutions of 2,048 pixels or more, and horizontal scan frequencies three to four times greater than that of VGA. Wouldn't it be great to have one of those monitors sitting on your desk? If current market trends continue, there's a good chance that you will—and soon.

TABLE 1—COMMON COMPUTER MONITOR FORMATS

System/Mode	Horizontal Frequency (kHz)	Vertical Frequency (Hz)	Horizontal Resolution (Pixels)	Vertical Resolution (Lines)
Color/Graphics Array (CGA)	15.7	60	640	200
Monochrome Display Adapter (MDA)	18.4	50	720	350
Hercules Graphics Adapter (HGC)	18.4	50	720	350
Enhanced Graphics Adapter (EGA)	21.8	60	640	350
Professional Graphics Adapter (PGA)	30.5	60	640	480
Video Graphics Array (VGA) Mode 1	31.5	70	640	350
Video Graphics (VGA) Mode 2	31.5	60	640	480
Video Graphics (VGA) (Mode 3)	31.5	70	720	400
Super VGA	35.2	56	800	600
8514A	35.2	87	1024	768
Extended Graphics Adapter (XGA)	35.2	87	1024	768
Apple Macintosh II	35.5	67	640	480



# 47st. Photo<sup>®</sup>

The latest in electronics is only a phone call away! **1-800-221-7774**

In N.Y. or if busy call: 1-718-722-4750. Please mention code ES892.



**NEW!**  
**AIWA CSD-EX1**  
**PORTABLE LCD**  
**RADIO CASSETTE CD PLAYER**

- High power output
- Power saving switch plus auto stop
- 20-selection random programmable memory CD
- AM wide/FM stereo tuner

(AIW-427)  
Sugg. Retail \$179.95 **Our Price \$139.95**



**NEW!**  
**AIWA NSX-330**  
**30W/ch HI-FI MINI COMPONENT**  
**SYSTEM WITH SURROUND SOUND**

- Super T-bass

**Includes:**

- 3-preset graphic equalizer
- 5-band spectrum analyzer
- Wireless remote
- FM/AM tuner with 32-station random preset
- Dual auto reverse cass. w/Dolby B NR
- Optical digital output terminal
- 3-way speaker

(AIW-424)  
Sugg. Retail \$560.00 **Our Price \$399.95**



**NEW!**  
**AIWA XP-7**  
**PORTABLE CD PLAYER**  
**WITH IN CAR USE**

- 1-bit dual D/A converter
- 8-times oversampling digital filter
- Optical digital output terminal
- 24-random programmable memory
- Heat-resistant for in car use
- Random play with 3-way repeat

**Includes:** Rechargeable battery BP-50, stereo headphones with remote control, AC adaptor recharger and connection cord.

(AIW-420)  
Sugg. Retail \$290.00 **Our Price \$249.95**



**BONUS!**  
Free case with purchase of E-63  
**\$59 Value!**

**CANON E-63**  
**8mm CAMCORDER WITH**  
**8:1 POWER ZOOM**

- High speed shutter
- 180° FlexiGrip
- 2-lux low light
- Sports finder
- Wireless Remote (CAN-6300)

**Super Value!**



**NEW!**  
**PANASONIC RQ-S35V**  
**AM/FM STEREO CASSETTE**  
**PLAYER WITH AUTO REVERSE**

- Ultra compact size
- Digital synthesizer tuner with 7AM/7FM presets
- S-XBS & Dolby NR
- LCD tpeae/radio display
- Dual clock/alarm functions
- One button wired remote

**Includes:**  
Rechargeable battery and charger.  
(PAN-275-2)  
Sugg. Retail \$209.95 **Our Price \$169.95**



**NEW!**  
**SONY WM-WX50**  
**WALKMAN®**  
**STEREO CASSETTE**  
**PLAYER**

**WIRELESS HEADSET!**

- Broadcasts up to 9 ft.
- Auto reverse Mega Bass 2x sound system with variable control
- Dolby NR (SON-3483)

Sugg. Retail \$249.95 **Our Price \$179.95**



**SHARP IQ-8400**  
**ELECTRONIC ORGANIZER**

- 256 KB memory
- Typewriter style keyboard
- Hi-contrast 40 char. by 8 line screen
- Month/week & day calendar
- 3 phone directories
- Business Card function (SHA-840C)

Sugg. Retail \$499.95 **Our Price \$319.95**



**PANASONIC KX-T4300**  
**CORDLESSPHONE WITH**  
**ANSWERING MACHINE**

- 10 channel access • Rubber antenna
- Tone/pulse • 2-way paging
- 10-number speed dial • Message alert
- LED readout
- 11-function tone remote
- Auto logic operation.

(PAN-4300)  
Sugg. Retail \$199.95 **Our Price \$159.95**



**PANASONIC KX-T9000**  
**900MHz POCKET-SIZED FOLDING**  
**CORDLESSPHONE**

- Operates on 902/928MHz
- Sound Charger technology
- 30ch auto scan • Auto Intercom
- 2 interchangeable batteries
- 2-way paging & auto intercom
- 10, 20 digit no. auto dial
- Handset Auto switch to 'talk' mode (PAN-9000)

Sugg. Retail \$499.95 **Our Price \$399.95**



**NEW!**  
**CASIO BP-100**  
**BLOOD PRESSURE**  
**MONITOR WATCH**

- Water resistant to 50 meter
- 12/24-hour formats
- 3 multi-function alarms
- Altimeter, Depth meter & Barometer
- Countdown alarm
- 1/100 stopwatch (CAS-826)

Sugg. Retail \$169.95 **Our Price \$129.95**



**SONY XVT-600**  
**ADD PRO STYLE SUPERIMPOSED**  
**TITLES TO YOUR VIDEOS!**

- 15 color picture computer superimposes picture title or background to video
- Draw lines, add color—endless possibilities!

(SON-409)  
Sugg. Retail \$600 **SALE! \$109.95**



**PANASONIC CTP-2066S**  
**20" STEREO MONITOR-RECEIVER**  
**WITH S-VHS INPUT (Over 500**  
**lines horizontal resolution)**

- Audio/Video Input jacks
- Unified TV/VCR remote
- Clock, Sleep-timer & on-timer (PAN-2796)

Sugg. Retail \$499.95 **SALE! \$357.95**

- Cameras
- Darkroom Supplies
- Video Equipment
- Televisions
- Hi-Fi Stereo Equipment
- Portable/Personal Audio
- Telephones
- Cellular Phones
- Computer Equipment
- Business Machines
- Calculators/Organizers
- Electronic Games
- Watches/Sunglasses
- Small Home Appliances
- Jewelry

Visit our superstores at:

**67 West 47th Street** **115 West 45th Street**  
Bet. 5th & 6th, NYC CA. LIC. #800189-691860 Bet. 6th & B way, NYC CA. LIC. #800191-81628

**1-212-921-1287**

Sun. 10:00-5:00, Mon-Thurs. 9:30-6:00, Fri. 9:30-2:00, Closed Saturday


**A New York Landmark for over 26 years!**

Toll-free line is open  
SUN. 10-5, DAILY 8-7, FRI. 8-2  
Local lines are open  
SUN. 10-5, DAILY 9:30-6, FRI. 9:30-2

**OVERNIGHT DELIVERY**  
to any point in the  
continental USA  
AVAILABLE  
at additional cost

Mall Order Dept.:  
455 Smith Street, Brooklyn, N.Y. 11231

EN1292

 

**TWO TRANSMITTERS IN ONE! 5 MINUTE ASSEMBLY! MONEYBACK GUARANTEE!** New Law Enforcement grade device on a single chip is the most sensitive, powerful, stable room transmitter you can buy. Uses any 3V-12V battery. Or attach to telephone line to monitor all telephone conversations over 1 mile away without batteries! 100mW output! 80-130MHZ. Receive on any FM radio or wideband scanner. VT-75 microtransmitter. \$49.95 + 1.50 S&H. VISA, MC, MO. COD's add \$4.00. **DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. 914-232-3878.**

CIRCLE 127 ON FREE INFORMATION CARD



**CABLE TV 50dB NOTCH FILTERS** for interference removal or channel censoring. Filters are user-adjustable to desired channel # or frequency. Eight Models available, each for certain channels: 2 & 3; 4 to 6; 7 to 13; 14 to 17; 18 to 22; 23 to 29; 30 to 36; 95 to 99 plus 0 & 1. Just \$30 each or 3 for \$75, includes shipping. **ONE MONTH MONEY BACK**, fast delivery. Visa, MC, check or M.O. (C.O.D. is \$5 extra) Huge discounts for higher quantities. **STAR CIRCUITS, P.O. Box 94917, Las Vegas, NV 89193. Call 24 hours 1-800-535-7827.**

## WHAT'S NEWS

continued from page 6

the development of table-top, laser-powered particle accelerators, as opposed to today's massive, expensive accelerators. Another potential use for supercharged laser beams is the development of an X-ray laser capable of observing the molecular and atomic action of living cells.

The secret to the record-breaking power levels is a technique called *chirped-pulse amplification*, in which laser pulses are first produced in short bursts of a fraction of a picosecond (about one trillionth of a second). The duration of the pulses is then stretched out about a thousand times before the pulses enter the laser's amplifier. After amplification, the pulse is compressed back to the original fraction of a picosecond burst.

The research teams' "ultimate goal," according to Jacques Coustant, department head at the Centre, "is to push the power of the beam to 1000 terawatts." **R-E**

## VIDEO NEWS

continued from page 8

HDTV service, since most major cable systems have channels to spare. It's easy to see the possibility of a pay channel carrying movies in widescreen near-theater definition, the way they were intended to be seen. In fact, HBO and other pay cable operators are excited over the prospect. The same is true of the proposed multi-channel direct satellite-to-home systems, such as Hughes Aircraft's DirecTV, which seem certain to earmark some channels for HDTV.

The real key to the equation lies with consumers. Will they be willing to pay \$2000 and up—perhaps way up—for the first HDTV sets when there is little or no programming? Test after test shows average viewers regard program content as more important than picture quality. A massive education job and some significant program pump-priming seem indicated if HDTV is to catch on in a faster time frame than color TV's 10 years. **R-E**



**CABLE TV CONVERTERS AND DE-SCRAMBLERS SB-3, TRI-BI, MLD, M35B, DRZ-DIC.** Call for catalog and price list. Special combos available. We ship COD. Quantity discounts. Call for pricing on other products. Dealers wanted. **FREE CATALOG.** We stand behind our products where others fail. One year warranty. **ACE PRODUCTS, 1-800-234-0726.**

CIRCLE 75 ON FREE INFORMATION CARD



**GET YOUR RECHARGE CATALOG FREE...EARN BIG \$\$ IN YOUR SPARE TIME**—All supplies and Do-It-Yourself kits with complete instructions available. Supplies cost from \$9.95 in qty and you can sell recharged toner cartridges for \$40.00 to \$55.00 each. Printers include HP LaserJet and Series II, Apple LaserWriter, QMS, etc. Canon PC-25 Copier also. **CHENESKO PRODUCTS, 2221 Fifth Ave., Suite #4, Ronkonkoma, NY 11779, 516-467-3205. FAX 516-467-3223, 1-800-221-3516**

CIRCLE 181 ON FREE INFORMATION CARD



**WORLD'S SMALLEST FM TRANSMITTERS!** New Surface Mount Technology (SMT) makes all others obsolete! XST500 Transmitter—powerful 3 transistor audio amplifier, transmits whispers up to 1 mile. XSP250 Telephone Transmitter—line powered, transmits conversations up to ¼ mile. Both tune 88-108 MHz. Easy to assemble **E-Z KITS** (SMT components pre-assembled to circuit board)! XST500—\$39.95, XSP250—\$29.95, VISA/MC. COD add \$5. **XANDI ELECTRONICS, 201 E. Southern Ave., Suite 111, Tempe, AZ 85282. 1-800-336-7389.**


CIRCLE 193 ON FREE INFORMATION CARD

## CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$940.00 per each insertion.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

Call 516-293-3000 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, ELECTRONICS NOW, 500-B Bi-County Blvd., Farmingdale, NY 11735.

FAX: 516-293-3115

 

**Science PROBE!** — the *only* magazine devoted entirely to Amateur Scientists! If you are fascinated by science in all its many forms . . . if you can't stay away from a microscope, telescope, calipers, or test tube — we invite you to share the wonders in every issue of **Science PROBE!** You will join a community of Amateur and Student Scientists who enthusiastically seek scientific knowledge or follow scientific pursuits for their own sakes and not merely as a profession.

Obtain your next issue of **Science PROBE!** by visiting a quality Newsstand, Convenience Store, or Supermarket or by reserving your personal copy through the mail by completing the coupon below.

From your very first issue of **Science PROBE!** you will be involved in a world of scientific facts, experiments, and studies pursued by amateur scientists who are university students, investors, academicians, engineers, or office workers, salesmen, farmers—whose *quest* is to probe into the mysteries of science and reveal them to all.

Plan to become a **Science PROBE!** reader!

# Welcome to . . .

# SCIENCE **PROBE!**<sup>®</sup>

The Amateur Scientist's Journal

Embark on an irresistible new journey into the realm of mystery, challenge, and exploration! The perfect magazine for the budding scientist, the serious amateur, the professional who would like to relax, and those who simply want to gaze at the stars.

Articles to appear in upcoming issues of **Science PROBE!** are:

**Inside Internet—A Scientific Computer Network**  
**Make your own Seismometer**  
**Operate a Solar-Powered Weather Station**  
**Assemble a Solid-State Portable Barometer**  
**The Bicycle—A Traveling Scientific Laboratory**

If you're fascinated by science in all its many forms, if you are compelled to experiment and explore, then **Science PROBE!** is your kind of magazine!

**For Faster Service—Call Today:**  
**1-800-777-5489**

**Science PROBE!**  
500-B Bi-County Boulevard  
Farmingdale, NY 11735

7RM26

Please forward my copy of **Science PROBE!** as soon as it comes off the press. I am enclosing \$3.95-U.S.A. (\$4.82-Canada-includes G.S.T.) plus \$1.00 for shipping and handling. Better still, please enroll me as a subscriber and send the next four (4) quarterly issues of **Science Probe**. I am enclosing \$11.95-U.S.A. (Canada: \$18.14—includes G.S.T.)

Next Issue Only       Next Four Issues (1 Year)  
Offers valid in the U.S.A. and Canada only. No foreign orders.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ ZIP \_\_\_\_\_

All Orders payable in U.S.A. Funds only.

**ON SALE AT QUALITY NEWSSTANDS, CONVENIENCE STORES AND SUPERMARKETS**  
**GET YOUR COPY TODAY—\$3.95-U.S.A.—\$4.50-Canada**

# BIG PROFITS IN VIDEO REPAIR!

WORK FROM HOME-EARN \$85 HR!

With the tens of millions of VCRs and Camcorders in use, there currently is a **serious shortage** of trained techs to perform cleaning and repair jobs on these popular devices...

Learn how you can start your own highly profitable, **Home-Based** video servicing business...

And since up to 95% of all VCR and Camcorder malfunctions are due to a simple **mechanical or electro-mechanical** failure, you need not spend months or even years of complicated study before starting **paid, professional service work!**

Let Viejo's Training Program show you how!

CALL TOLL-FREE **1-800-537-0589**  
or mail coupon today!

VIEJO PUBLICATIONS, INC.

4470-107 Sunset Blvd., Suite 600  
Dept. VK Los Angeles, CA 90027

Yes! Rush me your **FREE OPPORTUNITY KIT** today!  
(Check appropriate box)

- VCR Repair
- Camcorder Repair
- Advanced VCR Repair
- Fax Machine Repair

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City/State \_\_\_\_\_ Zip \_\_\_\_\_

Dept. RE

CIRCLE 192 ON FREE INFORMATION CARD

## Cable TV Article Parts

We stock the exact Parts & PC Board for an article published in Radio Electronics Magazine on building a Snooper Stopper.

Snooper Stopper Kit.....\$19.95

Includes all the original Parts & Etched, Drilled Silk-Screened PC Board.

Snooper Stopper.....\$39.00

This is an assembled and tested fixed frequency 106.5Mhz. Snooper Stopper for most Jerrald systems.

Protect yourself from descrambler detection and stop the Bullet with one of our Snooper Stoppers.

Macrovision..now you see it,  
now you don't.

Macrovision Kit.....\$29.00

Includes all the original Parts & Etched, Drill Silk-Screened PC Board. Originally Published in Radio Electronics Magazine.

Call Toll Free 1-800-886-8699

Visa, MasterCard or COD

Northeast Electronics, Inc.  
PO Box 3310  
N. Attleboro, Ma. 02761

CIRCLE 194 ON FREE INFORMATION CARD

## INRUSH CURRENT LIMITED

continued from page 50

 


FIG. 10—EXPLODED VIEW OF INRUSH-CURRENT limiter circuit in enclosure. Note the completion of ground within the case with a 3-wire power cord.

the completed circuit. Pull the three-wire cable through a grommet in the case sidewall as shown. Strip the jacket from the cable in the case, strip the end of the green ground wire, and connect it to the ground terminal of the three-prong receptacle. Solder one of the cable's conductors to the PC board, as shown, and solder the other conductor to one terminal of the switch.

Using short insulated lengths of the same cable conductor, solder a connection from the switch to the other side of the PC board, as shown. Solder two more short lengths of conductor to the output pads on the PC board, and connect their other

ends to the panel-mount receptacle.

Fasten the circuit assembly in the case with hold-down screws and close the cover. Fasten the cover in position with the four screws included. The inrush-current limiter then becomes a plug-in accessory and the host equipment need not be altered. The equipment's power switch should be clamped in the "on" position so that power to the equipment is then applied with the limiter's ON-OFF toggle or rocker switch.

Although the surge protector is in the circuit only for short time intervals, be sure that any protected equipment does not draw more than 2 amperes. R-E

# HARDWARE HACKER

Conventional currents, assorted wonderments, navigation and navicubes, FM Yagi antenna design, and two new piezo rate gyros.

DON LANCASTER

So many exciting new hacker opportunities have come down this month that I do not even know where to start. We seem to be moving into a boundless new era of hardware hacking.

Before we begin, though, there have been a few recent helpline calls over some really ancient history which we should go over one final time...

## Follow that current!

Which way does the current travel in any electrical or electronic circuit? Many years ago, one of the electrical pioneers ventured his wild guess that *electrical current always goes from the negative to the positive terminal in an energy source and from positive to negative in an energy sink.*

It took over a century to verify, but the guess turned out to be correct. At least for certain solid-state circuits, at least some of the time.

To this day, this guess is called the *conventional* electrical current, and appears in Fig. 1. Conventional current is the *only* standard taught in *all* university- and *all* graduate-level engineering courses, is used by *all* physicists, and is accepted by *all* large electronic firms worldwide.

Conventional current is shown in the direction of the arrows on *all* the standard electronic symbols. Even the IEEE tie clasp and cuff links strongly restates conventional current. So does the right-hand generator rule and left-hand motor rule.

Yeah, but just which way does the current *really* go? Well, a glib answer for the new age nineties is "any way you want it to."

In semiconductor loads, the current direction is decided by the majority carriers. In any PNP transistor or any P-channel MOSFET, conduction is by hole carriers, and the current does in fact go in exactly the same direction as the conventional

current. In N-type devices, the current is the opposite of the conventional current direction.

So what is the problem? And why am I standing here whipping this long-dead horse?

Way back during World War II, PNP vacuum tubes were very few and far between. Come to think of it, they still are. Because of that, the military introduced the concept of the *electron current* to explain how a vacuum tube works. And many trade schools and lower-level textbooks continued the practice into the fifties and sixties.

That led to the absurd result that a few hackers, technicians, and much of the hobby press had their currents heading in one way, while all of the engineers, physicists, and the rest of industry had their currents heading in the exact opposite direction.

The bottom line: If any individual or any textbook still tries to teach you electron current, they are ripping you off. They are also doing you a serious disservice that will lead you to untold confusion and latter day hassles.

*Neither* electron nor conventional current is correct all of the time. The overwhelming majority of industry and professional-level training *always* goes with the conventional current. Among the other reasons, because there is no compelling reason not to.

## NEED HELP?

Phone or write your **Hardware Hacker** questions directly to:  
Don Lancaster  
Synergetics  
Box 809  
Thatcher, AZ 85552  
(602) 428-4073

Just what would it take to convert industry over to electron current? For openers, extremely frigid conditions in a distinctly unpleasant locale. Or some words to that effect. Even then, I would not expect to see this happen until a few weeks after the Ayatolla's Bar Mitzvah.

## Navicube update

Way back in a July 1988 *Hardware Hacker*, we looked at the *Navicube*, a 3-inch, \$10 cube that always knew where it was and which way it was pointed. Well, we still don't have \$10 Navicubes, although I do expect some Korean toy manufacturer or two kids in an Iowa basement to come up with a really good one shortly.

A lot is happening with Navicubes, both evolutionary and revolutionary. An update summary of Navicube info appears as our resource sidebar.

Today's popular approaches to the Navicubes include the GPS satellite system, fluxgates, real gyros, laser gyros, accelerometers, and a pair of brand new piezo gyros.

The GPS global positioning system is going great guns. Their eighteenth satellite is now in orbit, and Russian and ECC competing systems are now being established. Receiver prices are in free fall, and the \$500 barrier has recently been broken.


*GPS World* is your foremost trade journal. Its publisher also just started up a new *GPS World Showcase* shopper. As before, the *Journal of the Institute of Navigation* is the finest Navicube technical resource.

Although *Rockwell* is still the most obvious source for the GPS chip sets, *Hewlett Packard* has just developed a new single-chip GPS front end. While it's too early for a part number, several details now appear in *Microwaves & RF* for August

The conventional current travels from **NEGATIVE to POSITIVE** in any **SOURCE**.



The conventional current travels from **POSITIVE to NEGATIVE** in any **LOAD**.

 

**FIG. 1—CONVENTIONAL ELECTRIC CURRENT** goes from negative to positive in any energy source and from positive to negative in any energy sink. This is *the standard* used by all graduate engineers and physicists, and in electronic symbols, and the industry worldwide. It even appears on the IEEE cufflinks.

1992. I expect cheap new GPS parts real soon now, from several obvious sources.

North sensing is best done using fluxgate magnetometers. Radio Shack has a cheap one in its car compass, and KVH sells expensive commercial units. We have seen several fluxgate construction projects, and references to them in those *Hardware Hacker II* reprints. Naturally, any magnetic sensor gets confused by nearby iron.

Many hackers still labor under the delusion that Hall-effect devices can be used as compasses. Well, possibly they can, but fluxgates are *thousands* of times more sensitive.

One exception is the very low cost *Dinsmore* magnetic compass sensor. Sadly, its best possible accuracy is a crude 22.5 degrees.

Solid-state accelerometers continue to drop in price, spurred on by newer automotive uses, especially airbags. While *Motorola* and *Micro Switch* are the largest suppliers, the better priced and more innovative sensors are now provided by *Analog Devices*, *SenSym*, *IC Sensors*, and *NovaSensor*.

Your two best accelerometer trade journals are *Measurement & Control* and *Sensors*.

Note that you could integrate (sum through time) any acceleration to get velocity, and then integrate velocity to get the position. There is one huge technical hassle with accelerometers, though—it's called the "t-squared" problem. Any bias or similar error in acceleration ultimately piles up as a position error that is proportional to time *squared*.

That means if you wait around long enough for your position, it is certain to be wrong. Accelerometers work best for short-term uses, when they can be repeatedly recalibrated or reset from some other standard every now and then.

Classic navigation is usually done by using mechanical gyros. They are nothing but rapidly spinning masses, comparable to a toy gyroscope. They can be costly, cumbersome, and often involve precision elements rotating at very high speeds. Gyros are available as surplus from

*Fair Radio Sales*, *Radio Research Instruments*, and *AST Servo Systems*. One current manufacturer is *Humphrey Products*.

Yes, there are laser gyroscopes. A coil of fiber-optic cable has coherent laser light beams routed through it in opposite directions which then can be phase compared. But not much seems to be happening here to drop the costs by the 1000:1 needed to make them a practical hacker tool. Good information on laser gyroscopes is available from the *IEEE Press* and from *SPIE*.

But our really big Navicube gyro news for this month involves a pair of brand new...

### Solid-state rate gyros

A *rate gyro* is a special gyroscope that can tell you how fast you are *turning*. By integrating your rate of turn, you can get your direction. By combining that with some separately measured velocity, you can find your present position. And there will be no t-squared problem, since no double integration is involved.

Traditional rate gyros are available from the sources of regular gyros we just looked at. A hackable and a low-cost fluidic rate gyro was made a few years back by Doug Garner at NASA. It used an airstream differential cooling a pair of thermistors. But not too much seems to have come of that approach either.

A pair of new solid-state rate gyros are now available. At least one of them promises to end up as a \$5 component. Because they both use vibrating piezo structures, it is not quite correct to say that they have no moving parts. But they certainly are simple and rugged single-piece units with no rotating parts or precision mechanisms.

The first unit is the *GyroChip* by *Systron Donner*, shown in Fig. 2-a. This is a pair of back-to-back tuning forks machined from a single piece of silicon. The phase of the output signal is determined by the *Coriolis* force caused by turning.

The second piezo gyro is that new *Gyrostar* by *Murata-Erie*, shown in Fig. 2-b. This is just a triangular piezo oscillator. The Coriolis force of rotation again changes the phase of the output signal in propor-

## NEW FROM DON LANCASTER

### HARDWARE HACKER STUFF

Hardware Hacker Reprints II or III	24.50
Midnight Engineering Reprints	18.50
Resource Bin Reprints	12.50
Incredible Secret Money Machine	18.50
CMOS Cookbook	24.50
TTL Cookbook	24.50
Active Filter Cookbook	24.50
Micro Cookbook vol I or II	19.50
Lancaster Classics Library	119.50

### POSTSCRIPT STUFF

Ask The Guru Reprints I, II or III	24.50
LaserWriter Secrets (Ile/Mac/PC)	29.50
PostScript Show & Tell	39.50
Intro to PostScript VHS Video	39.50
PostScript Beginner Stuff	39.50
PostScript Cookbook (Adobe)	16.50
PostScript Ref. Manual II (Adobe)	28.50
PostScript Program Design (Adobe)	22.50
Type I Font Format (Adobe)	15.50
LaserWriter Reference (Apple)	19.50
Real World Postscript (Roth)	22.50
PostScript Visual Approach (Smith)	22.50
Thinking in PostScript (Reid)	22.50
Undst PS Pgrmmg (Holtzgang)	29.50
The Whole Works (all PostScript)	349.50

### BOOK-ON-DEMAND STUFF

Book-on-demand resource kit	39.50
GENie PSRT sampler (Ile/Mac/PC)	39.50


FREE VOICE HELPLINE

VISA/MC


## SYNERGETICS

Box 809-RE  
Thatcher, AZ 85552  
(602) 428-4073

CIRCLE 219 ON FREE INFORMATION CARD

 

 (A) The Systron-Donner GyroChip is based on two coupled tuning forks. The Coriolis force from any rotation around the vertical axis changes the phase and amplitude of the synchronously demodulated output signal.



(B) The Murata-Erie GyroStar is based on carefully controlled vibration modes in a triangular piezo element. Any relative clockwise or counterclockwise rotation changes the phase and amplitude of the output signals.

**FIG. 2—NEW DEVELOPMENTS IN PIEZO RATE GYROS** should eventually lead to low cost Navicube solutions. A rate gyro tells you how fast you are now turning. Integrating the turn rate (summing through time) gives the present direction.

tion to the rotation rate. This new scheme looks ridiculously simpler and vastly more elegant than the GyroChip design.

While both of those breakthrough devices have the potential to become low-cost parts, samples today cost \$300 for Murata's GyroStar, and a ludicrous \$2000 for the GyroChip. Their support literature so far is also utterly dismal. But a new \$5 Hong Kong knockoff is just about certain to become quickly available.

#### Assorted wonderments

Continuing this month's stunning new developments, here is a double handful of great new stuff...

- **Image Striking**—Be sure to check out *Motion Imaging Processing: Striking Possibilities* in the August 1992 issue of *Advanced Imaging*. What we apparently have here is a unique new concept and toolset for video, movie, and multimedia editing.

Put one frame of a small image in

the upper left of your monitor screen. Next, move down one pixel and one pixel to the right, and then repeat the process for the next frame in the sequence. Continue until you have a diagonal smirp on down your screen, ending with a final full small image. While you are at it, show your sound amplitude for each frame along the top diagonal of the smirp.

What do you have? In one place and at one time, a display that lets you view the *temporal content* of a *time sequence* of multimedia or other video. In short, you can instantly look *forward or backward through time*, seeing the relationship between your current frame, its recent history, and its near future!

Looking at this "striking" concept in a slightly different way, say you had a few feet of movie film. Cut the individual images apart so they have no borders. Stack them up and look *sideways* at their top and left edges. Once again, in one place and

at one time, you can see what has happened and what is going to happen. An instant and real-time plot of images versus time.

Naturally, the edges will only show you wildly abstract colors or patterns. But, with practice, those patterns can easily be read for the scene, camera angle, panning, duration, sound sync, and much more.

A non-obvious application: Quickly finding a buried sequence in a humongous video data base. It is sort of the video equivalent to that ISAM, or *indexed sequential access method* long used in data bases.

The editing, tweening, scanning, high-speed access, and all the visual flow possibilities of this new scheme seem boundless.

- **Wavelets**—The onslaught continues. A second book is now available and titled *Ten Lectures on Wavelets* by Ingrid Daubechies and published by SIAM, shorthand for the *Society for Industrial and Applied Mathematics*. While it's a first-rate text, this is a very advanced math book that makes for rough reading by mere mortals.

A brief story on optical wavelet uses appears in the August 1992 issue of *Photonics Spectra*. All those optics folks sure do have it easy. They just dump a pile of crockery on the table, squirt some light through it, and they get instant real-time 2-dimensional *Fourier* or wavelet transforms. None of the old point-by-point computation nonsense for them.

An entire issue on optical wavelet transforms appears as the September 1992 issue of *Optical Engineering*. I have added #494 EMERGOP2.PS and #456 WAVELETS.PS to GENIE PSRT to go along with all the rest of our wavelet downloads. A complete list appears in Fig. 3.

- **Multilayer PC breakthrough**—I am still looking for a hacker solution that makes printed-circuit plated-through holes cheaply possible at home. Or some workaround that flat out does away with the need for through holes.

A major step in this direction has been taken by *Sheldahl*, whose new special adhesive lets you build ultra expensive multilayer boards out of

the cheaper double-sided ones. Sadly, you still need some plate-throughs.

Their *Zlink 1900* is basically a new adhesive that conducts only in its thickness direction. Just take a pair of double-sided boards and selectively apply the adhesive to one of them. You then add heat and pressure to bond the pair together. You can end up with either a three- or a four-layer board at a tiny fraction of the going price. And, yes, you can do six layers, eight layers, or as many as you want. You can even have buried plated-through holes! Far simpler, cheaper, and with a much lower scrap rate than before.

Carefully isolated solder particles make the adhesive conduct in only one direction with conductivity about the same as real multilayer conductors.

A small free sample is available from Sheldahl on request.

● **Buckyballs**—The price of Buckyballs continues to drop dramatically, and they are now hacker-affordable. The leading supplier remains *MER Inc.*, and their pricing starts as low as \$5.50 a gram raw, and \$90 per gram fully refined. Minimum order is \$50.

Meanwhile, a *fourth* carbon form has been discovered that is called the *Buckytube*: hollow cylindrical pipes of carbon that have both the hardness of diamond and the surface area of graphite. Possible new uses include their use as lubricants, and unique materials that conduct heavily in only one direction. Check out the August 17 issue of *E.E. Times* for a summary update.

### More on FM antennas

Last month, we checked into the fundamentals of distant FM reception. We have had some requests for still more information, so here goes...

The noise situation at 100 MHz is a tad further complicated than I first made out. If you do have any remote rural site, then your first-stage KTB thermal agitation noise does, in fact, dominate. And the best noise figure you can get is super important.

Atmospheric noise is negligible at FM frequencies. Galactic noise runs ten decibels or so above KTB,

## NAMES AND NUMBERS

### Advanced Imaging

445 Broad Hollow Rd Ste 21  
Melville, NY 11747  
(516) 845-2700  
CIRCLE 316 ON FREE INFORMATION CARD

### Anixter

8101 E Prentice #210  
Englewood, CO 80111  
(303) 740-8949  
CIRCLE 317 ON FREE INFORMATION CARD

### Channel Master

33 Gaylord Road  
St Thomas, Ont, CAN N5P 3R9  
(519) 631-0320  
CIRCLE 318 ON FREE INFORMATION CARD

### Cushcraft

PO Box 4680  
Manchester, NH 03108  
(603) 627-7877  
CIRCLE 319 ON FREE INFORMATION CARD

### EE Times

600 Community Drive  
Manhasset, NY 11030  
(516) 365-4600  
CIRCLE 320 ON FREE INFORMATION CARD

### GEnie

401 N Washington Street  
Rockville, MD 20850  
(800) 638-9636  
CIRCLE 321 ON FREE INFORMATION CARD

### Heartland America

6978 Shady Oak Road  
Eden Prairie, MN 55344  
(800) 229-2901  
CIRCLE 322 ON FREE INFORMATION CARD

### MER, Inc

7960 South Kolb Road  
Tucson, AZ 85706  
(602) 574-1980  
CIRCLE 323 ON FREE INFORMATION CARD

### MX-Com Inc

4800 Bethania Station Road  
Winston-Salem, NC 27105  
(800) 638-5577  
CIRCLE 324 ON FREE INFORMATION CARD

### Optical Engineering

1022 19th Street, Box 10  
Bellingham, WA 98227  
(206) 676-3290  
CIRCLE 325 ON FREE INFORMATION CARD

### Photonics Spectra

PO Box 4949  
Pittsfield, MA 01202  
(413) 499-0514  
CIRCLE 326 ON FREE INFORMATION CARD

### Play Meter

PO Box 24970  
New Orleans, LA 70184  
(504) 488-7003  
CIRCLE 327 ON FREE INFORMATION CARD

### RePlay

22157 Clarendon Street  
Woodland Hills, CA 91365  
(818) 347-3820  
CIRCLE 328 ON FREE INFORMATION CARD

### Sheldahl

PO Box 170  
Northfield, MN 55057  
(507) 663-8000  
CIRCLE 329 ON FREE INFORMATION CARD

### Soc Industrial & Applied Math

3600 University City Science Ctr  
Philadelphia, PA 19104  
(215) 382-9800  
CIRCLE 330 ON FREE INFORMATION CARD

### Synergetics

Box 809  
Thatcher, AZ 85552  
(602) 428-4073  
CIRCLE 331 ON FREE INFORMATION CARD

### Victory Engineering

Box 559, Victory Road  
Springfield, NJ 07081  
(201) 379-5900  
CIRCLE 332 ON FREE INFORMATION CARD

### Winegard

3000 Kirkwood Street  
Burlington, IA 52601  
(319) 754-0600  
CIRCLE 333 ON FREE INFORMATION CARD

around 100 MHz. But you do not normally point an FM antenna straight up on a clear day, so this is also no problem. The potential killer is the manmade noise, which can be 25 decibels above KTB in suburban locations, and 40 decibels or more in urban locations. Nearby dimmers or computers could also induce

those noise levels.

Most of the manmade noise comes from car ignitions. It sure would be interesting to watch the FCC try to enforce the same Part 15 rules and regulations on Detroit iron that they do on Hardware Hackers. Talk about potential noise levels! The howl over this would probably



**#508 HACK58.TXT & #509 HACKFG58.PS**

Reprint of *Hardware Hacker #58* from *Electronics Now*. Wavelets update includes optical applications, and new *Ten Lectures on Wavelets* book.

**#494 EMERGOP2.PS**

Reprint of *Blatant Opportunist #17* from *Midnight Engineering*. Wavelets are one of the eight hacker-friendly emerging tech opportunities reviewed.

**#456 WAVELETS.PS**

Reprint of *The Wavelet Onslaught* from the *Midnight Engineering Companion #2*. Brief summary on wavelets and a key resource bibliography.

**#403 PAK251.EXE**

Utility to unPAK an IBM \*.PAK\* file, such as #385 WAVELET.PAK

**#390 HACK50.TXT & #391 HACKFG50.PS**

Reprint of *Hardware Hacker #50* from *Radio-Electronics*. Wavelets update, including new book, IEEE-SP tutorial, *Aware* application notes.

**#373 HACK49.TXT & #374 HACKFG49.PS**

Reprint of *Hardware Hacker #49* from *Radio-Electronics*. Mentions *Wavelets and their Applications* book and *Ultrawave Explorer* software from *Aware*.

**#365 WAVELET.PAK**

Complete and ready-to-run IBM Wavelet Packet Lab shareware. This is a .PAK compressed file that needs file #403 or its equivalent for unpacking.

**#313 GURU73.TXT & #314 GURUFG73.GPS**

Reprint of *Ask the Guru #73* that discusses three video compression schemes. These include wavelets, DCT/JPEG, and fractal compression methods.

**#258 HACK42.TXT & #259 HACKFG42.PS**

Reprint of *Hardware Hacker #42* from *Radio-Electronics*. Fundamentals of transforms, along with examples of wavelet video compression.

**#195 HACK38.TXT & #197 HACKFG38.GPS**

Reprint of *Hardware Hacker #38* from *Radio-Electronics*. A first introduction to wavelets and wavelet theory. Includes 13 entry sampler bibliography that shows the wide extent of wavelet aps.

**FIG. 3—WAVELET TUTORIALS AND SHAREWARE available on GENie PSRT. You can call (800) 638-9636 for your voice-connect info.**

be unbearable.

At any rate, you'll still want to get the best first-stage noise figure you can. But it might not help you out too much if your external noise is much stronger than KTB. On the other hand, a slight increase in antenna gain can make a dramatic improvement in your FM reception.

That happens because of a limiter's *capture effect*. For instance, if you've got a noisy FM signal, an increase of only two decibels in antenna gain or S/N ratio can make up to a *seven or eight* decibel improvement in receiver quieting.

I've found several interesting FM antennas. The Radio Shack 15-1636 is cheap at \$17 and easy to find. And it does a good job in near-fringe areas. But it is just plain too small. It measures only four feet by five feet, while a no-compromise Yagi solution will measure five by thirteen.

Radio Shack used the broadband co-linear array, rather than a Yagi

design. Then, to save on the materials and size, they apparently designed it up at 120 megahertz or so and hoped there was still some gain down in the FM band. Almost always, a broadband antenna has lower gain than one cut for a single station. From their point of view, this is a useful engineering mix that gives you a small and cheap solution which meets the needs of a majority of their customers. Their gain is 6.4 dB over a dipole.

The most rugged "real" FM DX antenna is the *Cushcraft Y-FM5*. This is available by way of *Anixter*, the leading cable TV distributor chain. The gain is 9.5 decibels over a dipole, and the cost is around \$70. Size is 59 by 104 inches.

Another interesting antenna is the *ChannelMaster 4408* with a 9-decibel gain in a 138-inch boom length. The price seems high at \$104.

The highest-gain stock antenna I

## DIGITAL VIDEO STABILIZER

ELIMINATES ALL VIDEO COPYGUARDS



While watching rental movies, you will notice annoying periodic color darkening, color shift, unwanted lines, flashing or jagged edges. This is caused by the copy protection jamming signals embedded in the video tape, such as Macrovision copy protection. THE DIGITAL VIDEO STABILIZER: RXII COMPLETELY ELIMINATES ALL COPY PROTECTIONS AND JAMMING SIGNALS AND BRINGS YOU CRYSTAL CLEAR PICTURES.

**WARNING**

THE DIGITAL VIDEO STABILIZER IS INTENDED FOR PRIVATE HOME USE ONLY. IT IS NOT INTENDED TO COPY RENTAL MOVIES OR COPYRIGHTED VIDEO TAPES THAT MAY CONSTITUTE COPYRIGHT INFRINGEMENT.

**FEATURES**

- Easy to use and a snap to install
- State-of-the-art Microchip technology
- 100% automatic
- Compatible to all types of VCRs and TVs
- The best and most exciting Video Stabilizer in the market
- Light weight (8 ounces) and compact (1x3.5x5")
- Uses a standard 9 Volt battery (last 1-2 years)
- Fast UPS delivery
- Air shipping available
- UNCONDITIONAL 30 day money back guarantee
- 1 year warranty

(Dealers Welcome)  
**FREE 20P Catalog**

To Order: \$59.95 ea. +\$4 for p & h  
Visa, M/C, COD Mon-Fri: 9-6 EST

**1-800-445-9285**  
ZENTEK CORP. DEPT. CRE12

3670-12 WEST OCEANSIDE RD. OCEANSIDE, NY 11572

CIRCLE 195 ON FREE INFORMATION CARD

## CABLE TV DESCRAMBLERS

How You Can Save Money on  
Cable Rental Fees

**Bullet Proof**

1 Unit 5+

**BEST Super Tri-Bi Auto/  
Var. Gain Adjustment \$119.95...\$85**  
Jerrold Super Tri-Bi... \$109.95...\$79  
Scientific Atlanta... \$109...\$79  
Pioneer... \$109...\$79  
Panasonic TZPC145... \$99.95...\$79  
Stargate Converter... \$95...\$69  
Digital Video Stabilizer... \$59.95...\$29  
Wireless Video Sender... \$59.95...\$49.95

**US Cable'll Beat  
Anyone's Price  
Advertised in  
this Magazine!**

**30 Day Money Back Guarantee**  
**FREE 20 page Catalog**

Visa, M/C, COD or send money order to:  
**U.S. Cable TV Inc. Dept. KRE12**  
4100 N. Powerline Rd., Bldg. F-4  
Pompano Beach, FL 33073

**1-800-772-6244**

For Our Reader

I, the undersigned, do hereby declare under penalty of perjury that all products purchased, now and in the future, will only be used on Cable TV systems with proper authorization from local officials or cable company officials in accordance with all applicable federal and state laws. FEDERAL AND VARIOUS STATE LAWS PROVIDE FOR SUBSTANTIAL CRIMINAL AND CIVIL PENALTIES FOR UNAUTHORIZED USE.

Date: \_\_\_\_\_

Signed: \_\_\_\_\_

**No Florida Sales!**

CIRCLE 196 ON FREE INFORMATION CARD

# FREE Heathkit

Educational Systems

Electronics & Computer Software  
Education Catalog

- \*Fast-Track Individual Learning Programs
- \*State-of-the-Art Classroom Courses
- \*The Best Values in Electronics Education Today

New

Computer Aided Instruction

DC Electronics  
AC Electronics  
Semiconductors  
Electronic Circuits

The stunning animations, hypertext glossary, and easy-to-understand text make learning the concepts of electronics a breeze...and fun!

Learn Electronics the easy and affordable way from the Masters in Electronics Training - Heathkit Educational Systems. From Basic Electricity and Electronics to Advanced Microprocessor Applications and much more, Heathkit will provide you with an unparalleled learning experience at a fraction of the cost of other programs.

For your FREE Catalog, call  
**Toll-Free 1-800-44-HEATH**  
please mention this code when calling 020-004

CIRCLE 86 ON FREE INFORMATION CARD



Save on cable rental fees!

**CABLE TV  
DESCRAMBLERS  
WE'LL BEAT  
ANY PRICE**

JERROLD-TOCOM-ZENITH  
HAMLIN-OAK-PIONEER  
SCIENTIFIC ATLANTA

- 24 HOUR SHIPMENTS!
- MONEY BACK GUARANTEE!
- QUANTITY DISCOUNTS!

MASTER CARD / AMEX / VISA / C.O.D.



Have make and model number of  
equipment used in you area ready.

CALL TOLL-FREE

**1-800-284-8432**

**CABLE WAREHOUSE**

10117 West Oakland Park Blvd.,  
Suite 515, Sunrise, FL 33351

NO FLORIDA SALES

CIRCLE 183 ON FREE INFORMATION CARD

## NAVICUBE RESOURCES

### Analog Devices

PO Box 9106  
Norwood, MA 02062  
(617) 329-4700  
CIRCLE 334 ON FREE INFORMATION CARD

### AST Servo

115 Main Road, Box 97  
Montville, NJ 07045  
(201) 335-1007  
CIRCLE 335 ON FREE INFORMATION CARD

### FW Bell

6120 Hanging Moss Road  
Orlando, FL 32807  
(407) 678-6900  
CIRCLE 336 ON FREE INFORMATION CARD

### Dinsmore Instruments

1814 Remell Street  
Flint, MI 48503  
(313) 744-1330  
CIRCLE 337 ON FREE INFORMATION CARD

### Fair Radio

PO Box 1105  
Lima, OH 45802  
(419) 227-6573  
CIRCLE 338 ON FREE INFORMATION CARD

### GPS World

PO Box 10460  
Eugene, OR 97440  
(503) 343-1200  
CIRCLE 339 ON FREE INFORMATION CARD

### Hewlett-Packard

PO Box 10301  
Palo Alto, CA 94303  
(415) 857-1501  
CIRCLE 340 ON FREE INFORMATION CARD

### Humphrey

9212 Balboa Avenue  
San Diego, CA 92123  
(619) 565-6631  
CIRCLE 341 ON FREE INFORMATION CARD

### IC Sensors

1701 McCarthy Blvd  
Milpitas, CA 95035  
(408) 432-1800  
CIRCLE 342 ON FREE INFORMATION CARD

### IEEE Press

445 Hoes Lane  
Piscataway, NJ 08855  
(908) 981-0060  
CIRCLE 343 ON FREE INFORMATION CARD

### Journal of Navigation

1800 Diagonal St Ste 480  
Alexandria, VA 22314  
(703) 683-7101  
CIRCLE 344 ON FREE INFORMATION CARD

### KVH Instruments

110 Enterprise Center  
Middletown, RI 02840  
(401) 847-3327  
CIRCLE 345 ON FREE INFORMATION CARD

### M&C

2994 W Liberty Avenue  
Pittsburgh, PA 15216  
(412) 343-9666  
CIRCLE 346 ON FREE INFORMATION CARD

### MicroSwitch

11 W Spring Street  
Freeport, IL 61032  
(815) 235-6600  
CIRCLE 347 ON FREE INFORMATION CARD

### Microwaves & RF

611 Rt #46 West  
Hasbrouck Heights, NJ 07604  
(201) 393-6286  
CIRCLE 348 ON FREE INFORMATION CARD

### Murata

2200 Lake Park Drive  
Smyrna, GA 30080  
(800) 831-9172  
CIRCLE 349 ON FREE INFORMATION CARD

have found is the *Winegard* CA-6065; it has a whopping 10.6 decibels of gain on a 127-inch boom and costs around \$78. This appears to be the best choice.

Be sure to remember that raising your antenna height is usually the best way to improve the signal-to-noise ratio in typical locations. The closer to line of sight you can get, the better the results.

But I live in a pecan grove. Nuts. My trees glop over everything, most especially antennas. So some indoor solution seemed better for me.

What about building your own single-station FM antenna? In theory, you could pick up another decibel or two of S/N and as much as 8-10 dB of quieting over full-band commercial designs. Especially if you are extra careful in tuning and matching. And if you have a high loft in your living room or a wire- and metal-free attic crawl space, an indoor design can be much cheaper than a mast-mounted outdoor one—with fewer hassles. And a Yagi is just a bunch of free-floating conductors sitting in magic positions; a wood frame and

### NASA Tech Briefs

41 E 42nd Street Ste 921  
New York, NY 10017  
(212) 490-3999  
CIRCLE 350 ON FREE INFORMATION CARD

### Nova Sensor

1055 Mission Court  
Fremont, CA 94539  
(415) 490-9100  
CIRCLE 351 ON FREE INFORMATION CARD

### Radio Research Instruments

584 North Main Street  
Waterbury, CT 06704  
(203) 753-5840  
CIRCLE 352 ON FREE INFORMATION CARD

### Rockwell

PO Box 568842  
Dallas, TX 75356  
(214) 996-5863  
CIRCLE 353 ON FREE INFORMATION CARD

### Sensors

174 Concord Street  
Peterborough, NH 03458  
(603) 924-9631  
CIRCLE 354 ON FREE INFORMATION CARD

### SenSym

1255 Reamwood Avenue  
Sunnyvale, CA 94089  
(408) 744-1500  
CIRCLE 355 ON FREE INFORMATION CARD

### SPIE

PO Box 10  
Bellingham, WA 98227  
(206) 676-3290  
CIRCLE 356 ON FREE INFORMATION CARD

### Systron Donner

2700 Systron Drive  
Concord, CA 94518  
(800) 227-1625  
CIRCLE 357 ON FREE INFORMATION CARD

grommated screw eyes can be used for support.

First, note that there are two styles of driver elements to a Yagi antenna. As Fig. 4 shows, if you use a half-wavelength *dipole* hairpin loop, the terminal impedance should end up near a balanced 300 ohms.

If you use a pair of straight wires of half-wavelength total spacing, then your terminal impedance should be a balanced 75 ohms. Note that normal 75-ohm coaxial cable is unbalanced; you will need a

balun or a 1:1 transformer to go from balanced to unbalanced.

Note that driver impedances inside an antenna array usually end up *lower* than those values. They also must be carefully matched for best results.

The bottom line: use a hairpin loop for 300 ohms balanced or the pair of quarter-wave wires when you want 75 ohms balanced. Either way, a final matching will still be needed.

A six-element narrowband Yagi cut for 100 megahertz is shown in Fig. 5. Use quite *thin* but rigid conductors for the best narrowband gain. Something like *bare* 12 AWG solid copper house wire might be a good choice. To cut the antenna to your desired station, *divide* the frequency in megahertz by 100, and then *divide* all sizes by the resultant number. For instance, to pick up KDKB at 93.3 MHz, all element lengths and all spacings will get divided by 0.933. Note the inverse relationship: stations *under* 100 MHz need slightly *larger* antenna designs.

The directors should point towards your chosen station. Use a map for starters, and then try rotating a tad either way. Your beamwidth should be around thirty degrees, so pointing in just the right direction is super important.

Additional directors can, in theory be added, in a size progression. But all you gain is something like half a decibel per director, and the size does get out of hand real quick. And a careful match, or finding a local hot spot, or a tad extra height can often get you much more signal.

The theory behind a Yagi antenna? The optimum spacing is usually 0.2 wavelengths. The driver should be half a wavelength wide. The reflector should be around five percent longer, while the initial director should be five percent shorter. The rest of the directors should be progressively six, seven and, eight... percent shorter.

More on Yagi antennas appears in two ARRL publications, the *Antenna Handbook* and *Yagi Antenna Design*. Also see NBS technical note No. 688.

Close matching of an antenna to its transmission line is essential for the best gain. The simplest method

# Be an FCC LICENSED ELECTRONIC TECHNICIAN!



No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radiotelephone License." This valuable license is your professional "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Maritime, Radar, Avionics and more...even start your own business! You don't need a college degree to qualify, but you do need an FCC License.

**No Need to Quit Your Job or Go To School**  
This proven course is easy, fast and low cost! **GUARANTEED PASS**—You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

## COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 90  
P.O. Box 2824, San Francisco, CA 94126  
Please rush FREE details immediately!

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

## SUPER 12 HOUR RECORDER CALL TOLL FREE

Modified Panasonic Slimline,  
6 hrs per side  
120 TDK tape furnished.  
AC/DC Operation.  
Quality Playback.  
Digital Counter.  
Durable Lightweight Plastic.



**\$119.00\***

## PHONE RECORDING ADAPTER

Starts & Stops Recorder  
Automatically When  
Hand Set is Used.  
Solid State!



FCC Approved

**\$28.50\***

## VOX VOICE ACTIVATED CONTROL

Solidstate Adjustable  
Sensitivity. Voices &  
Sounds Activate Recorder  
Adjustable Sensitivity  
Provisions for Remote  
Mike




**\$28.50\***


\* Add for ship. & handling. Phone Adapter & Vox \$2.00 each, Recorders \$5.00 each. Colo. Res add tax. Mail Order, VISA, M/C, COD's OK. Money Back Guar. Qty Disc. available. Dealer inquiries invited. Free data on other products.

AMC SALES INC. 193 Vaquero Dr.  
Boulder, CO. 80303  
Phones (303) 499-5405 1-800-926-2488  
FAX (303) 494-4924  
Mon-Fri 8-5 MTN. TIME

CIRCLE 108 ON FREE INFORMATION CARD

 

 (A) An ordinary dipole has an impedance of a balanced 75 ohms resistive just below its resonance. But any thick conductors or nearby elements lower this resistance or add some unwanted series reactance.



(B) Folding a dipole into a hairpin loop will raise its input impedance by four times. The impedance just below half of a wavelength is a balanced 300 ohms resistive. Careful tuning is needed in the real world.

FIG. 4—FOLDING A DIPOLE can raise its resonant impedance by a factor of four.

All dimensions are shown in decimal inches. The antenna is shown top view, and assumes the station is horizontally polarized.

To cut your antenna for a specific station, divide the station frequency by 100 and then divide all sizes shown below by the same value.

For instance, a 93.3 Mhz station needs all the values divided by 0.933. A 104.5 Mhz station needs all of the values divided by 1.045.

 


FIG. 5—AN INDOOR SINGLE-STATION long-distance FM antenna can be built using nothing but bare 12 AWG house wire. Here is one possible design. Note that the antenna size should be "cut" for your favorite station. Values shown assume an insulated boom or other supports. All elements must be very straight, rigid, parallel, and precisely centered. Contact a local radio ham for help in matching.

is called a *gamma* match, and it is done by just spreading the ends of a 300-ohm twinlead to tap maximum

signal strength. Better methods appear in the books mentioned.

It would be real interesting to

route both of your dipole rods straight into a VHF differential amplifier. Such an *antennafier* can greatly simplify tuning and matching. But a lot of black magic could be involved, so be sure to experiment.

Let me know all your experiences with any homemade ultra-range FM antenna designs. I'll try to publish the best of them.

### New tech lit

A green 1991 *Product Handbook* from *MX-Comm*. This little-known semiconductor house offers all sorts of exciting hacker chips, especially those involved with tone signalling, speech scrambling, cellular phones, and pagers. One real sleeper: *MX-Comm's* MX009 octal digital gain-controlled amplifier array. Lots of application-notes are also included.

Free engineering samples of its new 41VHS-1 humidity sensor have been offered on professional request from *Victory Engineering*.

*Heartland America* is yet another Distressed Yuppy Surplus direct-mail outfit. It has all varieties of high-tech goodies. Its latest new catalog does offer the first laser pointers that I have seen selling for less than \$100.

*RePlay* and *Play Meter* are the two leading trade journals for the coin-operated video-game industry. While they mostly concentrate on the buying and selling of games and supply products, there are occasional technical articles plus repair books and videos.

If you are interested in starting up your own tech venture, be certain to check into my at long last available *Incredible Secret Money Machine II*. We have also begun shipping the latest *Hardware Hacker III* reprints with their newest updates. See my nearby *Synergetics* ad for more details.

A reminder here that lots of great technical downloads are available on *GENIE* PSRT.

As usual, we've gathered many of the resources mentioned together into either the *Names & Numbers* or the *Navicube Resources* sidebars. Do be sure to check these out *before* you use our no-charge tech helpline or call for a free hacker secrets brochure.

R-E

## GLITTER GLOBE

continued from page 40

 


FIG. 10—BOTH SIDES OF THE CONTROL BOARD are shown with only level 1 attached (top and middle), and levels 1-4 have been added in the bottom photo.

After testing the controller board, assemble the five boards of the first level. (A "1" is etched on each of them.) Assemble the level-1 boards into a ring shape using resistors R14-R18, which should already be bent to the proper length— $\frac{1}{2}$  or  $\frac{3}{4}$  inches (see Fig. 7). Creating the top ring in that manner will set the proper spacing for the rest of the globe. Leave the top hole on each level-1 board open (the hole

farthest from the number etched on the inside surface), for connecting level 1 to the globe's control board.

Figure 7 is a "component map," showing levels 1-4, and how they connect together. All connections marked "J" are zero-ohm jumpers; all connections showing a resistor symbol must be 680 ohms, and all unmarked connections are structural components and can be

made from anything you like (the kit includes additional 680-ohm resistors for use in these locations). Connect the level-1 ring to the control board as shown in Fig. 8; if you are using  $\frac{3}{4}$ -inch spacing, level 1 mounts as shown in Fig. 8-a; for  $\frac{1}{2}$ -inch spacing, level 1 mounts as shown in Fig. 8-b. To connect level 1, install five 1-inch leads rising vertically from the control board. Then bend them to fit the level-1 ring as shown in Fig. 8.

Next add the level-2 boards. Each level-2 board connects to level 1 with one resistor (R19-R23) and one zero-ohm jumper. Solder the resistor and jumper to each level-2 board first, and then attach them to level 1. While building the globe, you'll begin to notice patterns. For example, after level 2 is complete each new board (except for level 7) connects to the previous level with two resistors (one structural only), and one zero-ohm jumper.

Figure 9 shows the rest of the globe (levels 5-7). Note that Figs. 7 and 9 both show the outside surface of the globe. The letters surrounding each half of the globe in Figs. 7 and 9 indicate the connections between the two halves. Install each level in order from 1 to 7 (even though we have shown the globe in two halves).

Layer 2 is composed of five-point boards, so, to make a sphere, keep the lead spacing of the resistors and jumpers attached to all layer-2 boards at  $\frac{5}{8}$  inch. It's a good idea to plug in the globe after each layer is installed to make sure all LED's are working. It's best to repair errors early before they become difficult to correct. Continue adding each layer and testing the globe until it's finished. Figure 10 shows a globe in different stages of construction.

When complete, the Glitter Globe forms a surprisingly sturdy structure, and you can hold it while it's operating. If the globe is dropped or crushed, it is a simple matter to bend it back into shape. With reasonable care, it will last for decades to come.

R-E

# Your Holiday EL

*HOLIDAY SPIRIT* is your complete headquarters for surviving the holidays! Whether you need tips on the latest technology in sound systems, televisions or video games, Holiday Spirit will provide the latest information on electronic technology that will be just in time for



Audio Amplifier for your older teenagers and Royal Appliance's Dirt Devil for mom. For those looking for high fidelity, Holiday Spirit will profile the Bose Lifestyle Music System for listening to Christmas carols and will showcase Hitachi's Ultravision Big Screen Televi-



the holiday season.

Hosted by Spencer Christian, American's favorite weatherman, *Holiday Spirit* is a series of three, one hour television specials that guide Americans through their favorite holidays: Thanksgiving, Christmas-Hanukkah and New Year's.

Innovative electronic technologies are thriving in the 90's. An array of new technologies are unveiled every holiday season, increasing consumer confusion on how to choose the latest electronic gifts.

*Holiday Spirit* will look at the latest gifts; including Metrosound's Malibu 100 Car



sion for watching the New Year's bowl games like never before.

*Holiday Spirit* has valuable tips and information for everyone. For the youngsters in the family, Sunsoft's Road Runner's Death Valley Rally will be the latest Nintendo game to fill their stockings. For music lovers who

# Electronics Center

---



ing? *Holiday Inn* will give you a comfortable, affordable place to stay with the family.

Last year, you thought you had enough time to shop, you thought you bought the right brands, you thought you called every relative. This year, if you think you can't get everything



saving tips and gift recommendations.


Check your local TV guide for times and dates.

demand accurate and natural music reproduction, *Holiday Spirit* will feature Ohm Walsh 5 Loud Speakers for full room stereo sound.

Need a gift for the handyman or professional tradesman? *Snap-On Tools* Ratcheting Screwdrivers are fast, easy to use, and are economically sound. Travel-



 finished in time, *Holiday Spirit* will show you how to have "Happy Holidays" with time-



*HOLIDAY SPIRIT*  
A Brookstone Production

# DRAWING BOARD

## Let's get back to our SSAVI descrambler.

ROBERT GROSSBLATT

**B**efore we get into the nitty gritty of the SSAVI system, I have to take a few lines to make a few things clear. I've touched on them before, but it's important to repeat them. All we've gone into so far is gated sync suppression, which can be considered pretty unsophisticated these days.

The SSAVI system isn't the last word in scrambling but it's reasonably recent and it, or some variation of it, will be the scrambling system of choice for some time to come. That is true even if you consider only the economic side of changing scrambling methods.

I have no doubt that many cable companies use this scrambling technique, or at least something very similar. If that's true in your area, it would be a good idea to do some experimenting with the actual signal—hands-on experience is always the best. What you'll probably find out in the real world is that the system used in your area isn't an exact match for the one we'll be taking apart. The general principles might be the same, but the particular details will undoubtedly vary.

When the SSAVI system first started, there were some constants in the video signal that could be used to descramble it. Remember that the picture can be messed up in any one of three ways (see October's column for the details), and the instructions for the descrambler are transmitted somewhere in the vertical interval. The word "somewhere" is a late addition to the SSAVI system. When it first started, the descrambling information was always on the same line. That's where we'll start.

Once upon a time, the sanctity of the vertical interval was closely guarded by the FCC, but as alternatives to standard broadcast TV

became more popular (cable, satellite, etc), more and more junk started to show up there.

When the SSAVI system started, lines 0 to 9 were left alone by a request of the FCC, but lines 10 to 13 were where the cable companies transmitted individual subscriber codes. Don't forget that there are unique ID numbers stored in an EPROM (or some other kind of memory) in the cable box. There's also logic circuits there to count the video lines, read the transmitted code, and match it up against the one stored in the box. This is a big thing for the cable companies because it prevents a New York box from being used in California. The scrambling is the same, but the codes are completely different.

The decoder circuitry is also controlled by this coding process because a match between the

transmitted bytes and the ones stored in the box will enable or disable the decoder. That is true for both the premium cable services and the pay-per-view events.

That kind of coding might be important to the cable companies, but it doesn't mean anything to us. We can build an experimental descrambler without paying any attention to them.

Since the video can be transmitted with either normal or inverted picture information, one of the tasks that has to be done by the descrambler is to tell the rest of the circuit what has been done to the picture. The place to find that information was originally in line 20, but it has been moved around since the system became popular. As you can see in Fig. 1, the last half of the line will tell you whether the picture is normal or inverted. Remember that

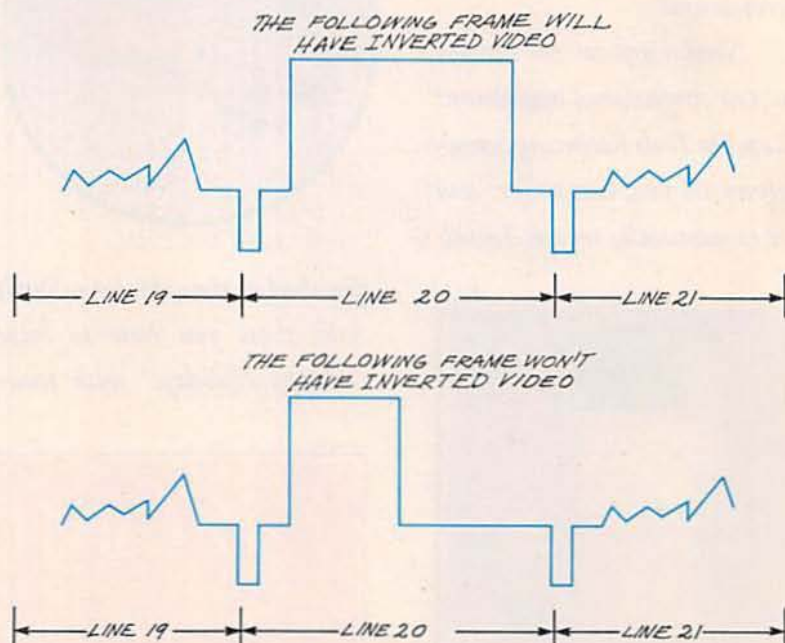


FIG. 1—THE LAST HALF OF THE LINE OF VIDEO will tell you whether the picture is normal or inverted. We're talking about the picture part of the line only.



we're talking about the picture part of the line only, and not the control section.


If the following field is normal, the last half of the line will be black, and if the picture is normal, the whole line is white. One of the things a decoder needs, therefore, is some way to detect the line and store the data it contains. The stored data is then used as a switch by the circuit to route the video through an inverter if the picture is being transmitted upside down.

This is pretty straightforward stuff. Since we're looking at only one piece of information, all we need is a place to store one bit of information. Your basic piece of cake. The circuitry needed to detect the data, however, is a bit more complex. We need a reference in the signal. So establish a zero point for a line counter, and some counting circuitry to keep track of which line is being received.

You might be wondering what we can count if the signal is being scrambled. But remember, that in the vertical interval (the first 26 lines of video), the signal is being sent in the clear.

Now that we have an approach to handling the possibility of an inverted picture, the last problem to tackle is the one of varying horizontal sync pulses. Sometimes they're there, sometimes they're absent, and sometimes they're not at the proper level. Anything that unstable is a pretty poor choice for a reference signal. So, to avoid a mammoth circuit design problem, the best way to deal with it is to scrap the transmitted horizontal sync (even when it's there), and come up with a way to generate the signal ourselves.

That can also seem to be an insurmountable problem but, just as in the case of the inverted picture, the answer is going to be found in the vertical interval. Once again, remember that the first 26 lines of video are sent in the clear and, even during the rest of the video frame, (no matter what's going on with the picture), the horizontal sync pulse is never inverted. It might be weak or missing entirely, but it's never upside down. That's important to keep in mind because if we generate our own horizontal sync, we don't want

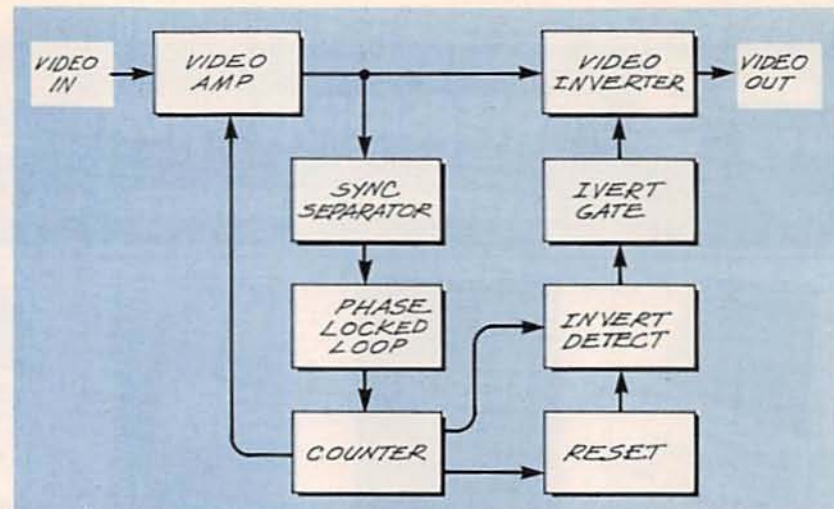

**FIG. 2—THIS CIRCUIT WILL MAKE SURE** the picture is always present at the output in a non-inverted state, and that it has horizontal sync pulses present at the right level and the right position.

an upside down, positive-going sync signal present. If that was the case, the two sync signals would add together and cancel, which is not a good thing.

We've talked about how to regenerate sync when the signal being received is unreliable. If you don't remember it or haven't read it, go back to October's column and review it. Basically, the approach is to take the horizontal pulses sent in the clear during the vertical interval and use them as the reference for a phase-locked loop that will supply the missing pulses during the rest of the video frame. If you've got twenty or so reliable pulses per frame, you can accurately generate the missing two hundred and forty or so for the rest of the frame.

The block diagram of the circuit we need is shown in Fig. 2. In a nutshell, the job of the circuit is to make sure the picture is always present at the output in a non-inverted state, and that it has horizontal sync pulses present at the right level and the right position.

The scrambled video is fed to an op-amp and the output is sent to a sync separator—the same basic circuit that's found in every TV set in the universe. The sync pulses drive a phase-locked loop whose output is decoded to provide the missing sync pulses for the video lines outside the vertical interval (where most of the interesting stuff is found). These generated sync pulses are mixed with the incoming

video and then sent, through a gated inverter, to the back of your TV set.

The gated inverter is controlled by a signal that tells it whether or not the picture portion of the video is upside down. The control signal is derived by watching the state of line 20, as we discussed before.

All this sounds incredibly complicated but, if you look over the block diagram, you'll see that it's just a collection of gates and counters—the same sort of stuff we've been messing around with for years.

The only box in the diagram I haven't explained is the reset circuit for the counter. I'll explain that in the next column but you should be able to figure out for yourself exactly what it is. If you get it right, you've got a good handle on the subject of video in general and scrambling in particular. If you can't figure it out, spend the next month getting ready by boning up on the essentials of basic video theory. **R-E**



# Take any **3** PROFESSIONAL BOOKS only for \$**9<sup>95</sup>**

when you join the **ELECTRONICS ENGINEERS' BOOK CLUB** <sup>SM</sup>

Values to  
\$134.40



**3258**      **\$28.95**  
This book offers up-to-date instructions for troubleshooting and repairing all major brands of equipment, with hundreds of diagrams, specs, and schematics. Covers TVs, VCRs, CD players, and much more. 310 pp.



**3991**      **\$39.95**  
Engineers and technicians will find full coverage of standard power supply sources. Covers new frequency devices including insulated-gate bipolar transistor (IGBT), mos-controlled thyristor (MCT). 464 pp., 365 illus.



**9255-XXX**      **\$105.00**  
"Outstanding, extensive reference to current technology of electronics. Covers everything from principles to applications."  
—Computer Book Review  
2,528 pp., 1,800 illus.  
Counts as 3



**003961**      **\$39.95**  
Here's your guide to basic electrical measurements, component measurements, system tests, and performance verification. Most of the methods and procedures you'll find here use available off-the-shelf test equipment. 224 pp., 180 illus.



**3438**      **\$39.95**  
Promotes true understanding by explaining how and why mathematics principles work. Step-by-step instructions and alternative techniques are provided for solving problems in basic arithmetic, algebra, geometry, trigonometry, and calculus. 512 pp., 481 illus.



**3138-XX**      **\$60.00**  
A GIANT "Circuit Book" of over 700 of the most widely-used, state-of-the-art electronic and integrated circuits ever compiled in a single source! The perfect sourcebook for all levels of electronics practitioners. 738 pp. Counts as 2



**3147-XX**      **\$38.95**  
Provides a ready source of basic information on using programmable controllers to achieve a wide variety of manufacturing goals. You'll find flowcharts and step-by-step explanations to develop, improve, and monitor process control. 304 pp., 187 illus. Counts as 2



**3203-XX**      **\$46.95**  
This reference offers you comprehensive discussion of theory and application of solder pastes with particular emphasis on how they affect the electronics industry. Covers metallurgy, rheology, fine particle measurement, and more. 288 pp., 162 illus., 4 pp. color Counts as 2



**1938-XX**      **\$60.00**  
For quick-reference and on-the-job use, this sourcebook puts over 1,300 state-of-the-art designs at your fingertips. From A (alarm circuits) to Z (zero crossing detector circuits) this compendium excels in content, scope, and design. 768 pp. Counts as 2



**2672**      **\$49.50**  
This "one-stop" sourcebook bridges the gap between data books and the designer's search for the right component. Covers how linear ICs are fabricated, how they work, what types are available, and techniques for designing. 624 pp.



**020975-XXX**      **\$104.50**  
The essential reference for all electrical engineers. Completely revised and updated, this classic handbook covers the generation, transmission, distribution, control, conservation, and application of electrical power. 2,416 pp., 1,388 illus., 430 tables. Counts as 3



**3540**      **\$26.95**  
This guide brings you up-to-date on today's most advanced power supply circuits, components, and measurement procedures. Covers switching rates up to 3-MHz and higher as well as the 20-kHz standard. 176 pp.



**3710**      **\$32.95**  
Understand the basics of receiver operation, the proper use and repair components in RF circuits, and principles of radio signal propagation from low frequencies to microwave. 416 pp., 411 illus.




**025354**      **\$29.95**  
Understand the latest data communications software systems and how they interface with the hardware. This hands-on guide emphasizes the practical side of the field while keeping mathematical theory to a minimum. 192 pp., 30 illus.



**3589**      **\$27.95**  
A practical toolbox reference for anyone in the electronics field. Pagan guides you through the practical calculations needed to design and troubleshoot circuits and components. 352 pp., 270 illus.



 
**053570-XX \$64.95**  
This is a "one-stop" guide to the theory and design of communications receivers: short-wave, broadcast, radar, military, broadcast (AM-FM), radar aeronautical, marine, and directions finding. 608 pp., 402 illus. *Counts as 2*



**022764-XX \$92.50**  
Packed with information for solving on-the-job design, operation, and analysis problems. This is the most complete collection of engineering facts, figures, techniques, and methods ever assembled into a single source. 1,072 pp., 400 illus. *Counts as 2*



 **2962P \$17.95**  
This complete EPROM instruction manual provides a detailed explanation of underlying theory, plus 15 different projects, including programmers, erasers, and EPROM-based circuits. 240 pp. *Softcover*




**049530 \$44.95**  
Keep the lines clean and fault-free with this organized approach to power systems analysis. You'll apply theoretical concepts to the solution of everyday power systems problems with the help of this book. 288 pp., 150 illus.




**050806-XX \$54.95**  
This book emphasizes circuit, transformer, and magnetics design. Provides worked-out examples of transformers, currents, power levels, and more. 550 pp., 250 illus. *Counts as 2*



 **3279 \$36.95**  
Perform routine maintenance and diagnose and repair any kind of computerized device. This popular reference covers large dynamic RAMs, 32-Bit processors, 80286, 80386, and Z8001-Z8002 processors. 570 pp.



 **037504 \$39.95**  
Packed with simplified, circuit-by-circuit troubleshooting examples, this handbook provides the practical know-how you need to operate and troubleshoot modern RF equipment. 352 pp., 150 illus.



**585261-XX \$52.00**  
Get clear, straightforward coverage of all principles underlying the operation and analysis of state-of-the-art circuits—along with a lot of examples, problems, and illustrations. 434 pp., Illustrated *Counts as 2*



**3365P \$24.95**  
Both a professional reference and a study guide for the aspiring technician, this is a well-illustrated introduction to modern communications. Use it to prepare for your FCC General Radiotelephone Operator License or CET exam. 704 pp. *Softcover*



**9290-XX \$36.00**  
This book provides the practical approaches and innovative, easy-to-perform troubleshooting techniques you need to pinpoint symptoms and effectively evaluate the cause of electronic malfunctions. 318 pp., Illus. *Counts as 2*

**Your source for quality, affordable and timely authoritative engineering books.**

**As a member of the Electronics Engineers' Book Club<sup>SM</sup> . . .**

. . . you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off of regular publishers' prices. If you want the Main Selection do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. And you'll be eligible for **FREE** books through the **NEW** Bonus Book Program. Your only obligation is to purchase 3 more books during the next 2 years, after which you may cancel your membership at any time.

©1992 EEBC  
All books are hardcover unless otherwise noted. Publishers' prices shown. If you select a book that counts as 2 choices, write the book number in one box and XX in the next. If you select a Counts as 3 choice, write the book number in one box and XXX in the next 2 boxes. A shipping/handling charge & sales tax will be added to all orders.

If card is missing, write to:  
Electronics Engineers' Book Club, Blue Ridge Summit, PA 17294-0860

**ELECTRONICS ENGINEERS' BOOK CLUB**

Blue Ridge Summit, PA 17294-0860

**YES!** Please rush me the books indicated below for just \$9.95 plus shipping/handling & applicable sales tax. Enroll me as a member of the **Electronics Engineers' Book Club** according to the terms outlined in this ad. If not satisfied, I may return the books within 10 days without obligation and my membership will be cancelled. A shipping/handling charge and sales tax will be added to all orders.

--	--	--

If you select a book that counts as 2 choices, write the book number in one box and XX in the next.  
If you select a Counts as 3 choice, write the book number in one box and XXX in the next 2 boxes.

Name \_\_\_\_\_

Address \_\_\_\_\_

City/State \_\_\_\_\_

Zip \_\_\_\_\_ Phone \_\_\_\_\_

Offer valid for new members only, subject to acceptance by EEBC. Canada *must* remit in U.S. funds. Applicants outside the U.S. and Canada will receive special ordering instructions. **DRE1292C**

## It's a matter of hear today, gone tomorrow

LARRY KLEIN

It's an unhappy paradox that at a time when music reproduction is approaching perfection, there is widespread failure in the music listener's ability to hear it fully. Four years ago I wrote in this column about the audiometric hearing tests given by the Audio Engineering Society at their 1986 Los Angeles convention. The more-than-200 AES members tested showed small but consistent hearing losses that exceeded those expected from the normal aging process. A wide variation of hearing thresholds was measured in the sensitive 3- to 6-kHz range with more than 10% of the respondents showing significant hearing loss at 4 kHz.

It's a sure bet that things have not improved any in the last six or seven years. In fact, from what I hear, the quantity and level of ear-damaging environmental sounds have escalated beyond reason. Under environmental sounds, I include everything from power mowers and blowers to live and reproduced rock music. Can anything be done to tame the wild decibels?

### English ears

For some reason, many of the extensive research studies on hearing loss and music listening have been done in the U.K. Several years ago, two researchers at the University of Keele tested two groups of Staffordshire high-school students; one group had frequent exposure to loud music at rock concerts, discos, and through personal stereo headphones. The control group (I wonder where they found them) had little or no such exposure.

Although conventional diagnostic tests revealed no overall hearing loss, two problems did become evident with more precise techniques. There was evidence of the group's diminished sensitivity to a narrow

band of mid frequencies and, surprisingly, a reduced ability to distinguish between adjacent musical pitches.

Environmentally engendered hearing loss is not limited to kids addicted to rock concerts, loud headphones, and killer car-stereo systems—all of which have been measured at noise levels over 110 dB. The older, if not wiser, generation is also surrounded by equipment that is not intentionally loud but just happens to be. I'm referring to a variety of home, yard, and recreational equipment. These include power tools (my radial-arm saw cutting through hardwood makes quite a racket!), power mowers, and leaf and snow blowers. Recreational vehicles such as outboard motor boats and snowmobiles, are also

potent sources of the kind of sustained sound levels that can be particularly damaging.

In general, the rule seems to be that constant sound levels, particularly in a narrow band, are more harmful than louder intermittent sounds. In other words, if your sound-pressure level (SPL) meter needle seems stuck at the 90-dB level, the sound is likely to be far more damaging than if the needle is swinging wildly with occasional 100-dB peaks.

Since the ear-damaging effects of noise result from cumulative exposure over time, noise-dosage meters have been developed for industrial use. They average out the varying sound-pressure level to provide an equivalent continuous sound level, or  $L_{eq}$ . Such devices are analogous to the radiation-dosage meters that are supposed to keep workers in the nuclear industries safe. Experience has shown that some hearing loss will occur in 20% to 25% of workers exposed to the legally allowed limit of 90 dB ( $L_{eq}$  in dBA) for 8 hours. That is the sound level of heavy street traffic or a subway train.

### Damage report

Exactly how does hearing damage occur? Aside from eardrum rupture caused by a high-pressure pulse from a loud nearby sound, rapid pressure changes and diseases of the auditory nerve and central nervous pathways, the major area of damage occurs in the microscopic hair cells residing in the spiral-shaped cochlea of the inner ear. Dr. John Rosowski of Harvard Medical School has been investigating the problem. At relatively low levels of intensity, he says, damage appears to be proportional to the amount of energy entering the ear during a particular period of time.

### MAXIMUM ALLOWABLE OSHA LEVELS


The Occupational Safety and Health Act (OSHA), which became law in late 1970, places limits on the noise conditions to which employers may subject their workers. The maximum allowable sound levels and daily exposure periods are given in the table. For industries that fall under the jurisdiction of the act, those limits have the force of law, and an employer is obliged to take corrective steps if it is found that any employee is being exposed to noise that exceeds the limit.

TABLE 1—MAXIMUM ALLOWABLE OSHA LEVELS

Exposure duration level (hours per day)	Maximum level ( $L_{eq}$ in dBA)
8	90
4	95
2	100
1	105
1/2	110

But beyond some critical level of sound pressure, the hair cells become much more susceptible to trauma. With only a small increase in SPL beyond this critical point, the damage increases significantly and disproportionately.

The microscopic hair cells are the specific transducers that convert the vibrations in the inner ear to the electrical impulses sent to the brain. Each hair cell, which has a diameter about 1/8 that of a hair, is topped off by 20 or so stereocilia that resemble the bristles on a toothbrush. Scanning electron micrographs of sound-damaged microcilia show them bent, fused, and even missing. That results in a medical diagnosis of "nerve deafness," an irreversible condition.

 

**FIG. 1. LOSS OF HEARING** is a natural result of aging (a), but a much more severe loss can result from long-term exposure to an excessively noisy environment (b). Both curves are at 4 kHz, but high-frequency hearing goes first.

In general, everyone who lives in a civilized (meaning noisy) environment is subject to some hearing loss over time. [See Fig. 1-a.] At first, the loss appears only in the upper frequencies usually reproduced by tweeters. In time, however, the loss progresses downward to the upper midrange frequencies that differentiate the sounds important to speech comprehension.

### Now hear this

There is good evidence that individuals vary in their physical tolerance of loud sounds. Nevertheless, there are some ground rules that those who care about their hearing should follow. Since ear damage is cumulative, resulting in a gradual deterioration, sounds that are instantly heard as too loud—


that cause ringing or other inner ear noises—should be avoided or at least diminished by placing damp cotton wads in the ears or by the use of more effective medically-approved ear-protection devices. However, loud, but not obviously excessive, sound sources, musical or otherwise, can also be damaging in the long run.

I have an audiophile friend who wears earplugs in the subway and in

other noisy environments. Aside from the noise level in public places, you should consider ear protection when performing such activities as power-tool carpentry and lawn care. Even wads of cotton stuffed tightly in your ear canals will help. It's not just that you are saving yourself an immediate headache, but you might avoid a hearing-aid purchase 30 or 40 years from now. Don't be dumb today—and deaf tomorrow. **R-E**

## Economic Choice for High Quality from GOLDSTAR

### OSCILLOSCOPE

 

### DIGITAL MULTIMETER



### FREQUENCY COUNTER FUNCTION GENERATOR



- DM-9055S**
  - 3 1/2 Digits
  - Pen Type DMM
  - Auto and Manual Range
  - Logic tester
  - Current
- DM-9183**
  - 3 1/2 Digits
  - Manual Range
  - Diode Check
  - Continuity
  - Large LCD Display
- DM-6335**
  - 3 1/2 Digits
  - Auto Range
  - Memory
  - Data Hold
  - Diode Check
  - Continuity
- DM-8135**
  - 3 1/2 Digits
  - Auto Range
  - Bar Graph
  - hFE Check
- DM-7333**
  - 3 1/2 Digits
  - Manual Range
  - hFE Check
  - Capacitance Check
  - Freq. Counter
- DM-8433**
  - 3 1/2 Digits
  - Manual Range
  - hFE Check
  - Temperature Check
  - Capacitance Check
- DM-7143**
  - 4 1/2 Digits
  - Manual Range
  - Data Hold Function
- DM-8243**
  - 4 1/2 Digits
  - Manual Range
  - Data Hold Function
  - hFE Check
  - Capacitance Check
  - Freq. Counter
- DM-7241**
  - 4 1/2 Digits
  - Bench Type
  - Manual Range
  - Measuring Unit Display with LCD
  - Function Indication
- FC-7012: 100MHz**
- FC-7052: 550MHz**
- FC-7102: 1GHz**
- FG-8002**
  - 0.02 Hz To 2MHz
  - Sweep
- GP-103: 18V/1.0A**
- GP-105: 30V/0.5A**
- GP-235: 18V/1.0A**
- 30V/0.5A**

**GoldStar Precision Co., Ltd**

13013 East 166th Street, Cerritos, Ca, 90701 U.S.A.  
TEL: (310) 404-0101 FAX: (310) 921-6227

CIRCLE 198 ON FREE INFORMATION CARD

# ATTENTION! ELECTRONICS TECHNICIANS

EARN YOUR  
**B.S.E.E.  
DEGREE**



THROUGH HOME STUDY

Our New and Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete Program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through this Special Program you can pull all of the loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the Engineering Level. Advance Rapidly! Many finish in 12 months or less. Students and graduates in all 50 States and throughout the World. Established Over 40 Years! Write for free Descriptive Literature.

**COOK'S INSTITUTE**  
OF ELECTRONICS ENGINEERING



4251 CYPRESS DRIVE  
JACKSON, MISSISSIPPI 39212

CIRCLE 58 ON FREE INFORMATION CARD



## Your Ticket To SUCCESS

Over 28,000 technicians have gained admittance worldwide as certified professionals. Let your ticket start opening doors for you.

ISCET offers Journeyman certification in Consumer Electronics, Industrial, Medical, Communications, Radar, Computer and Video. For more information, contact the International Society of Certified Electronics Technicians, 2708 West Berry Street, Fort Worth, TX 76109; (817) 921-9101.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Send material about ISCET and becoming certified.

Send one "Study Guide for the Associate Level CET Test." Enclosed is \$10 (inc. postage).

## EQUIPMENT REPORTS

continued from page 16

(5000 counts) signals with crest factors up to 3.0 can be measured. At full scale, a signal must have a crest factor less than 1.5 to be measured accurately.

The HD160 offers impressive overload and safety protection. The voltage inputs can withstand up to 1000 volts AC or DC. Both current jacks are protected by fuses. An added safety feature protects the meter, user, and the device under test: When a probe is inserted in one of the current jacks and the function switch is set to a non-current mode, the meter's display will show an error message to warn the user.

The HD160 is priced at \$199. The capable, rugged high-quality meter will be appreciated by anyone who needs a DMM for serious professional use.

R-E

## COMING NEXT MONTH

The January 1993 Issue  
goes on sale  
December 3, 1992

### WORLD BAND SHORTWAVE RECEIVER

Keep informed on world events and learn RF construction techniques!

### BUILD THE RING THING

Now you can have remote access to your PC even if the power is off!

### BUILD A VOICE CHANGER

A project that's as fun to use as it is to build!

### RESISTORS

A comprehensive guide.

AND LOTS MORE!

To prevent crime  
in Tucson,  
police use sensitive,  
highly sophisticated  
surveillance equipment:

**Tim, Rose, Gert,  
Anthony, Yvonne,  
and Ramon.**

Citizen participation is critical to police effectiveness. Do you care about your neighborhood enough to help protect it?

### The Case of the Tucson Tip-off.

In a particular neighborhood in Tucson, Arizona, folks were having a real problem with burglaries and break-ins.

They started talking to each other about what they could do. They got fed up. About 400 people went to the police for advice. They learned about surveillance. They got to know their beat officers. Citizens and police became partners in crime prevention.

In just three weeks, 17 arrests were made and burglaries went down 30%. And Tucson is only one case where people successfully worked to beat crime. To find out more, write: **The McGruff Files, 1 Prevention Way, Washington, D.C. 20539-0001.**

You can make a difference.  
You can help...



TAKE A BITE OUT OF  
**CRIME**



A message from the Crime Prevention Coalition, the U.S. Department of Justice and the Advertising Council. © 1989 National Crime Prevention Council.

# COMPUTER CONNECTIONS

## Computers and Consumer Electronics

JEFF HOLTZMAN

**C**omputers and consumer electronics are merging. Kodak and Tandy have added fuel to the fire with their recent introductions of Photo-CD and the Visual Information System (VIS), respectively. Photo-CD and VIS join CD-ROM Interactive (CD-I) and Commodore Dynamic Total Vision (CDTV) as the major attempts to put computer-like interactivity on a television screen, thereby capturing the hearts and minds—and pocket-books—of noncomputerized consumers. VIS, CDTV, and CD-I are direct competitors; although similar in some ways, Photo-CD is really in a category by itself. (You might also want to keep in mind upcoming CD-based systems from Nintendo and Sega.) Photo-CD, CD-I, CDTV, and VIS all share the following in common:

- They are meant to be operated in

the family room, not in a home office or corner of the bedroom.

- They use the home entertainment system (TV and stereo) for audio and video output.
- They emphasize early education, games, entertainment, and reference works.
- They use some form of CD-ROM as the primary delivery medium.
- They operate with simple infrared remote-control devices rather than computer keyboards.
- They are meant to appeal to less technically sophisticated consumers than computer users.
- They cost in the \$600–1000 range.

To understand what each of these technologies has to offer and which is likely to be successful, let's summarize the key points of each.

**CDTV** This system descends from a long-time player in the per-

sonal-computer market. Starting way back with the Pet (in the late 1970's), and moving on through the C-64, and then to the Amiga, Commodore has always had a presence in personal computing. However, the company has never developed and executed a clear marketing strategy, hence has been a sideline player in most areas. The single exception is video production on the Amiga, where word of mouth and an unbeatable price/performance ratio have brought success. CDTV was introduced in the early summer of 1991, and has yet to achieve major acceptance. CDTV consists of a stripped-down Amiga 500 computer that has been specially modified to respond to commands from an infrared remote. The unit can be expanded to be a functional Amiga 500 by adding keyboard, disk drive, memory, and mouse. CDTV is sold by Commodore dealers.

**CD-I** Philips Consumer Electronics introduced the CD-I system in the fall of 1991 after several delays. It consists of a proprietary 68000-based system running a special version of the OS-9 operating systems. CD-I players are sold by consumer-electronics outlets. Approximately 65 CD-I titles are available, including several "celebrity" titles narrated by Danny Glover, Mia Farrow, Robin Williams, Jack Nicholson, Raul Julia, and Sir John Gielgud. One CD-I disc explores jazz giants such as Charlie Parker, Miles Davis, and Sarah Vaughn. Another disc explores the paintings of Rembrandt, and includes narration in seven languages (Dutch, English, French, German, Italian, Japanese, and Spanish). Titles start at \$15; most are priced in the \$20 to 40 range.

**VIS** Like Commodore, Tandy has been involved with personal com-



**FIG. 1—KODAK'S PHOTO-CD** puts 100 images in five different resolutions on a single CD-ROM disc. The player displays images on your TV screen and plays regular audio CD's through your stereo. A future upgrade will allow you to add audio and text to a Photo-CD disc, thereby allowing annotated, navigable slide shows.

puters since the earliest days. Its chief products include the TRS-80 series, the Color Computer, the Model 100/200 portables, a line of semicompatible PC's, and a line of fully compatible PC's. While never achieving great success in the business community, the PC compatibles have, nonetheless, held their own in the hobbyist/consumer market. VIS, is in fact, the "Wintendo" device discussed here in the October issue that has fueled the industry rumor mill for months. Unlike the other products discussed here, VIS software architecture is based on MS-DOS and Modular Windows, a ROM version of Microsoft's Windows optimized for use in a consumer (television) environment. Virtually all leading content developers, including Berlitz/Cruise Watch, Broderbund, Compton's New Media, Electronic Arts, Lucas Arts, Sierra, and others, are developing VIS titles; AimTech (IconAuthor) and OWL (Guide) have authoring systems, and Microsoft might have something up its sleeve in that area as well.

The DOS/Windows platform is good for several reasons. Content developers don't have to buy specialized and costly development platforms; standard PC's (with emulation boards) will do the trick. Porting VIS titles to and from other systems (e.g., MPC-compatible PC's) will be simpler than porting to or from a whole new architecture. Tandy's immense retail network ensures broad product availability and servicing. Zenith will also be selling VIS systems under its own brand name.

**Photo-CD** Kodak's technology is not currently designed to compete in the interactive-TV market, although it does have architectural features that might eventually provide interactivity. Photo-CD is designed to appeal to both professional and broad consumer bases. In the consumer world, Kodak hopes Photo-CD will supplement the family photo album and slide projector. In a professional setting, it will be useful for desktop publishing, corporate image databases, stock photo image bases, medical imaging, image archiving, and probably lots more. Photo-CD works like this: You take

or mail a standard roll of print or slide film (up to 4 x 5 inches now, with larger formats coming) to a special Photo-CD processor, which then scans each image at five resolutions ranging from catalog-quality "thumbnails" (128 x 196) to publication-quality scans (6000 x 4000).

Depending on image size and content, it is possible to store about 100 images per disk in the standard consumer Photo-CD format. Other professional formats are available

### Resources

- **The Visual Display of Quantitative Information (\$40), Envisioning Information (\$48), Graphics Press, Box 430, Cheshire, CT 06410, (203) 250-7007.**  
CIRCLE 41 ON FREE INFORMATION CARD
- **Photo CD, Eastman Kodak Company, 343 State Street, Rochester, NY, 14650-0519, 800-242-2424.**  
CIRCLE 42 ON FREE INFORMATION CARD
- **Pro 16 Multimedia System, MediaVision, 3185 Laurelview Court, Fremont, CA 94538, 800-348-7116, 510-770-8600.**  
CIRCLE 43 ON FREE INFORMATION CARD
- **Visual Information System, Tandy Corporation, 1800 One Tandy Center, Forth Worth, TX 76102.**  
CIRCLE 44 ON FREE INFORMATION CARD
- **Compact Disc Interactive, Philips Consumer Electronics Company, One Philips Drive, P.O. Box 14810, Knoxville, TN, 615-475-0317.**  
CIRCLE 45 ON FREE INFORMATION CARD
- **Commodore Dynamic Total Vision, Commodore Business Machines, Inc., 1200 Wilson Drive, West Chester, PA 19380, 215-431-9100.**  
CIRCLE 46 ON FREE INFORMATION CARD

that allow storage of as many as 6000 low-resolution images (e.g., for image catalogs).

For family-room use, Photo-CD's can "play back" on special players (like that shown in Fig. 1) that also handle audio CD's, and on select computer-based CD-ROM drives (in particular, those claiming CD-ROM/XA compatibility). For computer-based use, Kodak has introduced low-cost PC- and Macintosh-based software packages for viewing images and getting them into standard bitmap formats such as

PICT, TIFF, and EPS. Some commercial graphics editors (e.g., Publishers Paintbrush) already offer built-in Photo-CD support. Apple has announced that it will support the Photo-CD format directly in System 7 software, and via QuickTime (Apple's set of technologies and specifications for time-dependent data, (e.g., audio and video sequences)). Kodak has also announced several advanced image-editing packages.

Photo-CD uses a multiple-write technology that allows several sessions to be placed on a single disc at several times. If you're interested in using multi-write capabilities on a computer, make sure your CD-ROM drive can handle it. Check Kodak's hotline at the number shown in the sidebar for information on compatible CD-ROM drives, processing centers, and software availability.

### You want a revolution?

Will CDTV, CD-I, VIS, or Photo-CD bring about some revolution in the computer industry, the consumer electronics industry, or both? Are they destined for the junk heap, along with the early personal computers and dedicated video games of the 70's and 80's?

They're probably all headed for the junk heap sooner or later, but VIS and Photo CD have the best chance of survival during the next few years. Commodore's on-again/off-again marketing style inspires confidence in neither developers nor consumers. Philips' system has some technical advantages, for example hardware-assisted full-motion video based on the industry-standard Motion Picture Expert Group (MPEG) compression format. But even that is an add-on to the basic player. Development systems are proprietary, and there is a lack of broad industry support.

Photo-CD, on the other hand, offers immediate advantages to the computing community, especially desktop publishing and professional imaging concerns.

Broad appeal is problematic in that Photo-CD will be competing for consumer dollars against VIS and the other systems, all of which offer more general-purpose functionality.



It seems unlikely that people would want to buy more than one CD-based digital information appliance to connect to their TV's and stereos. Viewed in that light, Photo-CD might find it difficult to crack the home market. If VIS (or the other systems) could provide Photo-CD compatibility, then Kodak might lose the player battle but win the format/usage war. There is a lot of money to be made in processing Photo-CD's and in selling processing its workstations.

Photo-CD stands a very good chance of survival, simply because the publishing and imaging industries need it. The consumer market might go for it, depending on consumer awareness of the more general-purpose nature of VIS. I think Kodak would be smart to work with Tandy to ensure that VIS can play Photo-CD discs.

On paper, VIS looks like the safest bet among the interactive systems, both for developers and consumers. Like CDTV, VIS is really a general-purpose computer, albeit not in the present incarnation an expandable one. Because VIS is so closely related to the DOS/Windows platform, content developers can create and port titles at low cost and low risk. Assuming Tandy stays with the architecture, upgrading to higher-performance technology (e.g., full-motion video) should be fairly painless. Also, if anywhere near the number of promised titles actually materialize by the time VIS hits the market (presently aimed for Christmas 1992), Tandy will have a huge advantage.

VIS is extremely interesting. If it succeeds, it will mark the first success of a manufacturer in more than a decade in trying to penetrate the consumer market with a general-purpose digital information system. Computerphiles will probably view VIS as underpowered. But with the Windows platform underpinning the system, there's lots of potential for growth.

I'm looking forward to hooking a VIS system up to my home-entertainment center. However, I know up-front that it's a throw-away purchase; the computer industry is still evolving so rapidly that VIS will be superseded by something. My



FIG.2—TANDY'S VIS or Video Information System runs a Windows-like operating system designed by Microsoft.

hope is that, between now and obsolescence, my kids will get more from it than from a video game.

### Product watch

I've looked at several multimedia upgrade kits over the past year, and have reached several conclusions. First, the base MPC specification is pretty low-fi. Nonetheless, results can still be startling. The best MPC upgrade kit I've found is from Medi-aVision. It includes what is currently one of the best CD-ROM drives on the market, NEC's SCSI-based CDR-83, along with the ProAudio Spectrum 16-bit stereo audio card, which has a built-in SCSI interface. The bundle also includes a slew of software, including Lotus 1-2-3, Compton's Multimedia Encyclopedia, a CD-based version of Sierra's King's Quest V, an authoring tool called Action from Macromind, and numerous DOS and Windows utilities for recording, mixing, and playing back sound and MIDI files. The utility software varies widely in quality, user interface, and usefulness, and it does not include a Windows-based MIDI editor, the major shortcoming of the package. The methods for configuring system interrupts and I/O port use is poorly documented, but once running, the package works like a charm.

### Bookshelf

You probably take that voltage-versus-time display on the front of your oscilloscope for granted. What you might not know is that graphical displays of data were not even invented until the latter half of the nineteenth century, long after the invention of calculus. An En-

glishman, William Playfair, and a Swiss-German, J. H. Lambert, claim the honor of first publishing the many basic techniques of statistical graphics. You might also be unaware of what makes bar charts, time series, and other kinds of graphs really work. Why is that important? Because most technical professionals use spreadsheet, data-analysis, and visualization programs to analyze and display data, be it voltage, current, resistance, impedance, dollars, or other quantities. Computer tools give you lots of options for displaying your data using color, gray scales, hatching, perspective, and more. However, unless you're careful, you can get into trouble, graphically speaking, and thereby obscure your real message.

If you ever produce a chart or graph as part of your job, you absolutely must look at two books by Yale statistics professor Edward R. Tufte: *The Visual Display of Quantitative Information* (originally published in 1983), and *Envisioning Information* (1990). Alternate titles for those two exquisite works could be Volumes I and II of *Use and (Especially) Abuse of Statistical Data in Graphical Form*. In example after example, Tufte shows and tells why some things work and others don't, along the way exposing numerous misguided attempts at "improving" the presentation of statistical data. Tufte understands that effective communication of information involves carefully meshing form and content. He practices what he preaches. Beg, buy, or borrow copies of these works. You won't be disappointed.

# BUYER'S MART

## FOR SALE

**TUBES.** "oldest," "latest." Parts and schematics. SASE for lists. **STEINMETZ**, 7519 Maplewood Ave., Hammond, IN 46324 RE.

**RESTRICTED** technical information: Electronic surveillance, schematics, locksmithing, covert sciences, hacking, etc. **Huge selection. Free brochures.** **MENTOR-Z**, Drawer 1549, Asbury Park, NJ 07712.

**TUBES**, new, up to 90% off, SASE, **KIRBY**, 298 West Carmel Drive, Carmel, IN 46032.

**T.V. notch filters**, phone recording equipment, brochure \$1.00. **MICRO THinc**, Box 63/6025, Margate, FL 33063. (305) 752-9202.

## WIRELESS CABLE RECEIVERS 1.9 TO 2.7 GHz



30 CH PARABOLIC DISH SYSTEM \$173.90  
30 CH ROD ANTENNA SYSTEM \$193.90  
30 CH CRYSTAL CONTROLLED SYSTEM \$294.95  
SUN MICROWAVE INT'L. INC. SEND \$1.00 FOR  
P.O. BOX #34522 CATALOG ON THESE  
PHOENIX, AZ 85087 AND OTHER FINE  
(602) 230-1245 VIDEO PRODUCTS  
QUANTITY DISCOUNTS  
ORDERS ONLY 1-800-484-4190 CODE 9793

VISA/MC/AMEX

**ENGINEERING** software and hardware, PC/MSDOS. Circuit design and drawing, PCB layout, FFT analysis, mathematics, circuit analysis, etc. Data acquisition, generation, I/O PCB's, etc. Call or write for free catalog. (614) 491-0832, **B'SOFT SOFTWARE, INC.**, 444 Colton Rd., Columbus, OH 43207.

**CABLE TV Equipment.** Most type available. Special: Oak M35B \$39.95. No catalog. COD orders only. 1 (800) 822-9955.

**JERROLD, Tocom and Zenith "test" chips.** Fully activates unit. \$50.00. Cable descramblers from \$40.00. Orders 1 (800) 452-7090. Information (213) 867-0081.

**TOCOM-Jerrold Impulse-Scientific Atlanta** Converters, two year warranties, also test modules for your converters. Contact **NATIONAL CABLE**, (219) 935-4128 full details.

## FREE CATALOG

**FAMOUS "FIRESTIK" BRAND CB ANTENNAS AND ACCESSORIES. QUALITY PRODUCTS FOR THE SERIOUS CB'er. SINCE 1962**  
**FIRESTIK ANTENNA COMPANY**  
2614 EAST ADAMS  
PHOENIX, ARIZONA 85034

**SECRET cable descramblers!** Build your own descrambler for less than \$12.00 in seven easy steps. Complete instructions \$10.00. Radio Shack parts list and free descrambling methods that cost nothing to try included. **HARRYWHITE**, PO Box 1790, Baytown, TX 77520.

**PROTECT** yourself and equipment from electrical shocks. Complete unit \$98.95. **SAFETY-UNLIMITED**, 1743 Baldwin Road, Yorktown, NY 10598. S/H \$5.00.

**TEST** equipment pre-owned now at affordable prices. Signal generators from \$50.00, oscilloscopes from \$50.00. Other equipment including manuals available. Send \$2.00 U.S. for catalog refunded on first order. **J.B. ELECTRONICS**, 3446 Dempster, Skokie, IL 60076. (708) 982-1973.

**CABLE TV converters:** Jerrold, Oak, Scientific Atlantic, Zenith & many others. "New MTS" stereo add-on: mute & volume. Ideal for 400 and 450 owners! 1 (800) 826-7623, Amex, Visa, M/C accepted. **B & B INC.**, 4030 Beau-D-Rue Drive, Eagan, MN 55122.

**CABLE TV converters.** Jerrold, Zenith, Pioneer, Oak, Scientific Atlanta, and many more. 12 years experience gives us the **advantage.** Visa/MC Amex COD **ADVANTAGE ELECTRONICS, INC.**, 1 (800) 952-3916 1125 Riverwood Dr., Burnsville, MN 55337.

## CLASSIFIED AD ORDER FORM

To run your own classified ad, put one word on each of the lines below and send this form along with your check to:

**Electronics Now Classified Ads**, 500-B Bi-County Boulevard, Farmingdale, NY 11735

**PLEASE INDICATE** in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of **\$25.00**.

( ) Plans/Kits ( ) Business Opportunities ( ) For Sale  
( ) Education/Instruction ( ) Wanted ( ) Satellite Television

Special Category: \$25.00

### PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.

(No refunds or credits for typesetting errors can be made unless you clearly print or type your copy.) Rates indicated are for standard style classified ads only. See below for additional charges for special ads. **Minimum: 15 words.**

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15 (\$46.50)
16 (\$49.60)	17 (\$52.70)	18 (\$55.80)	19 (\$58.90)	20 (\$62.00)
21 (\$65.10)	22 (\$68.20)	23 (\$71.30)	24 (\$74.40)	25 (\$77.50)
26 (\$80.60)	27 (\$83.70)	28 (\$86.80)	29 (\$89.90)	30 (\$93.00)
31 (\$96.10)	32 (\$99.20)	33 (\$102.30)	34 (\$105.40)	35 (\$108.50)

We accept MasterCard and Visa for payment of orders. If you wish to use your credit card to pay for your ad fill in the following additional information (Sorry, no telephone orders can be accepted):

Card Number

Expiration Date

Please Print Name

Signature

**IF YOU USE A BOX NUMBER YOU MUST INCLUDE YOUR PERMANENT ADDRESS AND PHONE NUMBER FOR OUR FILES. ADS SUBMITTED WITHOUT THIS INFORMATION WILL NOT BE ACCEPTED.**


**CLASSIFIED COMMERCIAL RATE:** (for firms or individuals offering commercial products or services) \$3.10 per word prepaid (no charge for zip code). **MINIMUM 15 WORDS.** 5% discount for same ad in 6 issues; 10% discount for same ad in 12 issues within one year; if prepaid (not applicable on credit card orders). **NON-COMMERCIAL RATE:** (for individuals who want to buy or sell a personal item) \$2.50 per word, prepaid...no minimum. **ONLY FIRST WORD AND NAME** set in bold caps at no extra charge. Additional bold face (not available as all caps) **55¢ per word additional.** Entire ad in boldface, \$3.70 per word. **TINT SCREEN BEHIND ENTIRE AD: \$3.85 per word. TINT SCREEN BEHIND ENTIRE AD PLUS ALL BOLD FACE AD: \$4.50 per word. EXPANDED TYPE AD: \$4.70 per word prepaid.** Entire ad in boldface, \$5.60 per word. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD: \$5.90 per word. TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD PLUS ALL BOLD FACE AD: \$6.80 per word. DISPLAY ADS: 1" x 2 1/2"—\$410.00; 2" x 2 1/2"—\$820.00; 3" x 2 1/4"—\$1230.00. General Information:** Frequency rates and prepayment discounts are available. **ALL COPY SUBJECT TO PUBLISHERS APPROVAL. ADVERTISEMENTS USING P.O. BOX ADDRESS WILL NOT BE ACCEPTED UNTIL ADVERTISER SUPPLIES PUBLISHER WITH PERMANENT ADDRESS AND PHONE NUMBER.** Copy to be in our hands on the 1st of the third month preceding the date of the issue. (i.e., Aug. issue copy must be received by May 1st). When normal closing date falls on Saturday, Sunday or Holiday, issue closes on preceding working day. Send for the classified brochure. Circle Number 49 on the Free Information Card.


 
## You Need Tree City USA


City trees add the soft touch of nature to our busy lives. They cool our cities, fight pollution, conserve energy, give wildlife a home, and make our neighborhoods more liveable.

Support Tree City USA where you live. For your free booklet, write: Tree City USA, The National Arbor Day Foundation, Nebraska City, NE 68410.


 
# CABLE DESCRAMBLERS

Converters, Remote Controls, Descramblers, more



#EX192

All major brands carried

\*JERROLD, \*TOCOM, \*ZENITH  
\*GENERAL INSTRUMENTS  
\*SCIENTIFIC ATLANTA, \*OAK  
\*HAMLIN, \*EAGLE, \*PIONEER

7th Year in business. Thank You  
Member of Omaha Chamber of Commerce  
1 Year warranty on new equipment  
30 Day money back guarantee  
Orders shipped from stock within 24 hours

CALL TODAY FOR A FREE CATALOG  
**1-800-624-1150**



C.O.D.



**M.D. ELECTRONICS**  
875 SO. 72nd St.  
Omaha, NE 68114

CIRCLE 53 ON FREE INFORMATION CARD

### Triplet DMM

Large, easy to read 3-1/2 digit LCD display. Tests voltage in 5 ranges to 750VAC, resistance in 6 ranges to 20M, plus diode test with audible continuity, 6 current ranges to 10A. Built-in battery test and HFE test for NPN and PNP transistors. Test leads, instructions and carrying case included.

#RN-390-140



**\$4700**  
Each

### 6-1/2" Two-Way System

Perfect surround speakers. Customize your media room with these super quality, in-wall speaker pairs. Full size 6-1/2" woofer. Heavy duty 1" soft dome tweeter. Built-in crossover. Fits any standard 2 x 4 or larger wall. Retrofit design allows easy installation in new or existing walls. Response: 40-20,000 Hz. 8 ohm impedance. 40 watts RMS, 60 watts maximum. Includes provision for easy 70V/25V transformer mounting. Overall dimensions: 8-1/2" x 12". Net weight: 9 lbs.

#RN-300-036

**\$249<sup>95</sup>**  
Sug List

**\$99<sup>95</sup>**  
(1-3 prs)

**\$95<sup>50</sup>**  
(4 prs-up)



### Ultimate 5", 2 Way System

A perfect way to upgrade your car's sound system. 5", 2 way bridgeless speaker pair featuring paper cones that are impregnated with a special ingredient to prevent water damage. 1" aluminum voice coil, 6 oz. magnet. Impedance 4 ohm. Frequency response: 20-21,000 Hz. Power handling: 30 watts RMS, 55 watts maximum. SPL: 92 dB 1W/1M. Mounting depth: 1-3/4". Net weight: 4 lbs.

#RN-265-282

**\$46<sup>95</sup>**  
(1-3 prs)

**\$43<sup>50</sup>**  
(4 prs-up)



### 12" Pioneer Woofer

Ribbed paper cone with Pioneer special poly foam surround. Impedance: 8 ohm. Frequency response: 30-2,500 Hz. Sensitivity: 92 dB 1W/1M. Power handling capability: 60 watts RMS, 90 watts maximum. Magnet: 20 oz. Voice coil diameter: 1-1/2". Resonant frequency: 30 Hz. VAS= 11.78 cu ft., QMS= 2.217, QES= .425, QTS= .357. Hole: 10-7/8". Net weight: 5 lbs. Pioneer #A30FU20-52F.

#RN-290-105

**\$29<sup>95</sup>**  
(1-3)

**\$27<sup>50</sup>**  
(4-up)



### Black Widow Challenger Remote Security System

Dollar for dollar, and feature for feature the Challenger security system out performs most competitors in its class. Features include: Two-2 button remote transmitters, compact design for under dash or under seat installation, passive or active arming, visual/audible indication when arming/disarming, remote panic, 360 degree shock sensor, door lock output, starter disable with relay and harness. 120 dB siren, entry/tamper violation memory, built-in parking light flasher or horn sounding circuit, current and switch sensing, manual override switch. 1 positive and 2 negative triggers, flashing LED, RF safety lock-out, automatic reset, glass break sensor and more. Net weight: 3 lbs.

#RN-330-037

**\$99<sup>95</sup>**  
Each



### Mini Electrolytic Cap Kit

This 60 piece kit contains a selection of 16 volt and 50 volt mini electrolytic capacitors. 5 pieces each of 10, 47, 100, 220, and 470 uF, 16 volt radial caps. 5 pieces each of 2.2, 4.7, 10, 22, 33, 4.7 and 100 uF, 50 volt radial caps. This convenient kit has many of the "low profile" caps used in camcorders, VCRs, portables and other products where space is limited. A \$27.00 value.

#RN-024-900

**\$19<sup>95</sup>**  
Each

### The Ultimate Test CD

The Ultimate test CD was designed for use by both the audio amateur and the professional sound engineer. This CD can be used to test CD players, speakers, amplifiers, and for tuning instruments. The manual is written in easy to understand english and takes you step-by-step through each track of the CD and explains its purpose. The Ultimate test CD is a necessary tool for anyone who is serious about quality audio sound.

#RN-510-100

**\$7<sup>95</sup>**  
Each



FREE  
CATALOG



340 E. First St., Dayton, Ohio 45402  
Local: 513-222-0173  
FAX: 513-222-4644

• 30 day money back guarantee • \$20.00 minimum order • We accept Mastercard, Visa, Discover, and most C.O.D. orders. • 24 hour shipping • Shipping charge = UPS chart rate + \$1.00 (\$3.50 minimum charge) • Hours: 8:30 am - 7:00 pm EST, Monday - Friday, 9:00 am - 5:00 pm Saturday. Mail order customers, please call for shipping estimate on orders exceeding 5 lbs. Foreign destination customers please send \$5.00 U.S. funds for catalog postage.

CALL TOLL FREE  
**1-800-338-0531**

CIRCLE 56 ON FREE INFORMATION CARD



## REMOTE CONTROL KEYCHAIN



Complete w/mini-transmitter and +5 vdc RF receiver Fully assembled including plans to build your own auto alarm

**\$24.95** Check, Visa or M/C Add \$3 shipping  
5 @ \$19.95, 10 @ \$14.95

Visitect Inc. Box 14156, Fremont, Ca. 94539  
(510) 651-1425 Fax (510) 651-8454

**HOBBY/broadcasting/HAM/CB/surveillance** transmitters, amplifiers, cable TV, science, bugs, other great projects! Catalog \$1.00. **PANAXIS**, Box 130-F12, Paradise, CA 95967.

**DESCRAMBLER** kits. Complete cable kit \$44.95. Complete satellite kit \$49.95. Add \$5.00 shipping. Free brochure. No New York sales. **SUMMIT RE**, Box 489, Bronx, NY 10465.

**SURVEILLANCE** transmitter kits tune from 65 to 305 MHz. Mains powered duplex, telephone, room, combination telephone/room. Catalog with **Popular Communications, Popular Electronics** and **Radio-Electronics** book reviews of "Electronic Eavesdropping Equipment Design," \$2.00. **SHEFFIELD ELECTRONICS**, PO Box 377785-C, Chicago, IL 60637-7785.



**GREAT Project. Silent Sam** reminds you when you forget. SSTS (Turn Signal Reminder) beeps 3 seconds after 15 seconds. Cycle repeats until cancelled. Unobtrusive, recycles when braking. Compact kit mounts atop flasher. Parts, case, PCB, schematic, instructions \$15 PPD; 2/\$25; 3/\$30. Visa/MC. Free brochure 1-800-398-5605. Prewired \$20 PPD; 2/\$35; 3/\$45 **Silent Sam**, 1627 Basil Dr., Columbus, OH 43227.

**DESCRAMBLING**, new secret manual. Build your own descramblers for **cable and subscription TV**. Instructions, schematics for SSAVI, gated sync, Sinewave, (HBO, Cinemax, Showtime, UHF, Adult) \$12.95, \$2.00 postage. **CABLETRONICS**, Box 30502R, Bethesda, MD 20824.

**BUILD** 0-50 volt regulated dual tracking power supply. Complete schematics and instructions, \$5.95. **SMS ENGINEERING**, RE 5932 West Bell Road, Suite D106, Glendale, AZ 85308.

**PROTOTYPING** PC boards? Fast and easy from artwork to etched board in 30 minutes or less. Complete step by step plans and samples! \$6.50 check or money order to **E.G.G.**, PO Box 11390, Bradenton, FL 34282.

**BOOST** stereo transmitter kit output power! Super simple plans. \$4.00. **X-TEK**, PO Box 521164, SLC, Utah 84152-1164.

**60 SOLDERLESS Breadboard Projects** in two easy-to-read pocket books. Complete with circuit descriptions, schematics, parts layouts, component listings, etc. Both books (BP107 & BP113) only \$11.90 plus \$3.50 for shipping. USA and Canada only. US funds. **ETT, INC.**, PO Box 240, Masapequa Park, NY 11762-0240.

**WIRELESS** guitar transmission system. Build your own for \$39.95! (kit) **RADIOACTIVE TRANSMISSIONS** (519) 250-0559/FAX: 250-0560

**TEST-Aids** for testing units in full service mode. Starcom VII, \$40.00; Starcom VI, \$30.00; Starcom DPBB, \$50.00; Pioneer clears error codes E2-E5, \$60.00; Pioneer cubes, will not alter internal serial #, \$125.00; Tocom VIP 5503/5507, \$25.00; Tocom mapping, \$40.00; S.A. 8500, \$25.00; 8550 \$30.00; 8580, \$40.00; 8570/90, \$50.00; Zenith, \$25.00; security bits and remotes. **N.E. ENGINEERING**, (617) 770-3830.

Hi fidelity FM stereo transmitter \$49.95. Surround sound decoder amp \$29.95. 5 watt audio amp \$14.95. Kits are complete with PCB and pre-tested parts. **KEYVID**, 508 Plover Place, Palm Harbor, FL 34683. (813) 787-0311.



One tree can make 3,000,000 matches.



One match can burn 3,000,000 trees.



New solid-state and digital TV sets, stereos, and videorecorders are tougher to repair than old-fashioned tube type sets and require special training for the service technician who works on them.

Only a few states have laws requiring competency tests for licensing technicians who repair consumer electronics, but fifteen years ago the International Society of Certified Electronic Technicians (CET) began its own certification program to qualify these technicians and those in industry. To carry the CET designation, technicians must have four years experience and pass a rigid examination on general electronics and a specific area of expertise such as audio or radio-TV.

Many consumers look for a Certified Electronic Technician in the shop when they need any electronic item repaired.

**Free Consumer Checklist**  
A consumer checklist for selecting a service shop is available



Modern electronic equipment such as digital TVs or stereos should be repaired by specially trained people.

available free by sending a stamped, self-addressed envelope to: Checklist, ISCET, 2708 West Berry, Fort Worth, TX 76109. The list reminds consumers to check such items as "Does the business have the parts for your particular brand?", "Did you get an estimated price?", and "Did you check this company with the Better Business Bureau?"

# CABLETRONICS

## CONVERTERS

1-4Units 5 Units 10 Units

PANASONIC TZP 145	\$88.00	\$75.00	\$70.00
STARGATE 2000	\$79.00	\$69.00	\$65.00
*HAMLIN MCC 3000	\$25.00	\$19.00	\$15.00

## ADD-ON DESCRABLERS

SB-3 (NEW)	\$50.00	\$45.00	\$43.00
*SB-3 FACTORY	\$45.00	\$39.00	\$35.00
SA-3	\$56.00	\$50.00	\$45.00
DTB-3	\$65.00	\$55.00	\$50.00
KN12A-2 or 3	\$49.00	\$45.00	\$40.00
*HAMLIN MLD 1200-3	\$49.00	\$40.00	\$35.00
*ZENITH SSAVI	\$165.00	\$149.00	\$125.00
SA-DF	\$109.00	\$95.00	\$75.00

## COMBOS

JERROLD DPV7			
JERROLD DPBB			
SA8580 COMBO	\$299.00	\$225.00	\$215.00
*JERROLD DRX-3-DIC	\$165.00	\$105.00	\$89.00
JERROLD DRZ-3-DIC	\$175.00	\$115.00	\$99.00
*OAK M35B	\$45.00	\$35.00	\$30.00
HAMLIN SPC 4000 3M	\$50.00	\$44.00	\$44.00
ADD \$10.00 FOR VARISYNCH			

## CALL FOR PRICES

\*Refurbished as New

QTY	ITEM	OUTPUT CHANNEL	PRICE EACH	TOTAL PRICE
California Penal Code #593-D Forbids us from shipping any cable descrambling unit to anyone residing in the state of california. Prices subject to change without notice.			SUB TOTAL	
			Shipping Add 5.00 Per unit	
			COD/CreditCard Add 5%	
			TOTAL	

## Please Print

Name \_\_\_\_\_  
Address \_\_\_\_\_ City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_ Tel: ( ) \_\_\_\_\_  
 Cashier's Check  Money order  COD  
 Visa  MC CC# \_\_\_\_\_ Exp. Date \_\_\_\_\_

DECLARATION OF AUTHORIZED USE- I, the undersigned, do hereby declare under penalty of perjury that all products purchased, now and in the future, will only be used on TV systems with all applicable federal and state laws. FEDERAL AND VARIOUS STATE LAWS PROVIDE FOR SUBSTANTIAL CRIMINAL AND CIVIL PENALTIES FOR UNAUTHORIZED USE.

Date \_\_\_\_\_ Signed \_\_\_\_\_

## Cabletronics

9800 D Topanga Canyon Blvd., Suite 323, Chatsworth, CA 91311

For Free Catalog, or to place an order call (800) 433-2011 • FAX (818) 709-7565

# AMAZING ELECTRONIC PRODUCTS and KITS

Remember those Martian Space Ships in HG Wells War of the Worlds?



## MYSTERY Levitating Device

Objects float on air and move to the touch. Defies gravity! Amazing gift, conversation piece, magic trick or great scientific project.

ANT1K Easy-Ass'y Kit/Plans \$19.50



## 3 MILE FM Wireless Microphone!

Crystal clear, ultra-sensitive pickup transmits voices, sounds to any FM radio. For security, monitoring children, invalids. Be the local DJ! MVP1 Plans ..... \$7.00 MVP1K Kit/Plans ..... \$39.50

## 3 MILE Telephone Transmitter!



Automatically transmits 2 sides of phone conversation to any FM radio. Tunable, easy-assembly PC board. Operates only when phone is in use. VVPM7 Plans ..... \$7.00 VVPMK7 Kit/Plans ..... \$39.50



## TV & FM Joker/Jammer

Pocket size device lets you remotely disrupt TV or radio reception. Great gag! Discretion required. Easy-build electronic kit. EJK1KM .... \$19.50

## 100,000 V - 20' Range Intimidation Device!

Electronic module, may be enclosed for handheld, portable, or fixed uses. ITM2 Plans (creditable to kit) \$10.00 ITM2K Kit & Plans ..... \$49.50

## READY-TO-USE, AUTOMATIC Phone Recording System

Complete with extended play tape recorder & line interface switch. Automatically records both sides of conversation. Check Local Laws on Proper Use! Ready-to-Use System. TAP20X System ..... \$149.50

## Laser Pen

Pen sized laser, great for movies, drive-ins, pointer. Ready to use, with batt's. LAPN1 Laser Pen . \$149.50

## Pocket Laser Kit

3mw or 5mw Kits, with solid state 670nm diode. Caution, Class IIIa item. VRL3KM 3mw Laser Kit ... \$99.50 VRL5KM 5mw Laser Kit .. \$119.50

## MORE Laser Kits!

LAS1KM 1mw Laser, 632nm, HeNe Easy to Build Kit ..... \$69.50 LAS4KM 3mw Version, Kit \$99.50

## LAT05 Low Cost HeNe Laser Tube!

.5mw Tube & Plans .. only \$24.50 Other parts available separately. Great Low Budget Science Project!

## Shocker Force Field Vehicle Electrifier



Make hand shock balls, shock wands electrify objects, charge capacitors. Great pay back for those wise guys! SHK1KM Easy-Assembly Kit \$24.50

## CATALOG!

with many more items!  
FREE with order, or send \$1 P&H

## INFORMATION UNLIMITED

Dept RE-4 Box 716, Amherst NH 03031  
Phone 603-673-4730 FAX 603-672-5406  
MC, VISA, COD, Check Accepted. ADD \$5 S&H.

Order by Mail, or by 24 Hr Order Phone: 800-221-1705

## Cable TV Descrambler Kits

Universal Kit..... \$59.95

Includes all parts and PC Board. Not included is the ac adaptor or enclosure.

Tri-Mode Kit.....\$39.00

Includes all parts, PC Board and AC Adaptor. Not included is the enclosure.

SB-3 Kit.....\$29.00

Includes all parts, PC Board and AC Adaptor. Not included is the enclosure.

Universal Tutorial.....\$9.95

Includes an in depth study of the technology used and has troubleshooting hints.

Tri-Mode Tutorial.....\$9.95

Includes a gate by gate study of the circuit and has troubleshooting hints.

Snooper Stopper.....\$39.00

Protect yourself from descrambler detection and stop the "bullet".

Call Toll Free  
1-800-258-1134  
C.O.D.

M & G Electronics, Inc.  
301 Westminister Street  
Providence, RI. 02903

ETCH PCB's yourself, new technique, no chemicals, easy, cheap, full instructions, sharefare, \$1.00, SASE, NICKNAP, Suite 297 CN 1907, Wall, NJ 07719.

MASTERSWITCH. Turns your stereo on/off with your infrared remote television. Information, S.A.S.E. to: PROGRESSIVE CONCEPTS, 1313 North Grand, #291, Walnut, CA 91789.

## BUSINESS OPPORTUNITIES

YOUR own radio station! Licensed/unlicensed AM, FM, TV, cable. Information \$1.00. BROADCASTING, Box 130-F12, Paradise, CA 95967.

LET the government finance your small business. Grants/loans to \$500,000. Free recorded message: (707) 449-8600. (KS1).

EASY work! Excellent pay! Assemble products at home. Call toll free 1 (800) 467-5566 Ext. 5192.

Engineering Manager, Pro Audio Electronics, (Position located in Bethel, CT) to direct and coordinate activities of the Audio Eng. Dept. in the commissioning and maintenance of hard disc based recording systems used in post/video production. Must be able to supervise the commissioning and maintenance of hard disc based recording/editing systems, digital audio processors, and microphones. Minimum 2 yrs. experience with transporter and processor control in an embedded control system required. Forecast operating costs of dept. and direct preparation of budget, performance and evaluation of personnel. Associates degree in Electrical or Electronic Eng.- 1 year experience in position offered or 4 years experience as Service Engineer, Pro Audio Electronics. 40 hrs./week; \$45k/annum (overtime exempt).

Send Resume to: Job Service Technical Unit  
Connecticut Department of Labor  
200 Folly Brook Boulevard  
Wethersfield, CT 06109  
Attention: Job Order No. 3104532

## FREE CATALOG

- CABLE T.V. BOXES - ALL TYPES •
- LOW PRICES - DEALER PRICES •



ACE PRODUCTS  
1-800-234-0726



HOME assembly work available! Guaranteed easy money! Free details! HOMEWORK-R, Box 520, Danville, NH 03819.

MONEYMAKERS! Easy! One man CRT rebuilding machinery. \$6,900.00 rebuilt. \$15,900.00 new. CRT, 1909 Louise, Crystal Lake, IL 60014. (815) 477-8655. FAX (815) 477-7013.

MAKE \$75,000.00 to \$250,000.00 yearly or more fixing IBM color monitors. No investment, start doing it from your home (a telephone required). Information, USA, Canada \$2.00 cash for brochure, other countries \$10.00 US funds. RANDALL DISPLAY, Box 2168-R, Van Nuys, CA 91404 USA. FAX (818) 990-7803.

## CABLE TV DESCRAMBLERS

DEALERS WANTED  
QUANTITY DISCOUNTS ON  
5 OR MORE UNITS

MODEL	5	10	20	50	100
*DTI-3	65	60	50	45	CALL
*SAT-3	55	50	45	40	CALL
*SA-80	120	110	100	95	CALL

\* DTI - Digital Tri-Mode Impulse \* SAT - SCI ATL  
\* SA-80 - SCI ATL 8580 & above

All equipment is new and guaranteed

CALL V.C.I.

1-800-677-0321

Anyone implying theft of service will be denied assistance  
No Florida Sales

LEARN gold, silver, platinum scrap recycling business. (Free) information. Write: RECYCLING, Box 11216PE, Reno, NV 89510-1216.

ELECTRONICS dealers: Expand your product line. Make \$\$\$! Become an AMERICAN ELECTRONICS dealer! Profit opportunities since 1965. Call Scott Pruett, 1 (800) 872-1373.

## ELECTECH

### CABLE T.V. DESCRAMBLERS

- All quality brand names •
  - All fully guaranteed • All the time •
  - Knowledgeable Sales Service Department
- FOR FREE CATALOG 800-253-0099

## WANTED

INVENTORS: We submit ideas to industry. Find out what we can do for you. 1 (800) 288-IDEA.

ELECTRONIC jobs to do at home. 17 years experience. Mil spec quality. Reliable, references (602) 378-3226.

## INVENTORS

INVENTORS! Can you patent and profit from your idea? Call AMERICAN INVENTORS CORP. for free information. Serving inventors since 1975. 1 (800) 338-5656.

FULL- OR PART-TIME JOB/BUSINESS:

## Learn VCR repair!

Professional-level home study program. Master easy-to-learn, high-profit repairs *without* investing in costly high-tech instruments. Send or call today.

**Free career kit:  
800-223-4542**



Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

The School of VCR Repair, Dept. VP342  
2245 Perimeter Park, Atlanta, GA 30341

### EDUCATION & INSTRUCTION

F.C.C. Commercial General Radiotelephone license. Electronics home study. Fast, inexpensive! "Free" details. **COMMAND**, D-176, Box 2824, San Francisco, CA 94126.

**ELECTRONIC engineering**, 8 volumes complete. \$109.95. No prior knowledge required. Free brochure. **BANNER TECHNICAL BOOKS**, 1203 Grant Avenue, Rockford, IL 61103.

**BUILDING A Robot: A Straightforward Approach**, 152 pages fully illustrated. Instructions how you can easily construct a robot. Check or money order. \$19.95 plus \$3.00 shipping. **HUMANFORM ROBOTICS**, PO Box 158486, Nashville, TN 37215.

**CABLE TV DESCRAMBLERS  
★ CONVERTERS ★  
and ACCESSORIES.**

**SAVE MONEY.  
DON'T RENT!**

PANASONIC, JERROLD, OAK,  
PIONEER, SCIENTIFIC ATLANTA  
AND MORE. LOWEST PRICES. FREE CATALOG.

**CABLE READY COMPANY (800) 234-1006**

**CABLE BOX  
WHOLESALE, INC.**

**BEST BOXES—BEST PRICES**

**Immediate Shipping—COD's  
Satisfaction Guaranteed**

**FREE Catalog—Call Now  
800-841-7835**

THIS SPACE CONTRIBUTED AS A PUBLIC SERVICE

**A defense  
against cancer  
can be cooked up  
in your kitchen.**

There is evidence that diet and cancer are related. Follow these modifications in your daily diet to reduce chances of getting cancer:

1. Eat more high-fiber foods such as fruits and vegetables and whole-grain cereals.
2. Include dark green and deep yellow fruits and vegetables rich in vitamins A and C.
3. Include cabbage, broccoli, brussels sprouts, kohlrabi and cauliflower.
4. Be moderate in consumption of salt-cured, smoked, and nitrite-cured foods.
5. Cut down on total fat intake from animal sources and fats and oils.
6. Avoid obesity.
7. Be moderate in consumption of alcoholic beverages.

No one faces cancer alone.

AMERICAN CANCER SOCIETY

Try the

**Electronics  
NOW®**

bulletin board  
system

(RE-BBS)  
516-293-2283

The more you use it the more useful it becomes.

We support 1200 and 2400 baud operation.

Parameters: 8N1 (8 data bits, no parity, 1 stop bit) or 7E1 (7 data bits, even parity, 1 stop bit).

Add yourself to our user files to increase your access.

Communicate with other R-E readers.

Leave your comments on R-E with the SYSOP.

RE-BBS  
516-293-2283

**PLUG INTO  
THE SERVICE,  
SELECTION  
AND VALUE  
MCM  
ELECTRONICS  
PROVIDES**



To get the full power of MCM Electronics' array of products and services, you have to be plugged in. And that's easy. Just call. We'll wire you in to more than 20,000 components and parts; many of them top brand names, others hard-to-find items. We offer connectors, semiconductors, VCR parts and accessories, television components, test equipment, tools and chemicals. Everything you need for computer, audio, video, or telephone repair. We'll give you all the technical assistance you need. Then speed your order to you within 24 hours. That's selection, and service. And that means value to you, and to your customers.

**For A Free Catalog Call:**

**1-800-543-4330**

**To Order By Fax:**

**1-513-434-6959**

**For Product Questions:**

**1-800-824-TECH (8324)**



**MCM ELECTRONICS**  
650 CONGRESS PARK DR.  
CENTERVILLE, OH 45459-4072  
A PREMIER Company

RE-80

December 1992, Electronics Now

105

Courteous Service • Discount Prices • Fast Shipping

# ALL ELECTRONICS CORP.

Mail Order Electronic Parts And Supplies  
P.O. Box 567 • Van Nuys, CA 91408

## LASER POWER SUPPLY



Epoxy encapsulated power supply for up to 2 mW lasers. 4 1/2" X 1 1/2" X 1 7/16".  
Input: 9 Vdc @ 1 amp. Output starting voltage: 7 to 8 kV. Operating voltage: 1.1 to 1.5 kV  
Operating current: 4 to 5 mA. Recessed 0.250 quick connect terminals for output.  
Color coded wire leads for input.  
CAT # LPS-1 \$35.00 each

## RECHARGEABLE Gell Cell Batteries

Maintenance free, rechargeable batteries. Ideal for portable power or back-up power for communications, video, alarms etc. Useable in any position.

### 6 VOLTS @ 1.2 AMP/HOURS

Size: 3.81" X 1" X 2" high.  
CAT# GC-612  
\$6.50 each



### 12 VOLTS @ 10 AMP/HOURS


Two 6 volt 10 AH batteries, assembled as a single 12 volt package. Package size: 6" X 3.94" X 3.75"  
CAT# GC-1210 \$35.00 each


 
## RADIOSONDE WEATHER INFORMATION TRANSMITTER

Viz(r) Radiosonde


A "radiosonde" is a weather instrument, usually released at high altitudes, designed to transmit temperature, humidity, winds and pressure at various heights above the ground. These are new units, discontinued from NOAA national weather service. Contains lots of interesting parts: a solid state transmitter, barometric pressure sensor, humidity sensor and a 24 volt battery which is activated when submerged in water. Great for school science demonstrations or as a source for parts.



CAT# WIT-1 \$4.75 each • Case of 16 for \$64.00
 
## 4 AAA RECHARGEABLE BATTERY PACK (USED)

Battery pack with 4 AAA nickel-cadmium batteries in series to make a 4.8 volt pack. Batteries can be separated and reconfigured if desired. Terminated by 4 pin female connector (0.1" centers) on 4" leads.  
CAT# NCB-43U \$3.00 per pack



## TOLL FREE ORDER LINES

# 1-800-826-5432

CHARGE ORDERS to Visa, MasterCard or Discover

TERMS: Minimum order \$10.00. Shipping and handling for the 48 continental U.S.A. \$3.50 per order. All others including AK, HI, PR or Canada must pay full shipping. All orders delivered in CALIFORNIA must include state sales tax (7.25%, 7.5%, 7.75%, 8.25% 8.5%). Quantities Limited. NO C.O.D. Prices subject to change w/out notice.

Call or Write For Our

FREE 64 Page Catalog

(Outside The U.S.A. Send \$2.00 Postage)

**ALL ELECTRONICS CORP.**

P.O. Box 567 • Van Nuys, CA • 91408

## The World is Talking!



Shortwave Listening Guidebook  
by Harry Helms

Here's your guide to getting the most from a shortwave radio! In clear, nontechnical language, Harry explains how, when, and where to listen in. Its 320 heavily-illustrated pages are packed with advice on:

- antennas
- selecting the right radio
- accessories
- reception techniques

Learn how to hear the BBC, Radio Moscow, ham operators, ships, even spies and "pirate" radio stations! Includes hundreds of station frequencies and the times you can hear them.

Only \$16.95 at radio equipment dealers, or order direct from HighText! Add \$3 shipping (\$4 Canada, \$5 elsewhere). CA add sales tax. U.S. funds only please.

# HighText

publications inc.

7128 Miramar Road, Suite 15L  
San Diego, CA 92121

## WHY RENT? SAVE! SAVE!

### CABLE TV DESCRAMBLERS

JERROLD • OAK • HAMLIN • ZENITH  
PIONEER • SCIENTIFIC ATLANTA

**READY-TO-SHIP!**

6 MONTH WARRANTY! ABSOLUTELY  
LOWEST WHOLESALE / RETAIL PRICES!

MASTERCARD • VISA • AMEX • C.O.D.

FREE COLOR CATALOG!

# 1 (800) 950-9145



1470 OLD COUNTRY ROAD  
SUITE 315-PE  
PLAINVIEW, NY 11803  
NO NY SALES

## CABLE TV DESCRAMBLERS

\*\*\*\*\* STARRING \*\*\*\*\*  
**JERROLD, HAMLIN, OAK**  
AND OTHER FAMOUS MANUFACTURERS

- FINEST WARRANTY PROGRAM AVAILABLE
- LOWEST RETAIL / WHOLESALE PRICES IN U.S.
- ORDERS SHIPPED FROM STOCK WITHIN 24 HRS.
- ALL MAJOR CREDIT CARDS ACCEPTED

FOR ALL INFORMATION  
1-800-345-8927

PACIFIC CABLE CO., INC.  
7325 1/2 Reseda Blvd., Dept 2121  
Reseda, CA 91335

## Cable TV DESCRAMBLERS

30-day  
Money Back  
Guarantee



- > The Most Complete Line of Descramblers
- > Friendly, professional service
- > FREE Catalog

ORDER NOW!



# 1-800-228-7404

Go to the Source

## NU-TEK ELECTRONICS

3250 Hatch RD  
Cedar Park TEXAS 78613

## ANTIQUE RADIO CLASSIFIED

Free Sample!

Antique Radio's  
Largest Circulation Monthly.  
Articles, Ads & Classifieds.

6-Month Trial: \$15. 1-Yr: \$27 (\$40-1st Class).

A.R.C., P.O. Box 802-L9, Carlisle, MA 01741



## FREE CATALOG!

# 1-800-648-7938

JERROLD HAMLIN OAK ETC

## CABLE TV DESCRAMBLERS

- Special Dealer Prices!
- Compare our Low Retail Prices!
- Guaranteed Prices & Warranties!
- Orders Shipped Immediately!

REPUBLIC CABLE PRODUCTS, INC.

4080 Paradise Rd. #15, Dept RE1292  
Las Vegas, NV 89109  
For all other information (702) 362-9026

# BE A GOOD NEIGHBOR

Volunteer.



American Heart Association



# 1-800-831-4242

## Your Resource for Value. Only a Phone Call Away.



### REGULATED POWER SUPPLY KITS

Build the power supply you've been needing for years. Ideal for home or instructional use, select from three different versions. Each kit is complete with printed circuit board, electronic components, and user assembly instructions.

DR73613

Part No.	Product No.	Input Voltage (VAC)	Output Voltage (VDC)	Current (mA)	Dimensions (L x W x H inches)	Price
DR20360	JE200	120	+5	1000	3.5 x 5.0 x 2.0	14.95
DR20626	JE215	120	+5 to +15 -5 to -15	750 to 175 750 to 175	3.5 x 5.0 x 2.0	19.95
DR73613	JE225	120	+5 fixed +3 to +12 -3 to -12	1000 100 100	5.12 x 5.12 x 2.25	29.95

### VOICE SCRAMBLER KIT

Transmit voice messages with complete privacy and security. The Voice Scrambler Kit converts intelligible human speech into unrecognizable garble for recording or transmitting over standard media. The descrambler mode restores the signal to fully intelligible speech. Operate with a cassette tape recorder or build a secure telephone system using a separate kit at each end of the line.

Audio Power Output: 0.5 Watts  
Resolution: 8 bits (companded, Mu-Law)  
Sample Rate: 8 kHz  
Power Supply: +5 & -5 VDC @ 25 mA, +12 VDC @ 250 mA; (recommend power supply DR73613- left)

Dimensions: PCB is 3.55" x 3.10" (LxW)  
Part No. Price  
DR70519.....\$34.95

### TWO-DIGIT VOLTMETER KIT

Now you can build a versatile, practical, high-performance digital panel voltmeter. Finished kits deliver  $\pm 2\%$  accuracy at full scale. Its basic input range of 0.0 to 9.9 VDC is easily scaled for any application.

Input Impedance: 82K with 9.9 VDC range  
Displays: 0.3" red MAN74A type  
Power Supply: +5 VDC, regulated, 100 mA; (recommend power supply DR20360- left)  
Dimensions: 4.3" x 2.2" x 1.3" (LxWxH)

Part No. Price  
DR70527.....\$24.95

### EPROMS

Part No.	Product No.	Price
DR33611	TMS2716	\$5.95
DR39909	2708	4.95
DR40002	2716	3.95
DR40125	2732A-25	3.49
DR40230	2764A-20	3.75
DR39829	27C64-15	3.95
DR39853	27C64-45	2.95
DR39933	27128-25	7.75
DR39968	27128A-20	4.75
DR39984	27128A-25	3.75
DR39677	27C128-15	5.75
DR40037	27256-15	5.49
DR40061	27256-25	4.89
DR39714	27C256-15	5.95
DR39722	27C256-20	5.49
DR40150	27512-20	6.75
DR39781	27C512-15	6.95
DR65699	27C020-15	17.95
DR43692	68766-35	4.95

### Linear ICs\*

Part No.	Product No.	Price
DR33241	TL082CP	\$5.59
DR23579	LM317T	.59
DR23683	LM324N	.35
DR23771	LM336Z	1.09
DR23851	LM339N	.45
DR27422	NE555V	.29
DR24328	LM556N	.49
DR24467	LM723CN	.49
DR24539	LM741CN	.29
DR23131	LM1458N	.39
DR23157	LM1488N	.45
DR23181	LM1489N	.45
DR34278	ULN2003A	.69
DR24230	LM3914N	2.49
DR27385	NE5532	1.19
DR51262	7805T	.45
DR51334	7812T	.45

\* Name brand IC's in stock

### IC Sockets

Part No.	Product No.	Description	Price
DR51570	8LP	8-pin low profile	\$.10
DR37161	14LP	14-pin low profile	\$.11
DR37372	16LP	16-pin low profile	\$.12
DR39335	24LP	24-pin low profile	\$.19
DR40301	28LP	28-pin low profile	\$.22
DR41110	40LP	40-pin low profile	\$.28

### Connectors

Part No.	Product No.	Description	Price
DR15114	DB25P	Male, 25-pin	\$.65
DR15157	DB25S	Female, 25-pin	\$.75
DR15085	DB25H	Hood	\$.39
DR15106	DB25MH	Metal Hood	1.35

### Transistors And Diodes

Part No.	Product No.	Description	Price
DR28628	PN2222	TO-92 case	\$.12
DR28644	PN2907	TO-92 case	\$.12
DR35991	1N4004	DO-41 case	\$.10
DR38236	2N2222A	TO-18 case	\$.25
DR36126	1N4735	DO-41 case	\$.25
DR38359	2N3904	TO-92 case	\$.12
DR36290	1N751	DO-35 case	\$.15
DR38421	2N4401	TO-92 case	\$.15
DR36038	1N4148	DO-35 case	\$.07
DR38308	2N3055	TO-3 case	\$.69

### Switches

Part No.	Product No.	Description	Price
DR21936	JMT123	SPDT, on-on (toggle)	\$.15
DR38842	206-8	SPST, 16-pin (DIP)	1.09
DR26622	MS102	SPST, momentary (push-button)	\$.39

\*Additional components available

### Memory

Part No.	Product No.	Function	Price
DR41398	41256-120	256K DIP	120ns...\$1.69
DR42251	511000P-80	1MB DIP	80ns.....5.99
DR41523	41256A9B-80	256K SIMM	80ns....16.95
DR41718	421000A9A-80	1MB SIPP	80ns....54.95
DR41769	421000A9B-80	1MB SIMM	80ns....54.95

### LEDs

Part No.	Product No.	Description	Price
DR34761	XC556G	T1 3/4, (green)	\$.16
DR34796	XC556R	T1 3/4, (red)	.12
DR34825	XC556Y	T1 3/4, (yellow)	.16

Order toll-free  
1-800-831-4242



Call or write for your  
1993 Annual Catalog:  
1-800-637-8471

**JAMECO™**  
ELECTRONIC COMPONENTS

COMPUTER PRODUCTS

1355 Shoreway Road  
Belmont, CA 94002

FAX: 1-800-237-6948 (Domestic)

FAX: 415-592-2503 (International)

### \$30.00 Minimum Order

For International Sales, Customer Service, Credit Department and all other inquiries: Call 415-592-8097 between 7AM-5PM P.S.T.

CA Residents please add applicable sales tax.

Terms: Prices subject to change without notice. Items subject to availability and prior sale. Complete list of terms/warranties is available upon request.

© 1992 Jameco 12/92 All trademarks are registered trademarks of their respective companies.

### Other Jameco Resources

- Test/Measurement and Prototyping Equipment
- Computer Upgrade and Accessory Products
- Full line of Integrated Circuits and Electronic Components
- Exciting Project Kits for Hobbyists



# THE ELECTRONIC GOLDMINE

**The Electronic Goldmine**  
has one of the greatest selections of unique electronic project kits, gadgets & components. Send for a FREE CATALOG.

**METAL LOCATOR LOCANZA**  
Now the Goldmine offers you a new way to detect coins, buried treasure, buried pipes, etc. These are the basic components of a sensitive high quality (\$40) metal locator. An OEM has been buying new complete metal detectors for months for his own use. The meter, one section of a 2 section pole and the main case. We purchased the other parts from him and by you reconnecting them per our simple instructions and adding your own speaker and/or meter, you can build your own sensitive metal locator at a fraction of the cost of a new one. Here's what you get, a high quality metered 7' cable search coil that has a flexible cable, angle bracket and 1/2" aluminum pole (you can buy a longer pole from your hardware store if you wish), a sophisticated 5 transistor circuit board that has 3 controls: volume, tuning and balance (for ferrous or nonferrous metals). Size of board: 5-1/8" x 3-1/2". These are new functional assemblies and you need only to provide any speaker, any 0-1ma meter (optional as it will also work with only a speaker) and a 9V battery. You can use almost any plastic case that the board, speaker and meter will fit into or just mount the same directly on top of the coil assembly and bring about the case! HURRY, we have a limited quantity and these will sell FAST!

**G2960 \$12<sup>00</sup>**  
Circuit Board, Coil, Speaker and Instructions

**MUSIC MODULE**  
Tiny flat music module made for a greeting card company. Brand new & play "let me call you Sweetheart". Features a flat piezo disk, actuator lever, music IC & battery holder all on a small "PC board". Battery not included but operates from just about any 1.5V hearing aid cell.  
**G2744 \$9<sup>95</sup>**

**INFRARED DETECTOR KIT**  
Great for testing and verification of infrared output. 9V battery not included.  
**C6441 \$5<sup>95</sup>**

**INEXPENSIVE GEIGER COUNTER KIT**  
Detects both Beta and Gamma Rays. 9V battery not included.  
**C6447 \$39<sup>95</sup>**

**PRECISION HIGH SPEED MOTOR**  
Great for Robots, miniature fans, etc. Size 1 1/2" x 9/16". Operates from 1.0VDC up to 9VDC.  
**G2846 1<sup>st</sup> ea 10<sup>8</sup><sup>95</sup>**

**BURGLAR/FIRE ALARM KEYBOARD CONTROL PANEL**  
These are actual size model control panels made for use on home/business burglar fire alarms. They contain 6 bright LEDs, a 12 key control keypad with 7" cable and connector. These are brand new and the LEDs can be lighted with just the addition of a 9V battery to several points on the connector (we show you which ones) to provide you with the most realistic looking "take" burglar alarm. The average burglar is going to think that you have a very sophisticated alarm system installed! Size 4 9/16" square 1/2" thick with 3 molded standoffs under panel. These are a great low market item that can be sold for \$30.00 or more! Order fast to avoid disappointment!

**G2904 \$3<sup>95</sup> ea**  
**10 \$25<sup>95</sup> 100 \$230<sup>95</sup>**

MINIMUM ORDER: \$10.00 plus \$3.50 shipping and handling U.S.A.  
We accept MasterCard, Visa and Money Orders.  
SEND ORDERS TO: The Electronic Goldmine  
P.O. Box 5408 Scottsdale, AZ 85261  
PHONE ORDERS (602) 451-7454 FAX ORDERS (602) 451-9495

CIRCLE 179 ON FREE INFORMATION CARD

## "CABLE BOXES" BELOW WHOLESALE GUARANTEED STOCK - COD'S

### - DESCRAMBLERS -

(QTY)	(10)	(20)	(40)
NEW TBI-3	70	55	CALL
TB 2 or 3	45	40	CALL
SA-3B	45	40	CALL
OAK N-12	43	38	CALL
SB 2 OR 3	43	38	CALL

### COMBINATION UNITS

DRX-DIC	89	CALL
PYL DIC	59	CALL
PIONEER	295	275 CALL

### - CONVERTERS W/REMOTES -

PANASONIC-			
TZPC145	65	60	CALL
STARQUEST-			
E-Z550	65	60	CALL
E-ZY550	75	65	CALL

THEFT OF SERVICE IS A CRIME. INSTALLING ANY DEVICE WITHOUT PERMISSION MAY SUBJECT YOU TO CIVIL OR CRIMINAL PENALTIES. YOU MUST CHECK WITH YOUR LOCAL CABLE COMPANY AND PAY FOR ALL SERVICE YOU USE. IT IS NOT THE INTENT OF LAKE SYLVAN TO DEFRAUD ANY TELEVISION OPERATOR AND WE WILL NOT ASSIST ANY COMPANY OR INDIVIDUAL IN DOING THE SAME.

LAKE SYLVAN SALES, INC.  
SORRY NO MINNESOTA SALES

CALL FOR A CATALOG NOW!!  
**800-800-4582**

CIRCLE 177 ON FREE INFORMATION CARD

# ADVERTISING INDEX

Electronics Now does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page	Free Information Number	Page
—	47th Street Photo	197	Panavise
108	AMC Sales	56	Parts Express
75	Ace Products	78	Radio Shack
107	All Electronics	—	Star Circuits
—	Amazing Concepts	184	TECI
98	Beckman Industrial	178	Tech Spray
190	Beckman Industrial	92	Tektronix
—	Brookstone Production Co.	196	U.S. Cable
109	C & S Sales	192	Viejo Publications
—	CIE	31, 41	Xandi Electronics
183	Cable Warehouse	82	Zentek Corp.
—	Cabletronics	103	
54	Chemtronics	CV4	
181	Cheneko Products	74	
—	CLAGGK Video Offer	CV3	
—	Command Productions	83	
58	Cook's Institute	96	
127	Deco Industries	74	
179	Electronic Goldmine	108	
—	Electronics Book Club	33, 90	
—	Electronic Tech. Today	68	
121	Fluke Manufacturing	CV2	
187	Global Specialties	7	
198	Goldstar Precision	95	
—	Grantham College	13	
86	Heathkit	82	
—	HighText Publications, Inc.	106	
—	ISCET	96	
188	Interactive Image Tech	23	
114	Jameco	101	
185	Kelvin	27	
180	Kepeco Inc.	26	
177	Lake Sylvan Sales, Inc.	108	
199	M&G Electronics	104	
87	MCM Electronics	105	
53	MD Electronics	107	
191	Mark V. Electronics	102	
186	Mini Circuits	3	
—	NRI Schools	18	
194	Northeast Electronics	76	
182	Optoelectronics	17	

### ADVERTISING SALES OFFICE

**Gernsback Publications, Inc.**  
500-B Bi-County Blvd.  
Farmingdale, NY 11735  
1-(516) 293-3000  
President: Larry Steckler  
For Advertising ONLY  
516-293-3000  
Fax 1-516-293-3115  
Larry Steckler  
publisher  
Christina Estrada  
assistant to the President  
Arline Fishman  
advertising director  
Denise Mullen  
advertising assistant  
Kelly McQuade  
credit manager  
Subscriber Customer Service  
1-800-288-0652  
Order Entry for New Subscribers  
1-800-999-7139  
7:00 AM - 6:00 PM M-F MST  
ADVERTISING SALES OFFICES  
EAST/SOUTHEAST  
Stanley Levitan, Eastern Advertising Sales Manager  
Electronics Now  
1 Overlook Ave.  
Great Neck, NY 11021  
1-516-487-9357, 1-516-293-3000  
Fax 1-516-487-8402  
MIDWEST/Texas/Arkansas/Okla.  
Ralph Bergen, Midwest Advertising Sales Manager  
Electronics Now  
One Northfield Plaza, Suite 300  
Northfield, IL 60093-1214  
1-708-446-1444  
Fax 1-708-559-0562  
PACIFIC COAST/Mountain States  
Electronics Now Magazine  
Pamela Kuster  
Pattis/3M  
1800 North Highland Avenue  
Suite 717  
Hollywood, CA 90028  
EN Shopper  
Joe Shere, National Representative  
P.O. Box 169  
Idyllwild, CA 92549  
1-714-659-9743  
Fax 1-714-659-2469

Electronics Now, December 1992

# Countersurveillance

Never before has so much professional information on the art of detecting and eliminating electronic snooping devices—and how to defend against experienced information thieves—been placed in one VHS video. If you are a Fortune 500 CEO, an executive in any hi-tech industry, or a novice seeking entry into an honorable, rewarding field of work in countersurveillance, you must view this video presentation again and again.

Wake up! You may be the victim of stolen words—precious ideas that would have made you very wealthy! Yes, professionals, even rank amateurs, may be listening to your most private conversations.

Wake up! If you are not the victim, then you are surrounded by countless victims who need your help if you know how to discover telephone taps, locate bugs, or "sweep" a room clean.

There is a thriving professional service steeped in high-tech techniques that you can become a part of! But first, you must know and understand Countersurveillance Technology. Your very first insight into this highly rewarding field is made possible by a video VHS presentation that you cannot view on broadcast television, satellite, or cable. It presents an informative program prepared by professionals in the field who know their industry, its techniques, kinks and loopholes. Men who can tell you more in 45 minutes in a straightforward, exclusive talk than was ever attempted before.

## Foiling Information Thieves

Discover the targets professional snoopers seek out! The prey are stock brokers, arbitrage firms, manufacturers, high-tech companies, any competitive industry, or even small businesses in the same community. The valuable information they filch may be marketing strategies, customer lists, product formulas, manufacturing techniques, even advertising plans. Information thieves eavesdrop on court decisions, bidding information, financial data. The list is unlimited in the mind of man—especially if he is a thief!

You know that the Russians secretly installed countless microphones in the concrete work of the American Embassy building in Moscow. They converted



**CALL NOW!**

**1-516-293-3751**

**HAVE YOUR  
VISA or MC CARD  
AVAILABLE**

what was to be an embassy and private residence into the most sophisticated recording studio the world had ever known. The building had to be torn down in order to remove all the bugs.

## Stolen Information

The open taps from where the information pours out may be from FAX's, computer communications, telephone calls, and everyday business meetings and lunchtime encounters. Businessmen need counselling on how to eliminate this information drain. Basic telephone use coupled with the user's understanding that someone may be listening or recording vital data and information greatly reduces the opportunity for others to purloin meaningful information.

The professional discussions seen on the TV screen in your home reveals how to detect and disable wiretaps, midget radio-frequency transmitters, and other bugs, plus when to use disinformation to confuse the unwanted listener, and the technique of voice scrambling telephone communications. In fact, do you know how to look for a bug, where to look for a bug, and what to do when you find it?

Bugs of a very small size are easy to build and they can be placed quickly in a matter of seconds, in any object or room. Today you may have used a telephone handset that was bugged. It probably contained three bugs. One was a phony bug to fool you into believing you found a bug and secured the telephone. The second bug placates the investigator when he finds the real thing! And the third bug is found only by the professional, who continued to search just in case there were more bugs.

The professional is not without his tools. Special equipment has been designed so that the professional can sweep a room so that he can detect voice-activated (VOX) and remote-activated bugs. Some of this equipment can be operated by novices, others require a trained countersurveillance professional.

The professionals viewed on your television screen reveal information on the latest technological advances like laser-beam snoopers that are installed hundreds of feet away from the room they snoop on. The professionals disclose that computers yield information too easily.

This advertisement was not written by a countersurveillance professional, but by a beginner whose only experience came from viewing the video tape in the privacy of his home. After you review the video carefully and understand its contents, you have taken the first important step in either acquiring professional help with your surveillance problems, or you may very well consider a career as a countersurveillance professional.

## The Dollars You Save

To obtain the information contained in the video VHS cassette, you would attend a professional seminar costing \$350-750 and possibly pay hundreds of dollars more if you had to travel to a distant city to attend. Now, for only \$49.95 (plus \$4.00 P&H) you can view *Countersurveillance Techniques* at home and take refresher views often. To obtain your copy, complete the coupon or call.

**CLAGGK INC.** EN  
P.O. Box 4099 • Farmingdale, NY 11735

Please rush my copy of the Countersurveillance Techniques Video VHS Cassette for a total cost of \$53.95 each (which includes \$4.00 postage and handling).

No. of Cassettes ordered \_\_\_\_\_  
Amount of payment \$ \_\_\_\_\_  
Sales tax (N.Y.S. only) \_\_\_\_\_  
Total enclosed \_\_\_\_\_  
Bill me  VISA  MasterCard  
Card No. \_\_\_\_\_  
Expire Date \_\_\_\_\_ / \_\_\_\_\_  
Signature \_\_\_\_\_  
Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ ZIP \_\_\_\_\_

All payments in U.S.A. funds. Canadians add \$4.00 per VHS cassette. No foreign orders.

## SODER-WICK® FACTS # 1: The Desoldering System.

Soder-Wick® Fine-Braid is uniquely designed for each desoldering application, from SMT pads to large wire connectors. This ultra-pure, oxygen-free copper is engineered in an open-weave pattern that provides near-perfect capillary action. Solder is wicked cleanly away, without damaging the board or surrounding components.

Choose from nine widths and three flux arrangements, including static dissipative packaging for ESD-sensitive operations. Call us at 1-800-SOS-WICK and get all the facts on the Soder-Wick System.

**SII**  
**SODER-WICK® FINE-BRAID**  
The State of the Art in Desoldering.

## SODER-WICK FACTS # 22:

# The SMT Wick.

Soder-Wick® Ultra-Braid is designed for precision cleaning tight-tolerance SMT pads. This ultra-pure, oxygen-free copper wire is engineered for superior thermal conductivity which ensures lower heat transfer and faster wicking action.

Solder and contaminants are quickly removed, without affecting surrounding pads or integrated circuits.

Call us at 1-800-SOS-WICK and get all the facts.

**SII**  
**SODER-WICK® FINE-BRAID**  
The State of the Art in Desoldering.

## SODER-WICK® FACTS # 12:

# The Fastest-Acting Wick.

Soder-Wick® Fine-Braid exceeds the desoldering rate specified by Mil Standard 883B, Method 2022. This ultra-pure, oxygen-free copper wire is engineered for superior thermal conductivity, which lowers heat transfer and won't cause damage to the board or surrounding components.

Soder-Wick® Fine-Braid is designed for desoldering operations from SMT pads to large wire connectors. Call us at 1-800-SOS-WICK and get all the facts on the Soder-Wick System.

**SII**  
**SODER-WICK® FINE-BRAID**  
The State of the Art in Desoldering.

## SODER-WICK® FACTS # 7:

# The Static Dissipative System

Soder-Wick's unique Static Dissipative blue bobbin packaging qualifies under DOD Standard 1686 and DOD Handbook 263, and meets the decay rate provision specified in MIL-B-81705B. Soder-Wick Fine-Braid and Ultra-Braid in the SD blue bobbin provide maximum protection for circuit boards and components during ESD-sensitive operations.

Soder-Wick® is engineered for desoldering applications from SMT pads to large wire connectors. Call 1-800-SOS-WICK for all the facts on the Soder-Wick System.

**SII**  
**SODER-WICK® FINE-BRAID**  
The State of the Art in Desoldering.  
CIRCLE 54 ON FREE INFORMATION CARD